

ELECTRIC CIRCUITS

ECSE-2010


Fall 2002

Class 3

REVIEW

- **Kirchhoff's Laws: KCL, KVL**
 - **Current In = Current Out**
 - **Sum of Voltages Around a Closed Path = 0**
- **Series: $R_{eq} = R_1 + R_2 + R_3 + ..$**
- **Parallel: $1/R_{eq} = 1/R_1 + 1/R_2 + 1/R_3 + ...$**


KIRCHHOFF'S LAWS

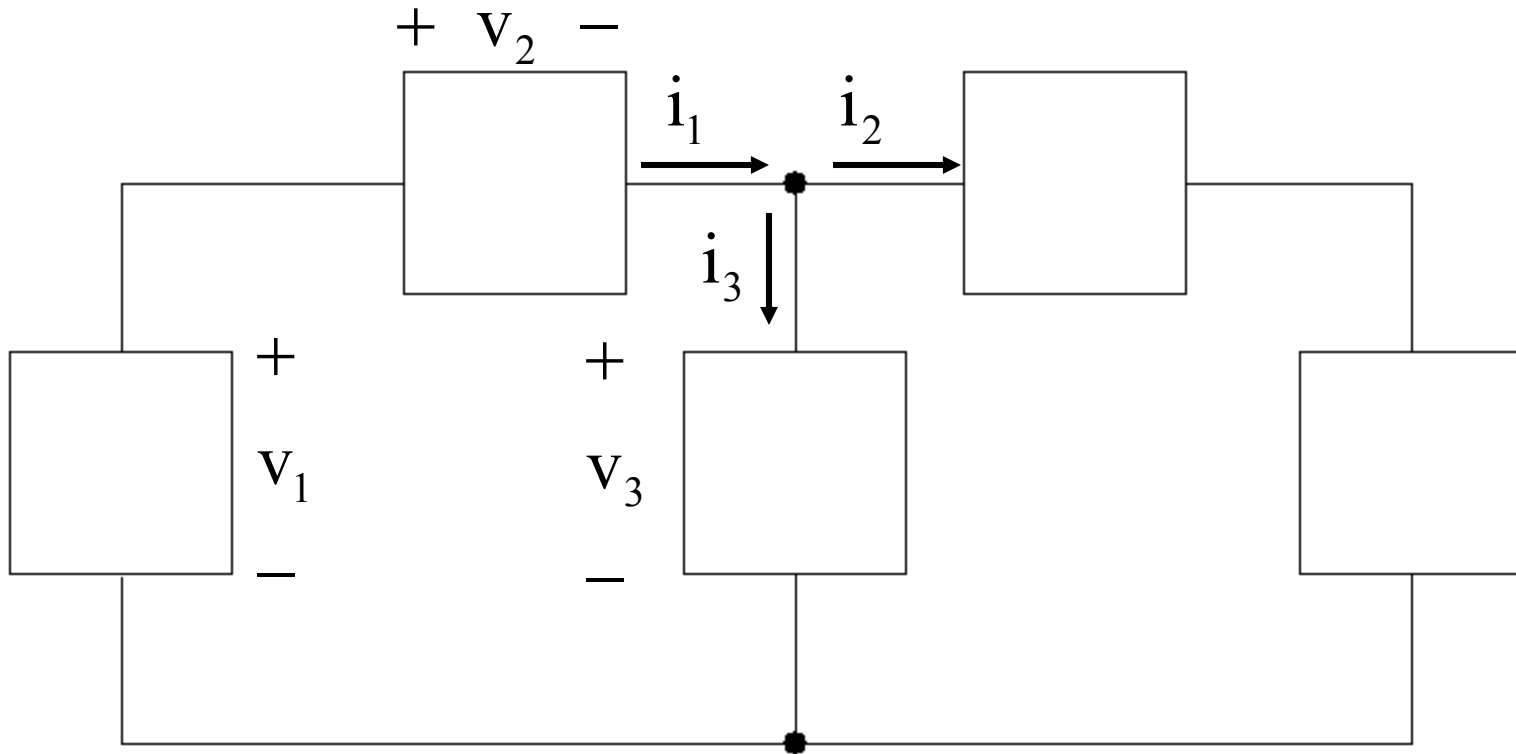

$$\text{KCL: } i_1 = i_2 + i_3$$

$$\text{KVL: } v_1 = v_2 + v_3$$

RESISTORS IN SERIES

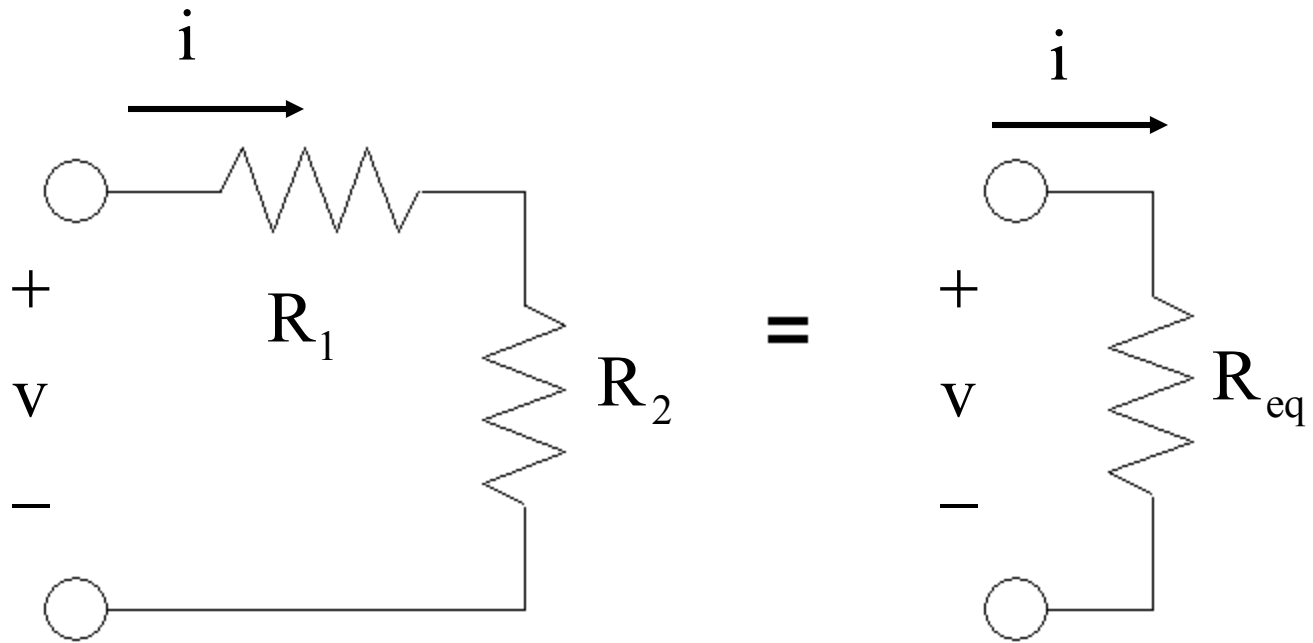

$$R_{eq} = R_1 + R_2$$

VOLTAGE DIVIDER RULE

- $v_1 = i R_1 = V/R_{eq} \times R_1$
 - $v_1 = [R_1/(R_1 + R_2)] V$


$$V_1 = \frac{R_1}{R_1 + R_2} V$$

- $v_2 = i R_2$
 - $v_2 = [R_2/(R_1 + R_2)] V$

$$V_2 = \frac{R_2}{R_1 + R_2} V$$

- **Elements in Series**
 - $v_1 \sim R_1$
 - $v_2 \sim R_2$

RESISTORS IN PARALLEL

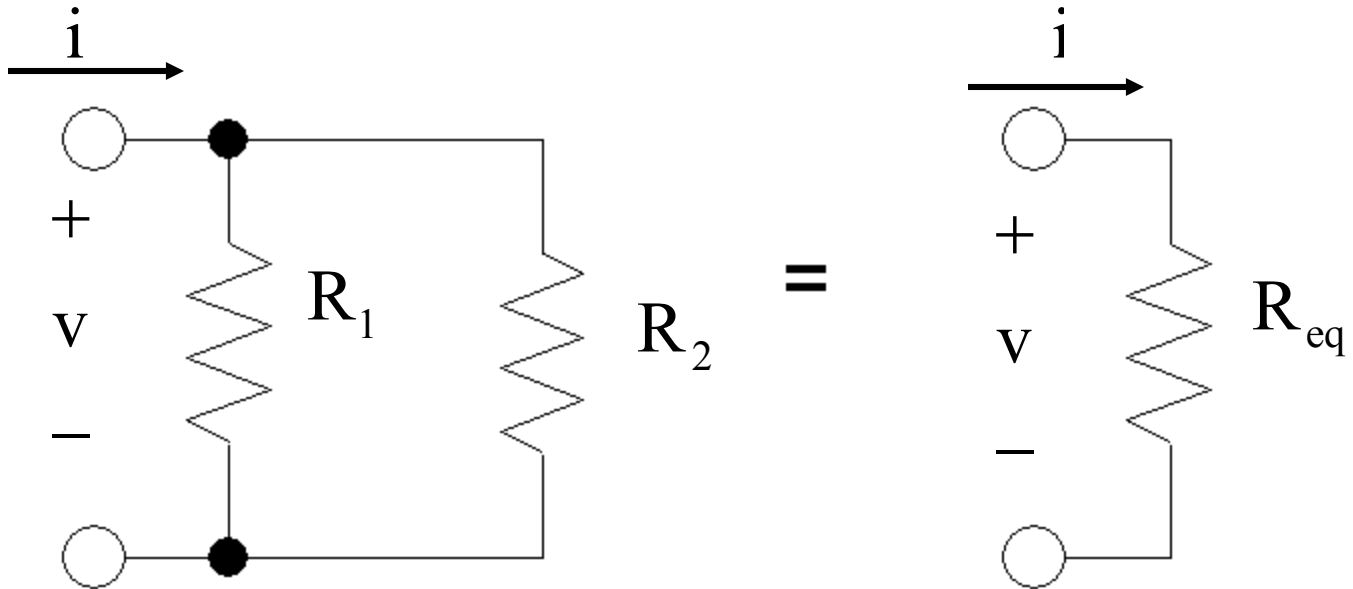

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

CURRENT DIVIDER RULE

- $i_1 = [R_2 / (R_1 + R_2)] i$ $i_1 = \frac{R_2}{R_1 + R_2} i$

- $i_2 = [R_1 / (R_1 + R_2)] i$ $i_2 = \frac{R_1}{R_1 + R_2} i$

- **Elements in Parallel**

- $i_1 \sim R_2$
- $i_2 \sim R_1$

PSPICE

- **Widely Used Simulation Package**
 - Industry Standard for Circuits and Electronics
- **Student Version is FREE**
 - <http://cadencepcb.com/products/downloads/PSpicestudent/default.asp>
 - We will use PSpice A/D and Probe primarily
 - Will also want to use Schematics; possibly Capture
- **Get a Copy and Use it Often**

PSPICE

- **P Spice has Many Rules:**
 - Will build up slowly
- **Use P Spice for Circuits that are Computationally Challenging:**
- **Will Often Analyze a Circuit to Learn Principles - Then “test” with P Spice:**


STEPS FOR PSpICE

- **Create Simulation Diagram:**
 - Original Circuit
 - Label Nodes, Name Elements, Identify Sources
- **Create Circuit File:**
 - Must save as <filename>.cir
 - Tells PSpice what to do
- **Run PSpice and Observe Output**
 - Usually using Probe
- **OR – Use Schematics**
 - Draw Circuit in Schematics and run PSpice

SIMULATION DIAGRAM

- **Circuit Diagram but with all Nodes and all Elements Labeled for PSpice**
- **Each Node must have a unique Number**
- **Each Element must have both a Name and a Value**
 - **Both Active and Passive Elements**

SIMULATION DIAGRAM

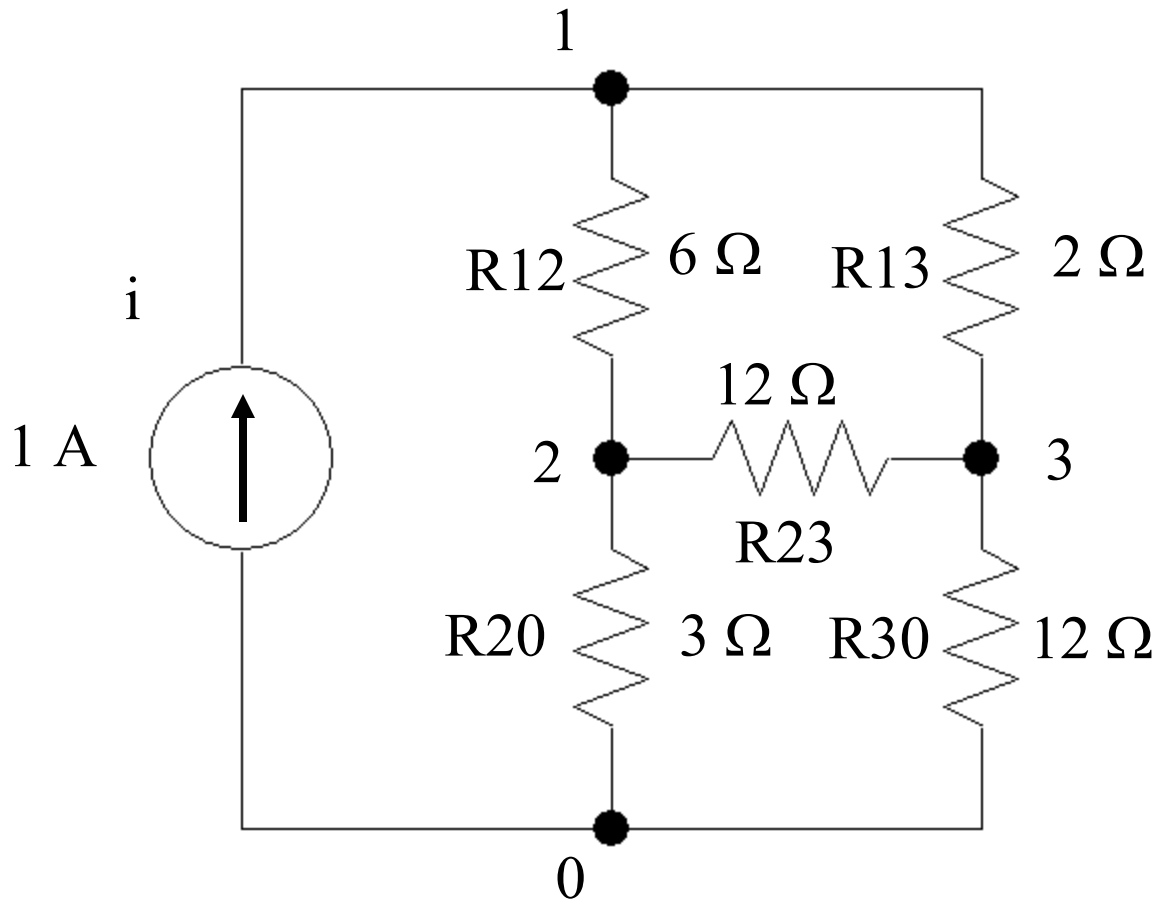

Simulation Diagram for PSpice

CIRCUIT FILES

- **Circuit File Describes Circuit to PSpice and Tells PSpice What to Do:**
- **First Line Not Used by PSpice: => Name**
- **To Describe a Current Source:**

i2 0 1 DC 1

Name of Source = i2; “i” means current (i or I)

Current flows from Node 0 to Node 1

DC Source

1 Amp

CIRCUIT FILES

- **To Describe a Voltage Source**

v4 1 0 DC 2

Name of Source = v4; “v” means voltage

Positive terminal is Node 1

Negative terminal is Node 0

DC Source

2 Volts

CIRCUIT FILES

- **Resistors:**

R45 2 3 12

Name of Resistor = R45; “R” => Resistor

Connected between Nodes 2 and 3

Positive Terminal is Node 2

Negative Terminal is Node 3

Resistance is 12 ohms

COMMANDS

```
.dc lin i1 -1, 1, 0.1
```

Perform a DC Analysis

Do a Linear Sweep

Sweep the variable named i1

**Sweep from -1 Amp to +1 Amp in steps of
0.1 Amps**

COMMANDS

.probe


Tells PSpice to run Probe after performing the specified circuit analysis

.end

Tells PSpice that the file is at the end

Will Add More Commands Later

ACTIVITY 3-1

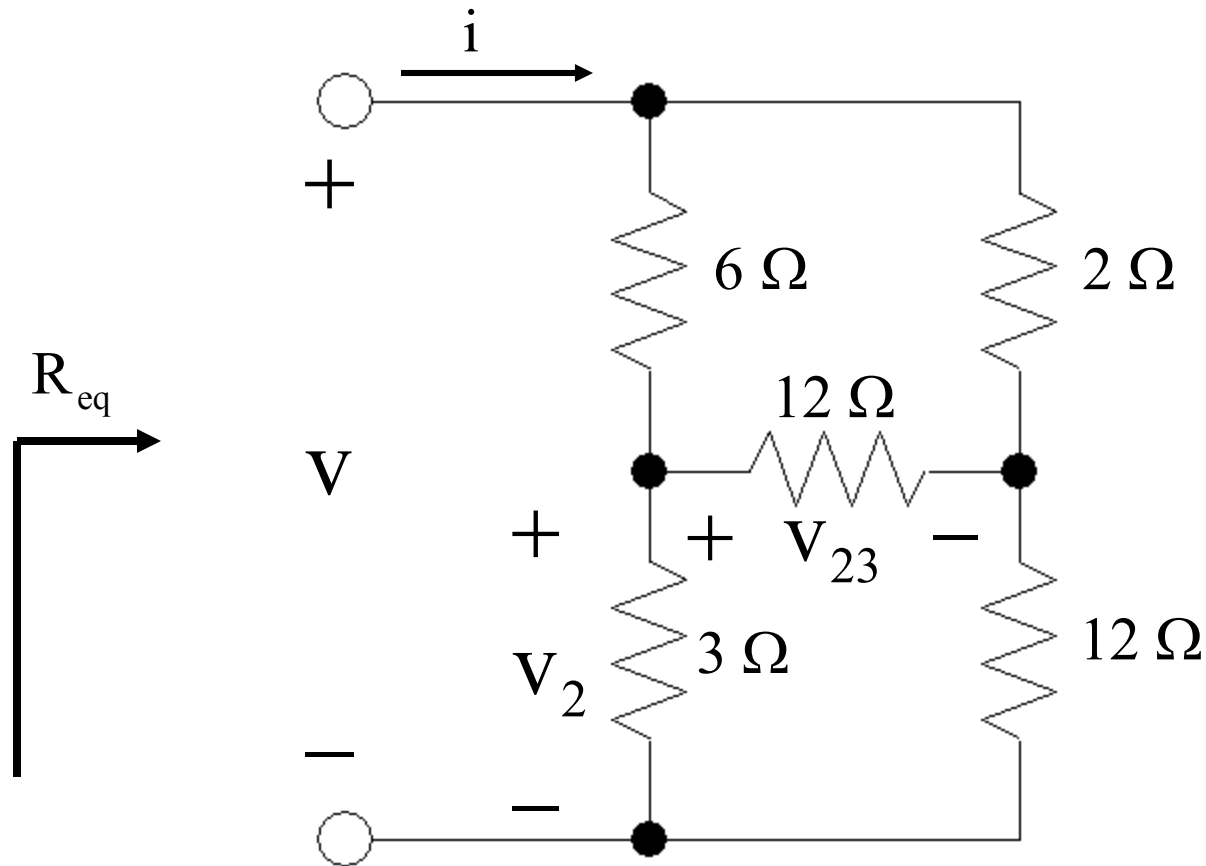


Find v_2 and v_{23}

Resistive Bridge Circuit

ACTIVITY 3-1

- **Cannot use Series/Parallel Reduction for this Circuit**
 - Nothing is in Series or Parallel
- **Plot i vs v (or v vs i)**
 - Slope = $1 / R_{eq}$ (or Slope = R_{eq})
- **Let's Do Using PSpice**

ACTIVITY 3-1

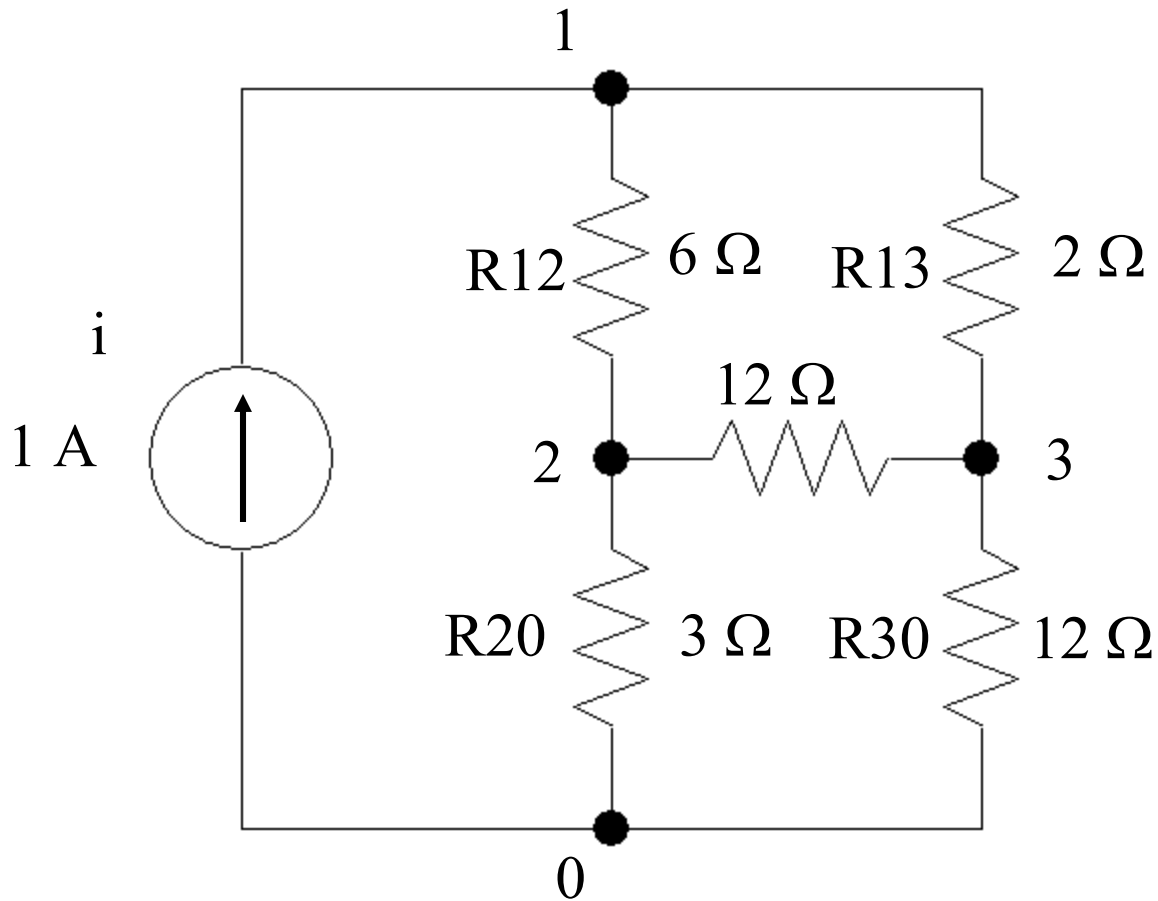

Simulation Diagram for PSpice

ACTIVITY 3-1

- **Circuit File**


Activity 2-2 * PSpice does not use first line

```
i          0          1          dc          1
R12        1          2          6
R13        1          3          2
R23        2          3          12
R20        2          0          3
R30        3          0          12
.dc lin    i          -1,          1,          0.1
.probe
.end
```

ACTIVITY 3-1

- **Save Circuit File as <name>.cir**
- **Open PSpice A/D**
- **Open <name>.cir**
- **Under Simulation – Run <name>.cir**
- **Probe comes up automatically**
- **x axis = i**
- **Add Trace: v(1), v(2), v(2) – v(3)**
- **$R_{eq} = 5 \text{ Ohms}$**

ACTIVITY 3-1

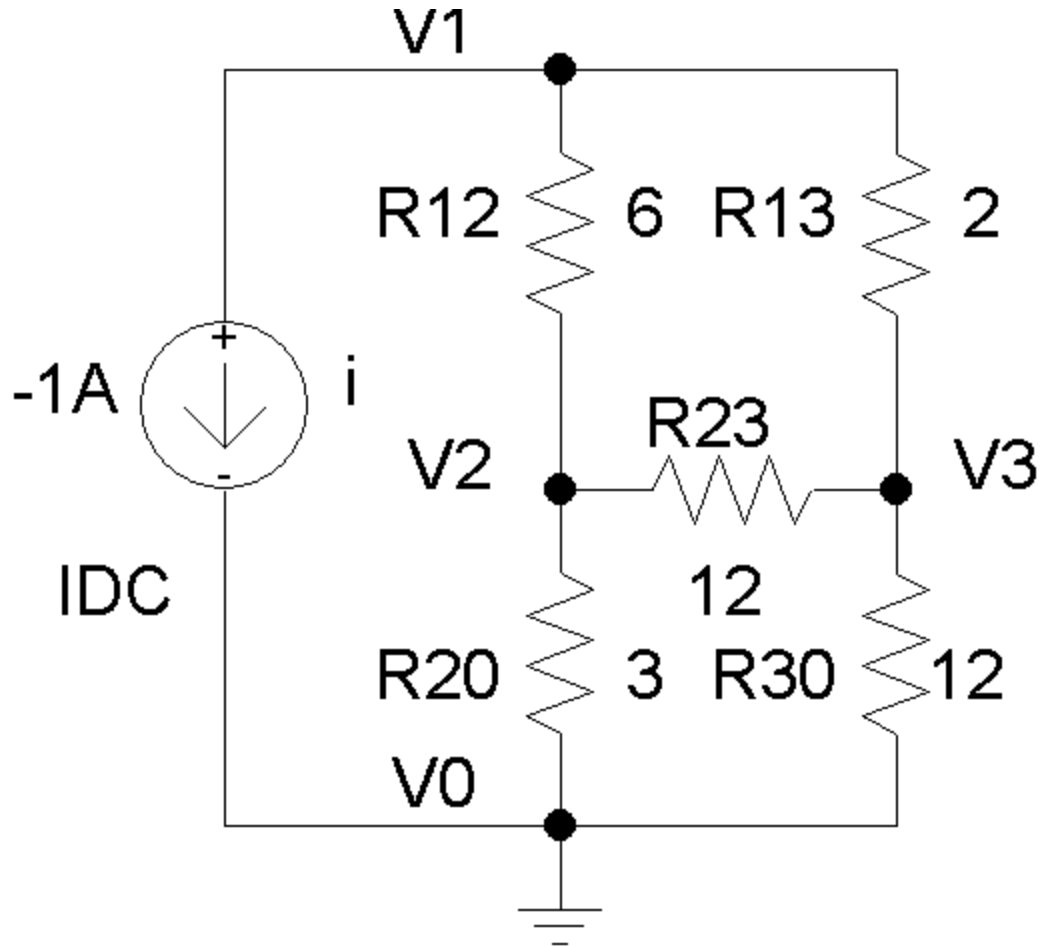

USING SCHEMATICS


ACTIVITY 3-1

- **SCHEMATICS:**
 - Schematics uses Passive Convention for Sources
 - Note Current Arrow points in “wrong” direction
 - Must put in – 1 Amp Source
 - Add extra “wires” so you can label them
 - v1, v2, v3
 - Use DC Sweep
 - Sweep i from –1 to +1
 - Run Simulation
 - Change x axis variable to from i to – i
 - Add Trace; v1, v2, v2 - v3

MULTIMETER MEASUREMENTS


- **Model for Real Voltmeter:**
 - Ideal Voltmeter in Parallel with R_M
 - Ideal Voltmeter Draws No Current
 - $R_M = \text{“large”}$; Typically a few Mohms
- **Model for Real Ammeter:**
 - Ideal Ammeter in Series with R_m
 - Ideal Ammeter has no voltage drop
 - $R_m = \text{“small”}$; Typically a few ohms

VOLTMETER

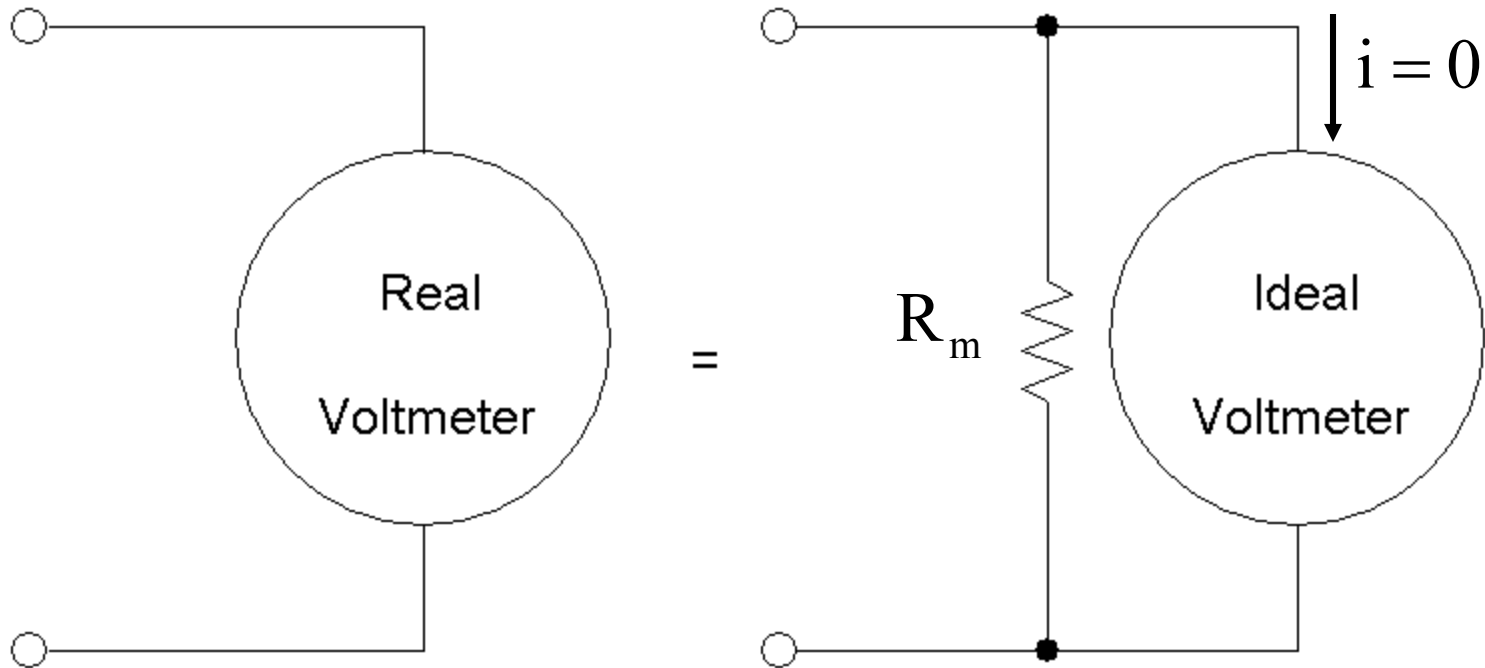


R_m = Meter Resistance
= Large (few $M\Omega$'s)

AMMETER

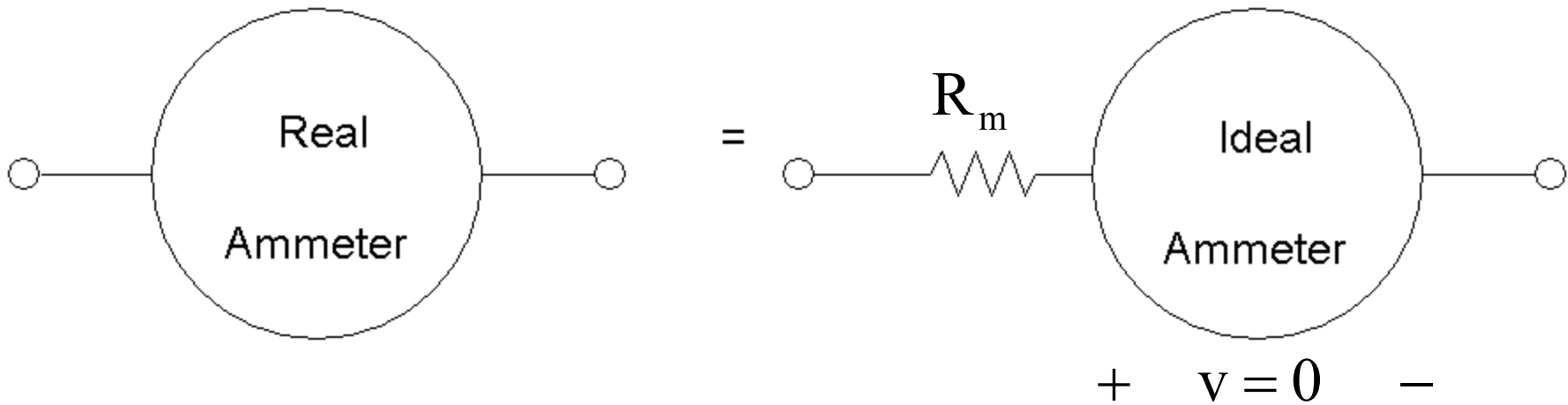


R_m = Meter Resistance
= Small (few Ω 's)

EXAMPLE

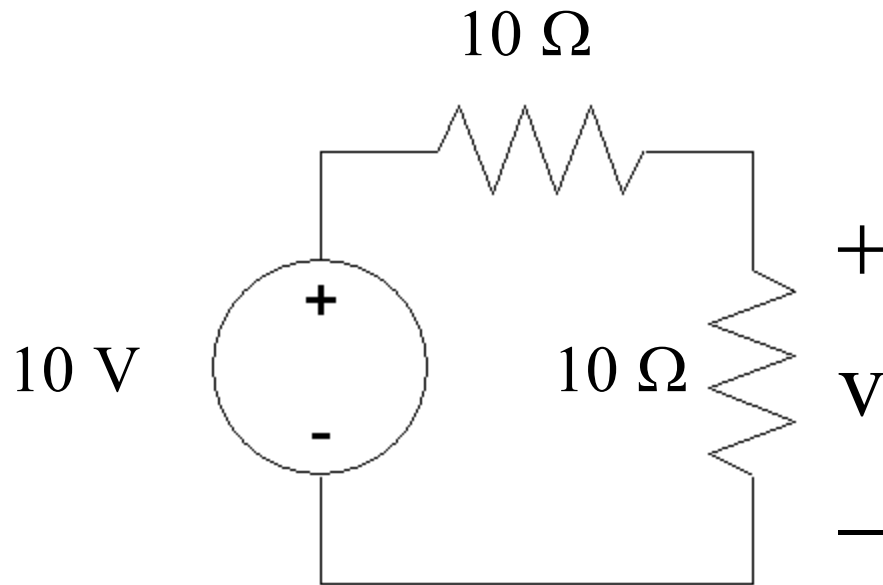

$$v = \frac{10}{10 + 10} (10) = 5 \text{ Volts}$$


EXAMPLE

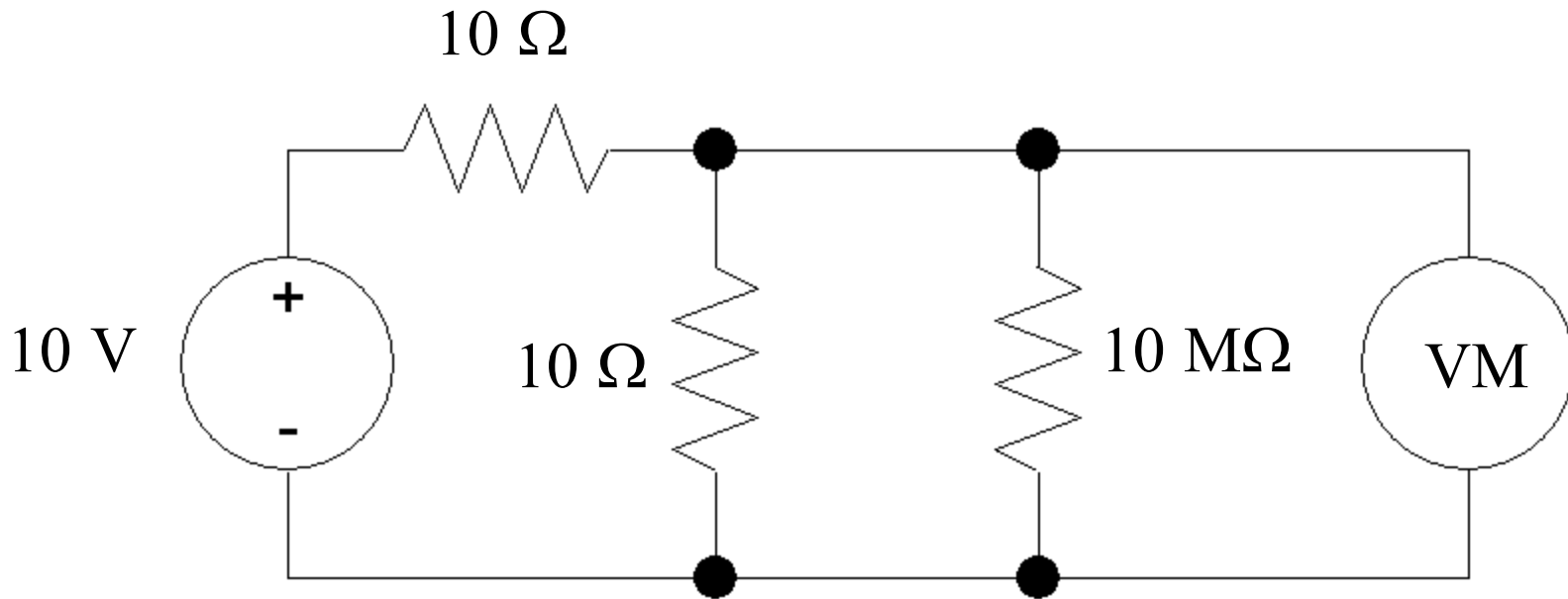

$$R_{\text{eq}} = 10 \parallel 10 \text{ M} \approx 10 \Omega$$

VM reads ≈ 5 Volts

EXAMPLE

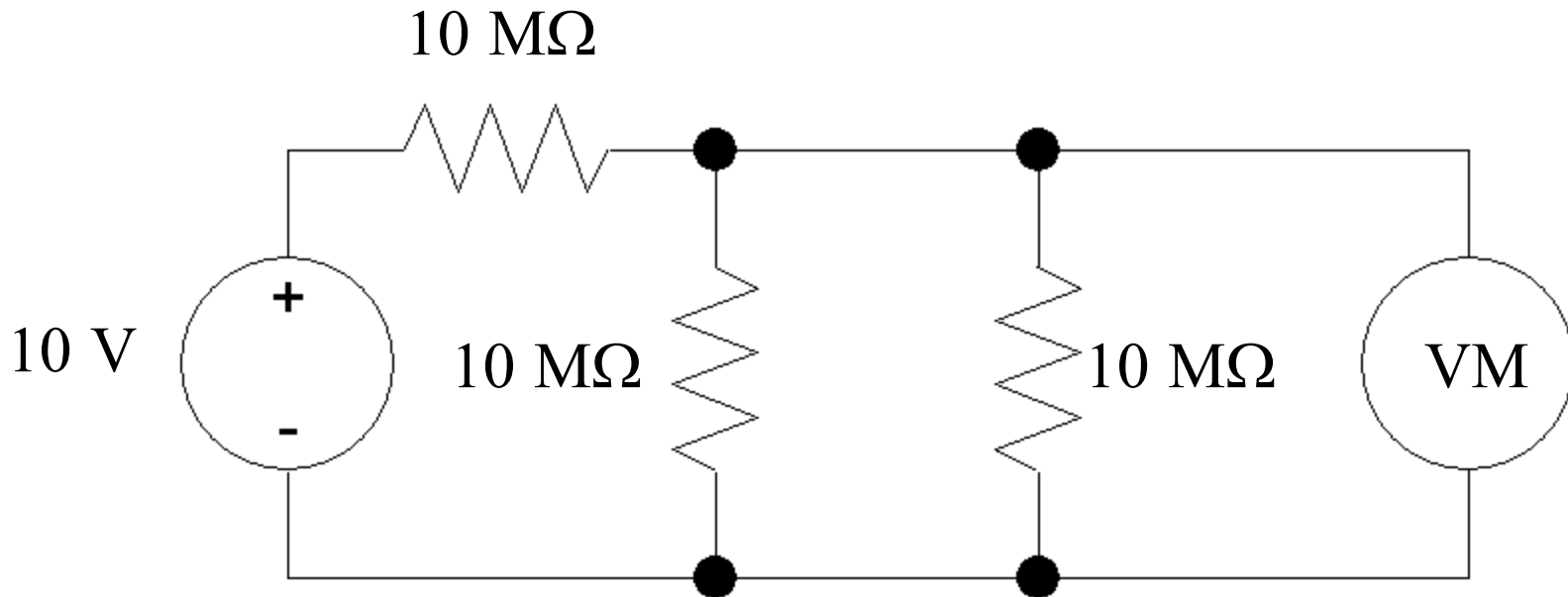

$$R_{eq} = 10 \text{ M} \parallel 10 \text{ M} = 5 \text{ M}\Omega$$

$$\text{VM reads } \frac{5}{5+10} (10) = 3.33 \text{ Volts}$$

Meter affects the measurement

EXPERIMENT 1

- **Use E3631A Voltage Source:**
 - + 25 V output; +, Com
 - Adjust output to be + 12 Volts
- **Think About Model for Ammeter:**
 - **With Switch Open; Current flows thru Meter**
 - Measures current as if Switch were Closed
 - **With Switch Closed; Current flows thru Switch**
 - Ammeter measures 0; as if Switch were Open

EXPERIMENT 1

