

Canonical Forms and Logic Minimization

Today:

- **First Hour: Canonical Forms**
 - Section 2.2.2 of Katz's Textbook
 - In-class Activity #1
- **Second Hour: Incomplete Functions, Introduction to Logic Minimization**
 - Section 2.2.4 and 2.2.1 of Katz's Textbook
 - In-class Activity #2

1

minterms

#	A	B	C	minterms
0	0	0	0	$A' B' C' = m_0$
1	0	0	1	$A' B' C = m_1$
2	0	1	0	$A' B C' = m_2$
3	0	1	1	$A' B C = m_3$
4	1	0	0	$A B' C' = m_4$
5	1	0	1	$A B' C = m_5$
6	1	1	0	$A B C' = m_6$
7	1	1	1	$A B C = m_7$

Shorthand notation for minterms of 3 variables

5

SOP Shorthand

Shorthand notation for SOP expressions

$$F(A,B,C) = A' B C + A B' C' + A B' C + A B C' + A B C$$

$$= \sum m(3,4,5,6,7)$$

$$F(A,B,C)' = A' B' C' + A' B' C + A' B C'$$

$$= \sum m(0,1,2)$$

6

POS Shorthand

Shorthand notation for POS expressions

A	B	C	F	\bar{F}
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F(A,B,C) = (A + B + C) \cdot (A + B + C') \cdot (A + B' + C)$$

$$= \prod M(0,1,2)$$

$$F(A,B,C)' = (A + B' + C') \cdot (A' + B + C) \cdot (A' + B' + C')$$

$$= \prod M(3,4,5,6,7)$$

10

Do Activity #1 Now

• Reference: Section 2.2.2 of Katz's Textbook

- **Minterms: (Shorthand)**
 - m_0, m_1, \dots etc
 - $\sum m(0,1,\dots)$
- **Minterms: (Canonical)**
 - $A' B' C', A' B' C \dots$ etc
 - $A' B' C' + A' B' C + \dots$ etc
- **Maxterms: (Shorthand)**
 - M_0, M_1, \dots etc
 - $\prod M(0,1,\dots)$
- **Maxterms: (Canonical)**
 - $(A' + B' + C), (A' + B' + C'), \dots$ etc
 - $(A' + B' + C) \cdot (A' + B' + C') \cdot \dots$ etc

12

Don't Cares & Canonical Forms

Shorthand Representation

Representation of "D" in BCD

$$D(A,B,C,D) = m_4 + m_3 + m_5 + m_7 + m_9$$

$$+ d_{11} + d_{13} + d_{15}$$

$$= \sum [m(1,3,5,7,9) + d(11,13,15)]$$

$$D(A,B,C,D) = M_0 \cdot M_2 \cdot M_4 \cdot M_6 \cdot M_8$$

$$\cdot D_{10} \cdot D_{12} \cdot D_{14}$$

$$= \prod [M(0,2,4,6,8) \cdot D(10,12,14)]$$

15

Alternative Gate Realizations

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Two-Level Realization
(inverters don't count)

Multi-Level Realization
Advantage: Reduced Gate Fan-ins

Complex Gate: XOR
Advantage: Fewest Gates

20

Simplifying Equations

Example: full adder's carry out function

$$Cout = A \cdot B \cdot Cin + A \cdot B' \cdot Cin + A \cdot B \cdot Cin' + A \cdot B' \cdot Cin'$$

Alternative	Equation	Group
[9]	$(A' + A) B Cin + A B' Cin + A B Cin' + A B Cin$	[8]
[9]	$(1) B Cin + A B' Cin + A B Cin' + A B Cin$	[5]
[9]	$B Cin + A B' Cin + A B Cin' + A B Cin$	[10] [9]
[9]	$B Cin + A(B' + B) Cin + A B Cin' + A B Cin$	[8]
[9]	$B Cin + A(1) Cin + A B Cin' + A B Cin$	[5]
[9]	$B Cin + A Cin + A B (Cin' + Cin)$	[10] [8]
[9]	$B Cin + A Cin + A B (1)$	[5]
[9]	$B Cin + A Cin + A B$	[10]

NOTE: Minimization is just an exercise in applying laws of Boolean Algebra learnt earlier!

22

Do Activity #2 Now

Due: End of Class Today

RETAIN THE LAST PAGE (#3)!!

For Next Class:

- Bring Randy Katz Textbook

- **Required Reading:**
 - Sec 2.2.1 & 2.3 (omit 2.3.6) of Katz

- This reading is necessary for getting points in the Studio Activity!

23