

ECSE 2010  
Electric Circuits  
Exam 3  
Spring 2004

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12

**2**

MWR  
4-6

**3**

MTR  
2-4

| Problem No. | Pts.   | Score |
|-------------|--------|-------|
| 1           | 20pts  |       |
| 2           | 20pts  |       |
| 3           | 20pts  |       |
| 4           | 20pts  |       |
| 5           | 20pts  |       |
| Total       | 100pts |       |

Please Note:

- \* Place all your answers in the spaces provided.
- \* You MUST show your work to receive any credit.

**Problem 1 (20pts)**

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

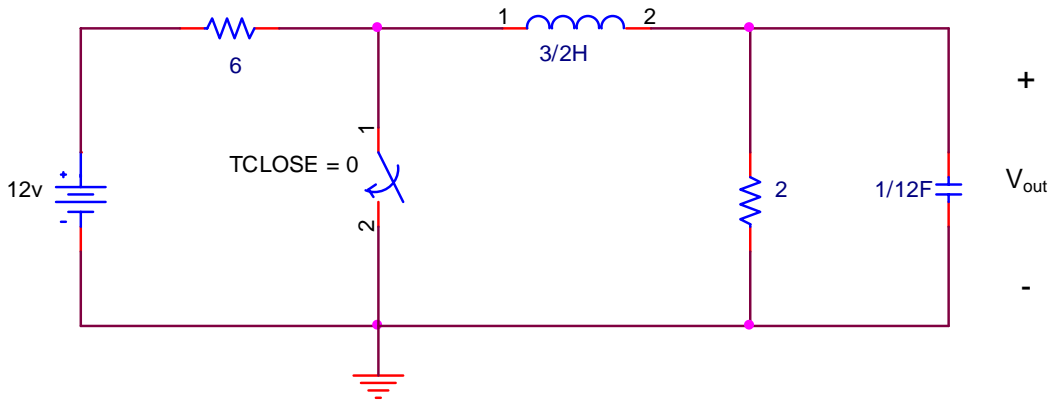**3**

MTR  
2-4

a.) Find  $I_L(0^-)$  and  $V_C(0^-)$  in the circuit shown. (4pts)



|            |  |
|------------|--|
| $I_L(0^-)$ |  |
| $V_C(0^-)$ |  |

Problem 1 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

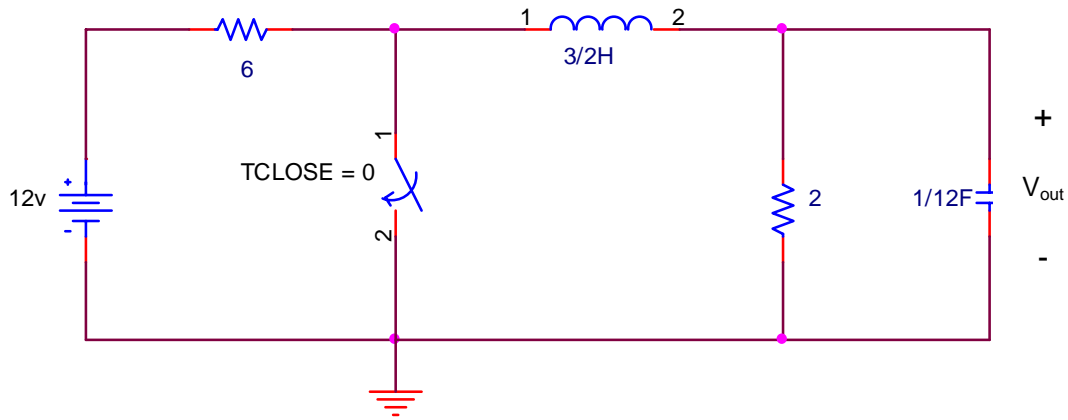**3**

MTR  
2-4

b.) Find  $V_{out}(s)$  for  $t > 0$  (same circuit as in part a). (10pts)



|              |  |
|--------------|--|
| $V_{out}(s)$ |  |
|--------------|--|

Problem 1 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

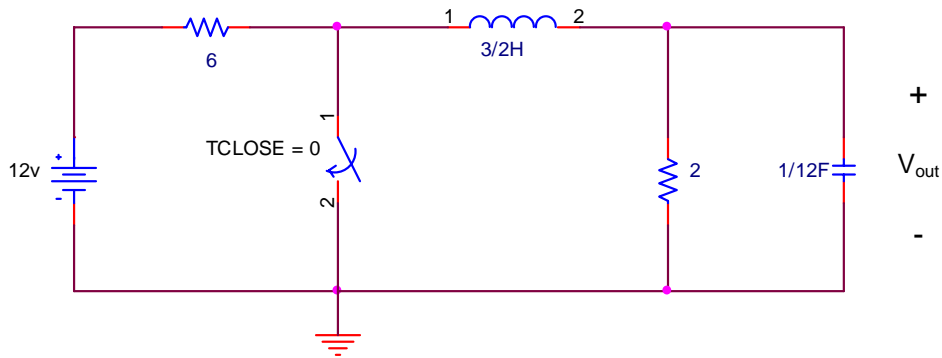**3**

MTR  
2-4

c.) Find  $V_{out}(t)$  for  $t \geq 0$  (same circuit as in parts a & b). (6pts)



|              |  |
|--------------|--|
| $V_{out}(t)$ |  |
|--------------|--|

Problem 2 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

**2**


**3**

MTR  
10-12

MWR  
4-6

MTR  
2-4

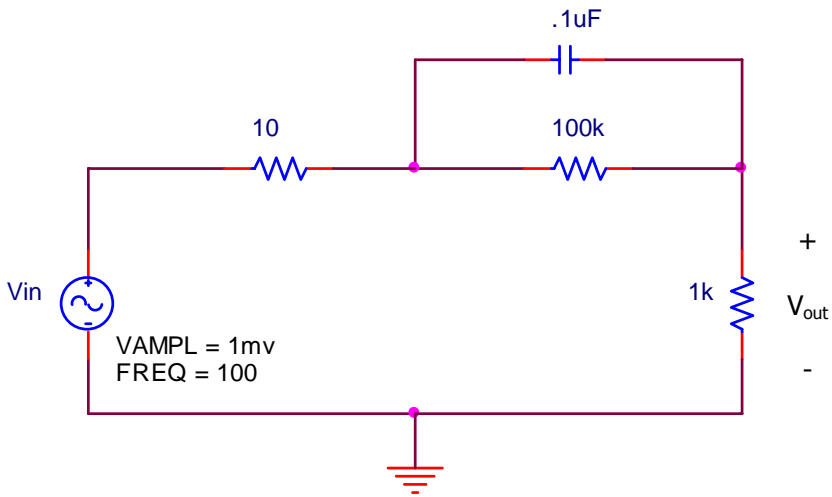a.) Find  $V_{out}(t)$  in the circuit shown if  $V_{in}(t) = 1\text{mV} \cos(200\pi t)$ . (10pts)



|              |  |
|--------------|--|
| $V_{out}(t)$ |  |
|--------------|--|

Problem 2 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

**2**


**3**

MTR  
10-12

MWR  
4-6

MTR  
2-4

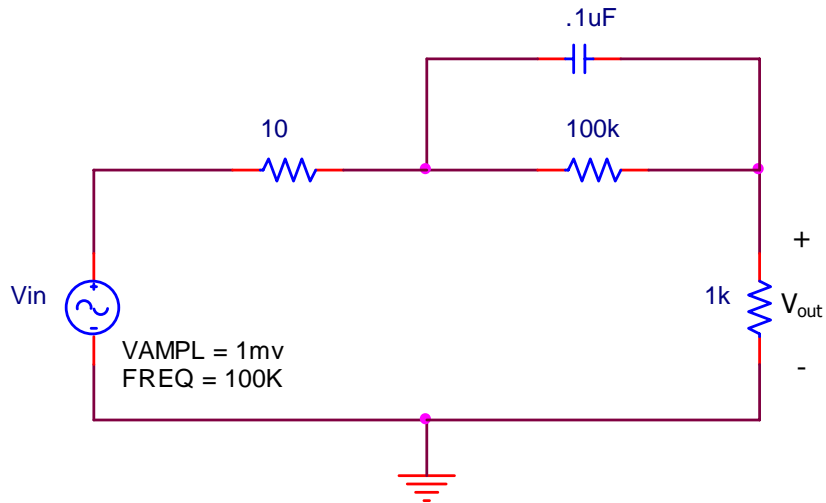b.) Find  $V_{out}(t)$  in the circuit shown if  $V_{in}(t) = 1\text{mV} \cos(200,000\pi t)$ . (10pts)



|              |  |
|--------------|--|
| $V_{out}(t)$ |  |
|--------------|--|

**Problem 3 (20pts)**

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

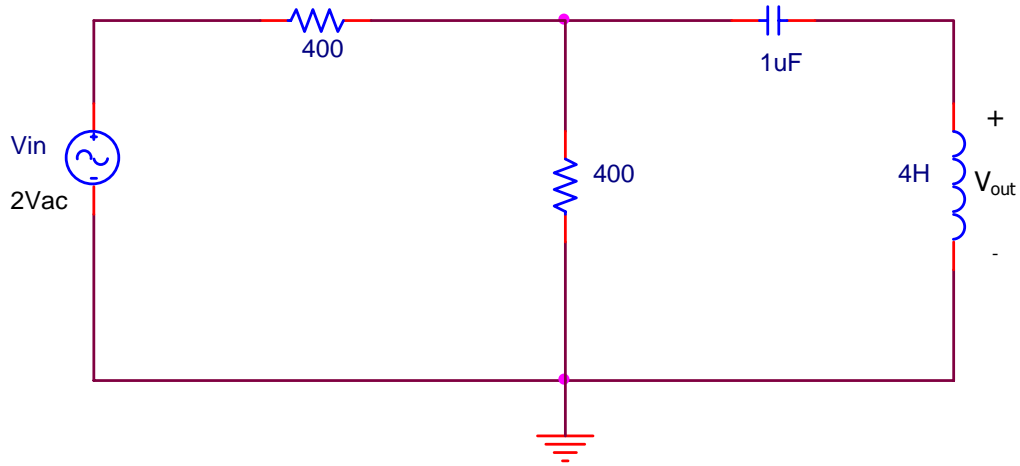**3**

MTR  
2-4

a.) Find  $H(s) = V_{out}/V_{in}$  for the circuit shown below. (10pts)



|        |  |
|--------|--|
| $H(s)$ |  |
|--------|--|

Problem 3 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

**3**

MTR  
2-4

b.) Sketch the asymptotic graphs of  $|H(j\omega)|$  and  $\Phi(j\omega)$  for the circuit shown. (10pts) (Please be sure to label and mark your axes as appropriate)

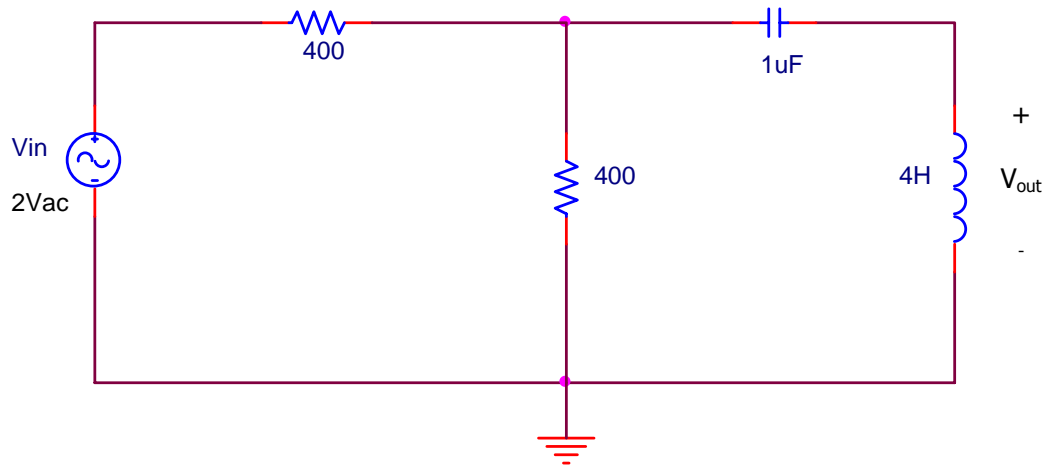

**Problem 4 (20pts)**

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

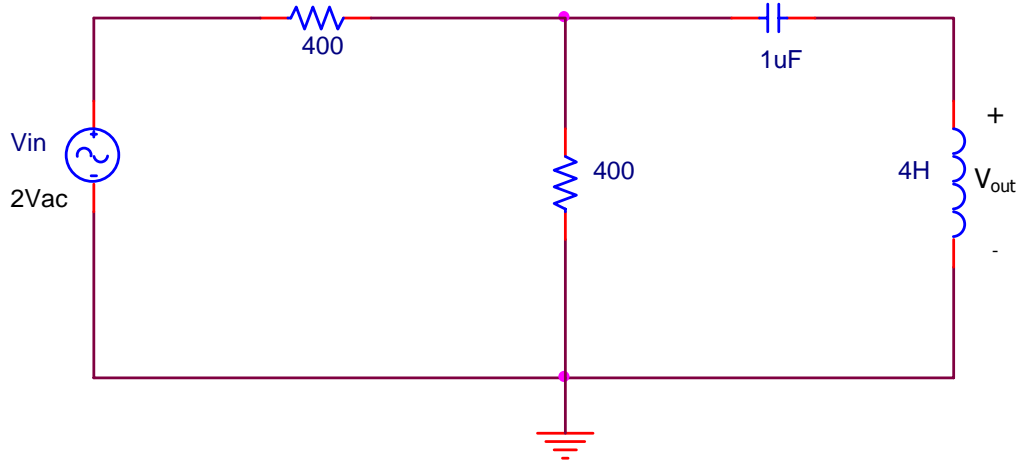**3**

MTR  
2-4

a.) What frequency ( $\omega_0$ ) of  $V_{in}$  would cause the circuit shown below to resonate? (10pts) (Please justify your response)



|            |  |
|------------|--|
| $\omega_0$ |  |
|------------|--|

b.) What is the Q of the circuit shown above? (5pts)

|   |  |
|---|--|
| Q |  |
|---|--|

c.) What is the magnitude  $|V_{out}|$  of the circuit shown above at  $\omega_0$ ? (5pts)

|             |  |
|-------------|--|
| $ V_{out} $ |  |
|-------------|--|

Problem 5 (20pts)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12


**2**

MWR  
4-6

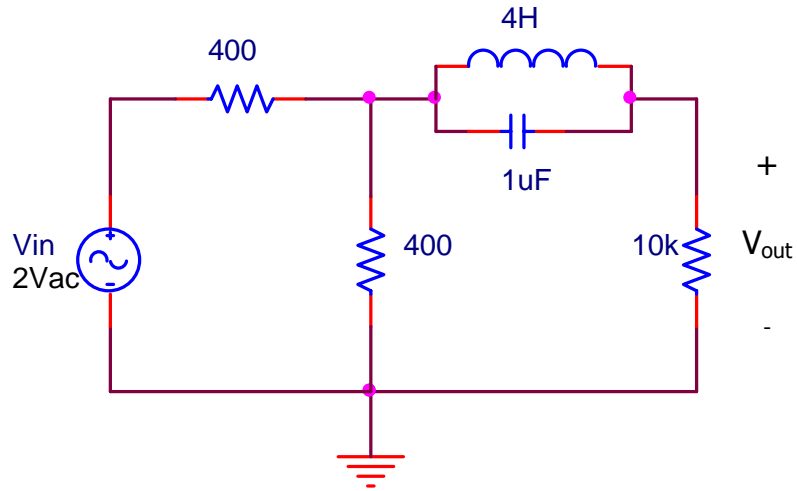**3**

MTR  
2-4

a.) What kind of frequency response would the circuit shown have? (10pts)



(Please circle one and justify your response in the space provided below)

|                 |                |                 |              |
|-----------------|----------------|-----------------|--------------|
| Bandpass filter | Lowpass filter | Highpass filter | Notch filter |
|-----------------|----------------|-----------------|--------------|

Problem 5 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

**2**


**3**

MTR  
10-12

MWR  
4-6

MTR  
2-4

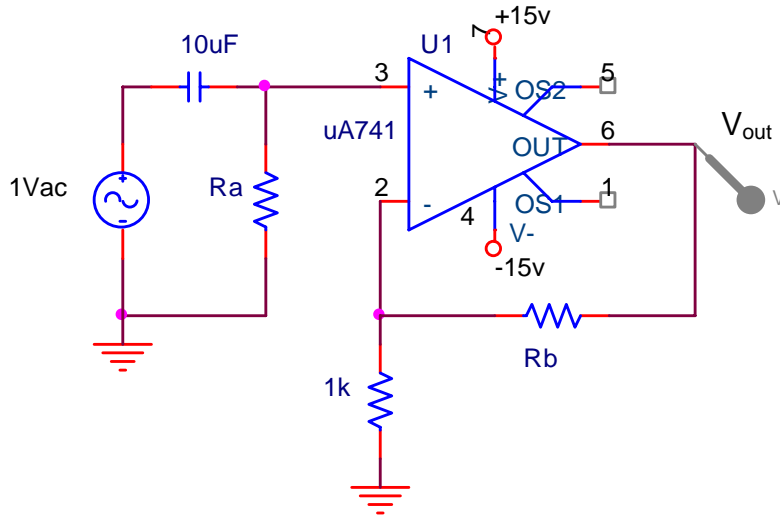b.) What values of **R<sub>a</sub>** and **R<sub>b</sub>** in the following circuit could produce the frequency plots shown on the following page? (10pts)



|                |  |
|----------------|--|
| R <sub>a</sub> |  |
| R <sub>b</sub> |  |

# Problem 5 (cont)

Name \_\_\_\_\_

Section Number (please circle one)

**1**



MTR  
10-12

**2**

MWR  
4-6

**3**

MTR  
2-4

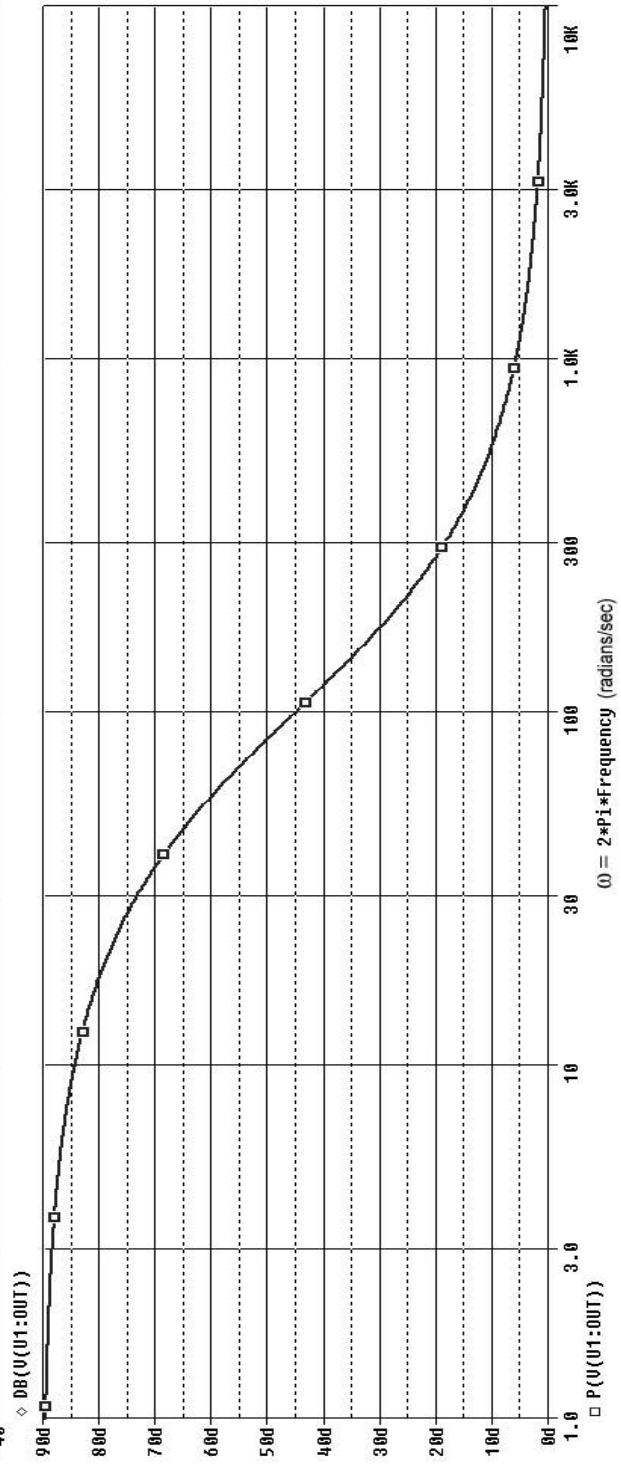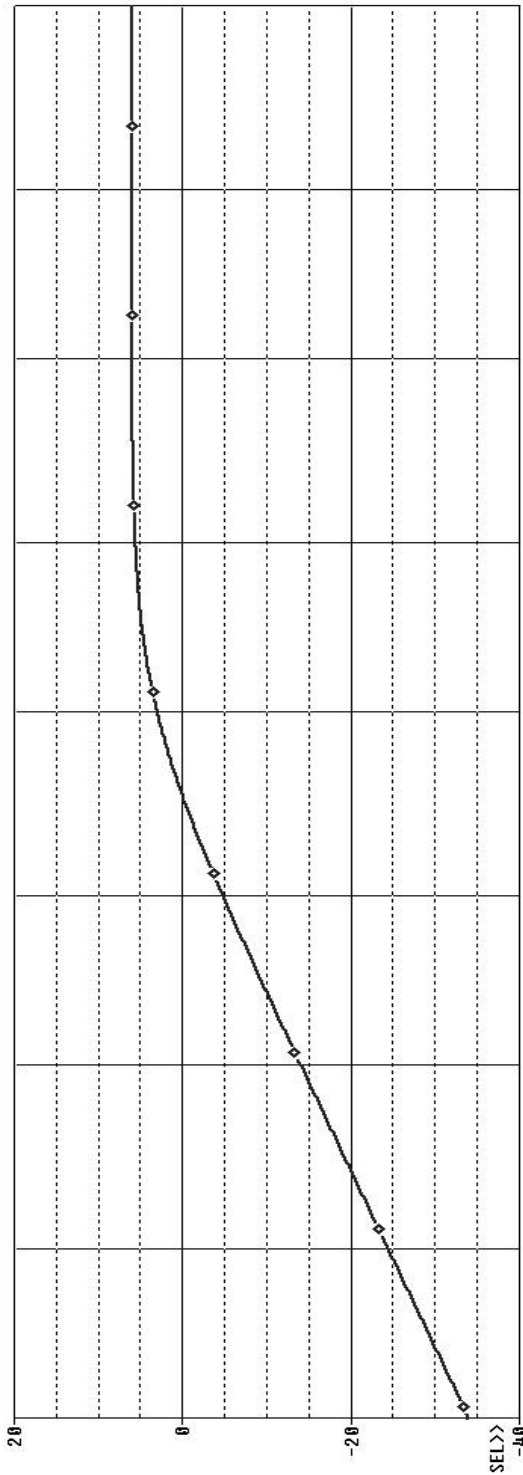

Extra space (if needed)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12

**2**

MWR  
4-6

**3**

MTR  
2-4

Extra space (if needed)

Name \_\_\_\_\_

Section Number (please circle one)

**1**

MTR  
10-12

**2**

MWR  
4-6

**3**

MTR  
2-4

### *Laplace Transform Theorems*

- |                             |  |
|-----------------------------|--|
| 1. Definition               | $L[f(t)] = F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt$                                    |
| 2. Linearity                | $L[k_1 f(t_1) + k_2 f(t_2)] = k_1 F_1(s) + k_2 F_2(s)$                                   |
| 3. Time shift               | $L[f(t - \tau)] = e^{-\tau s} F(s)$  |
| 4. Frequency Shift          | $L[e^{-at} f(t)] = F(s + a)$   |
| 5. Scaling Theorem          | $L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$                                       |
| 6. Differentiation Theorem  | $L\left[\frac{df}{dt}\right] = sF(s) - f(0)$   |
| 7. Differentiation Theorem  | $L\left[\frac{d^2 f}{dt^2}\right] = s^2 F(s) - sf(0) - \dot{f}(0)$                       |
| 8. Differentiation Theorem  | $L\left[\frac{d^n f}{dt^n}\right] = s^n F(s) - \sum_{k=1}^n s^{n-k} f^{(k-1)}(0)$        |
| 9. Integration Theorem      | $L\left[\int f(\tau) d\tau\right] = \frac{F(s)}{s} + \frac{\int_{0^+} f(\tau) d\tau}{s}$ |
| 10. Final value theorem*    | $f(\infty) = \lim_{s \rightarrow 0} sF(s)$   |
| 11. Initial value theorem** | $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$   |

\* Provided all poles of  $F(s)$  have negative real parts with the exception of possibly one pole at the origin.

\*\* Provided  $f(t)$  is continuous or has a step discontinuity at  $t = 0$ .

### *Laplace Transform of Time Functions*

|     |   |   |
|-----|---|---|
| 1.  | $\delta(t)$   | 1   |
| 2.  | $u(t)$  | $1/s$   |
| 3.  | $tu(t)$   | $1/s^2$   |
| 4.  | $\frac{1}{2!}t^2u(t)$   | $1/s^3$   |
| 5.  | $\frac{1}{(m-1)!}t^{m-1}u(t)$   | $1/(s^m)$   |
| 6.  | $e^{-at}u(t)$   | $1/(s+a)$   |
| 7.  | $te^{-at}u(t)$  | $1/(s+a)^2$   |
| 8.  | $\frac{1}{(m-1)!}t^{m-1}e^{-at}u(t)$  | $1/(s+a)^m$   |
| 9.  | $(1 - e^{-at})u(t)$   | $a/[s(s+a)]$  |
| 10. | $\frac{1}{a}(at - 1 + e^{-at})u(t)$   | $a/[s^2(s+a)]$  |
| 11. | $(1 - at)e^{-at}u(t)$   | $s/(s+a)^2$   |
| 12. | $\sin(\omega t)u(t)$  | $\omega/(s^2 + \omega^2)$                                   |
| 13. | $\cos(\omega t)u(t)$  | $s/(s^2 + \omega^2)$  |
| 14. | $e^{-at} \cos(\omega t)u(t)$  | $(s+a)/[(s+a)^2 + \omega^2]$                                |
| 15. | $e^{-at} \sin(\omega t)u(t)$  | $\omega/[(s+a)^2 + \omega^2]$                               |
| 16. | $\left\{ 1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} [\sin(\omega_d t + \theta)] \right\} u(t)$                       |   |
|     | $\omega_d = \omega_n \sqrt{1-\zeta^2}; \quad \theta = \cos^{-1}(\zeta)$   |   |
| OR  | $\left\{ 1 - e^{-\zeta\omega_n t} \left[ \cos(\omega_d t) + \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_d t) \right] \right\}$ | $\frac{\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$ |

**Laplace Transform of Time Functions (cont)**

$$F(s) = \frac{Bs + C}{s^2 + 2\alpha s + \omega_0^2}$$

$$L^{-1}[F(s)] = f(t)$$

17.

$$f(t) = Ae^{-\alpha t} \cos(\omega_d t + \phi), \text{ where}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \phi = \tan^{-1}\left(\frac{\alpha B - C}{\omega_d B}\right) \text{ and}$$

$$A = \sqrt{B^2 + \left(\frac{\alpha B - C}{\omega_d}\right)^2} = \frac{\sqrt{B^2 \omega_0^2 - 2\alpha BC + C^2}}{\omega_d}$$