

ECSE 2010
Electric Circuits
Exam 3
Spring 2004

Name

Solutions - Dr

Section Number (please circle one)

1

MTR
10-12

2

MWR
4-6

3

MTR
2-4

Problem No.	Pts.	Score
1	20pts	X/20
2	20pts	X/20
3	20pts	X/20
4	20pts	X/20
5	20pts	X/20
Total	100pts	X/100

Please Note:

- * Place all your answers in the spaces provided.
- * You MUST show your work to receive any credit.

Problem 1 (20pts)

Name Solutions Jim



Section Number (please circle one)

1
MTR
10-12

2
MWR
4-6

3
MTR
2-4

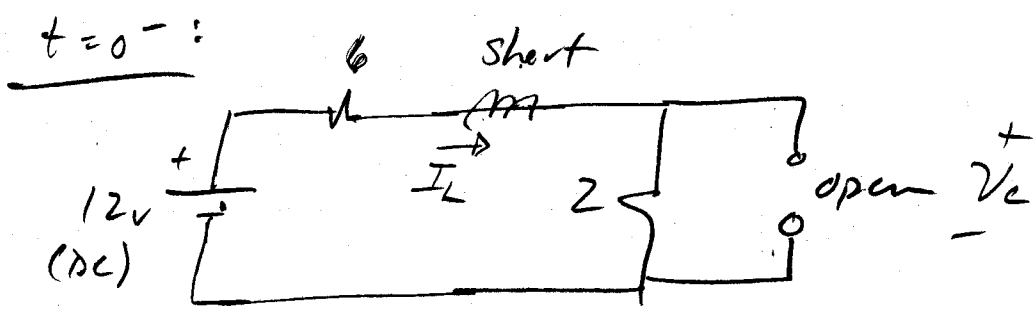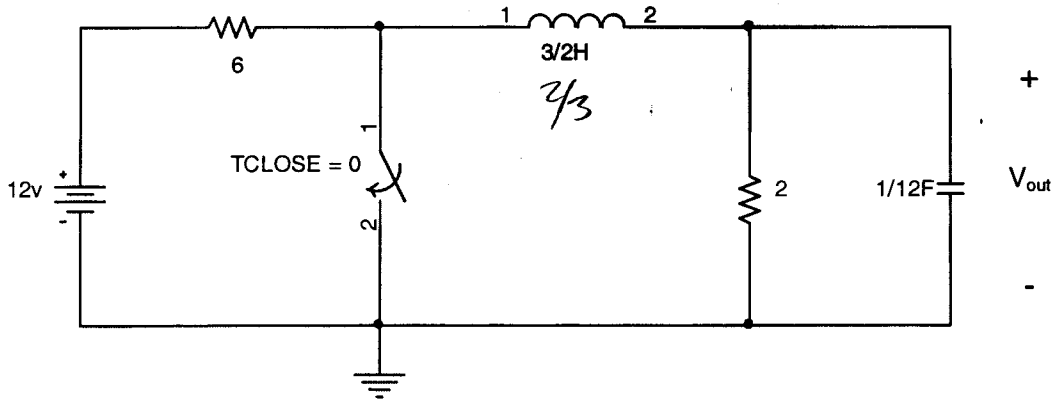a.) Find $I_L(0^-)$ and $V_c(0^-)$ in the circuit shown. ~~(9pts)~~ (10pts)



$$V_c(0^-) = 12v \frac{2}{2+6} = 3v$$

$$I_L(0^-) = \frac{3v}{2} = 1.5A$$

$I_L(0^-)$	1.5 Amps
$V_c(0^-)$	3 volts

Problem 1 (cont)

Name Solutions - JM

Section Number (please circle one)

1

2

3

MTR

MWR


MTR

10-12


4-6

2-4

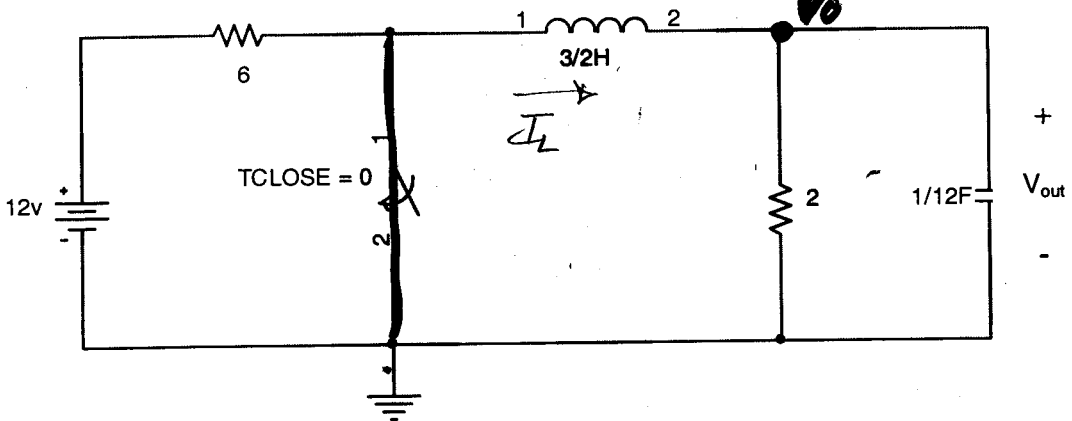b.) Find $V_{out}(s)$ for $t > 0$ (same circuit as in part a). ~~(10pts)~~ (5pts)



$t > 0$:

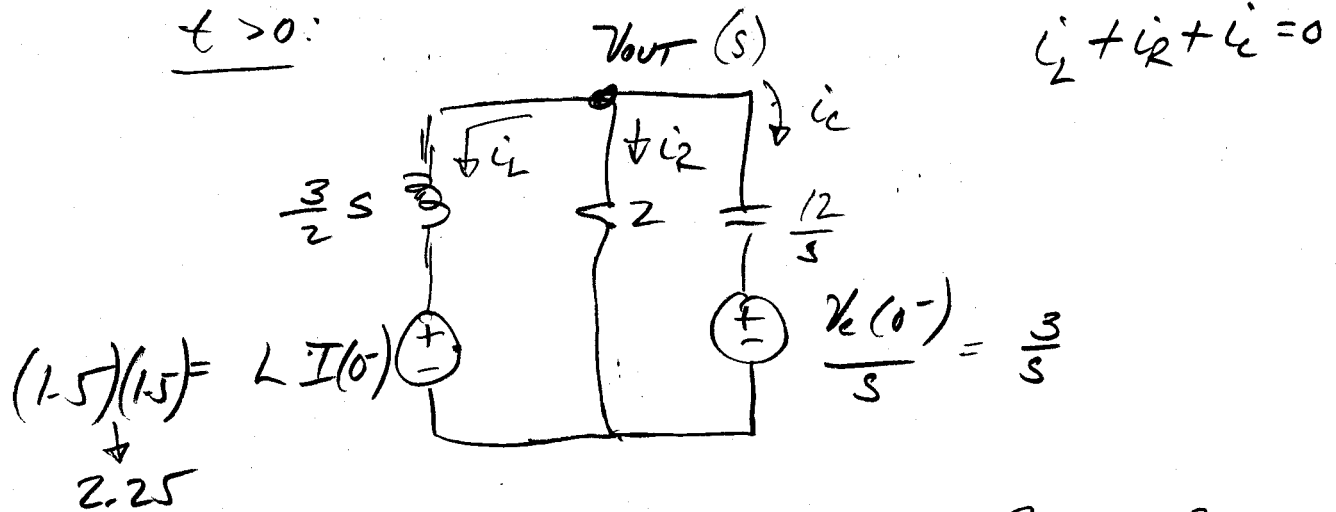

$$\frac{V_{out} - 2.25}{\frac{3}{2s}} + \frac{V_{out}}{2} + \frac{V_{out} - \frac{3}{s}}{\frac{12}{s}} = 0$$

$$V_o \left[\frac{2}{3s} + \frac{1}{2} + \frac{s}{12} \right] =$$

$$\left[\frac{4.5}{3s} + \frac{1}{4} \right] \rightarrow V_o =$$

$V_{out}(s)$	$\frac{3(s+6)}{s^2+6s+8} = \frac{3(s+6)}{(s+2)(s+4)}$
--------------	---

$$V_o = \frac{3(s+6)}{(s^2+6s+8)}$$

Problem 1 (cont)

Name Solutions

Section Number (please circle one)

1

2


3

MTR
10-12

MWR
4-6

MTR
2-4

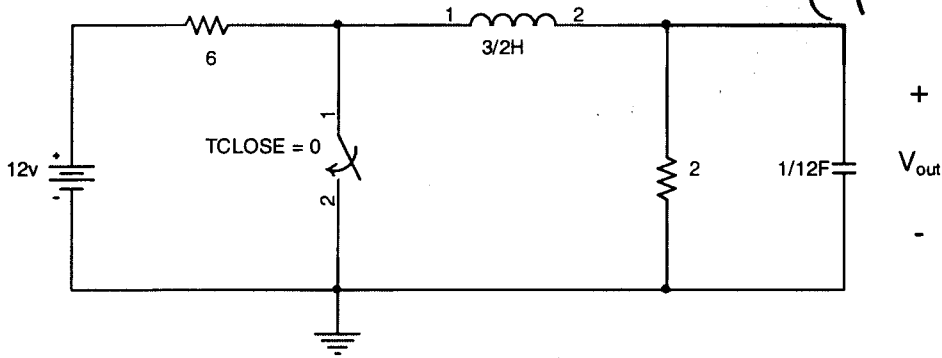c.) Find $V_{out}(t)$ for $t \geq 0$ (same circuit as in parts a & b). (6 pts)



$$\frac{3(s+6)}{s^2+6s+8} \rightarrow \frac{A}{(s+4)} + \frac{B}{(s+2)}$$

$$A = \frac{(s+4) 3(s+6)}{(s+4)(s+2)} \Big|_{s=-4} = \frac{3(-4+6)}{-4+2} = \frac{3 \cdot 2}{-2} = -3$$

$$B = \frac{(s+2) 3(s+6)}{(s+2)(s+4)} \Big|_{s=-2} = \frac{3(-2+6)}{-2+4} = \frac{12}{2} = 6$$

$V_{out}(t)$	$6e^{-2t} - 3e^{-4t}$
--------------	-----------------------


Problem 2 ~~XXXXXXXX~~

Name Solutions

Section Number (please circle one)

- | | | |
|----------|-----|-----|
| <u>1</u> | 2 | 3 |
| MTR | MWR | MTR |
| 10-12 | 4-6 | 2-4 |

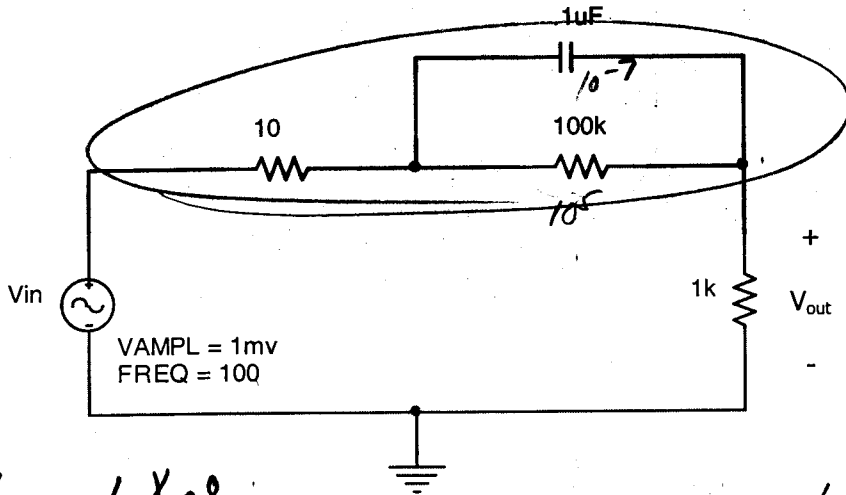a.) Find $V_{out}(t)$ in the circuit shown if $V_{in}(t) = 1\text{mV} \cos(200\pi t)$. (10pts)



$\approx -j16K$
~~almost all Capacitive!~~

$$V_{in} = 1 \angle 0^\circ$$

$$\omega = 200\pi \text{ rps}$$

$$Z_c = \frac{1}{j(200\pi) \cdot 1\mu F} = -j \frac{1}{628} \times 10^3$$

$$\approx -j16K$$

$$V_{out}(j\omega) = \frac{1K}{1K + 10 + (Z_c \parallel 100K)} V_{in}(j\omega)$$

$\approx -j16K$

$$V_{out}(j\omega) = \frac{1K}{1010 + (-j16K)} = \frac{1K \angle 0^\circ}{16K \angle 86.4^\circ} 1\text{mV}$$

$$V_{out} \approx 62.5 \mu V \angle 86.4^\circ$$

$V_{out}(t)$	$62.5 \mu V \cos(200\pi t + 86.4^\circ)$
--------------	--

$\rightarrow 0V$
 $\approx 0V!$


Problem 2 (cont)

Name Solutions - [Signature]

Section Number (please circle one)

- | | | |
|----------|----------|----------|
| 1 | 2 | 3 |
| MTR | MWR | MTR |
| 10-12 | 4-6 | 2-4 |

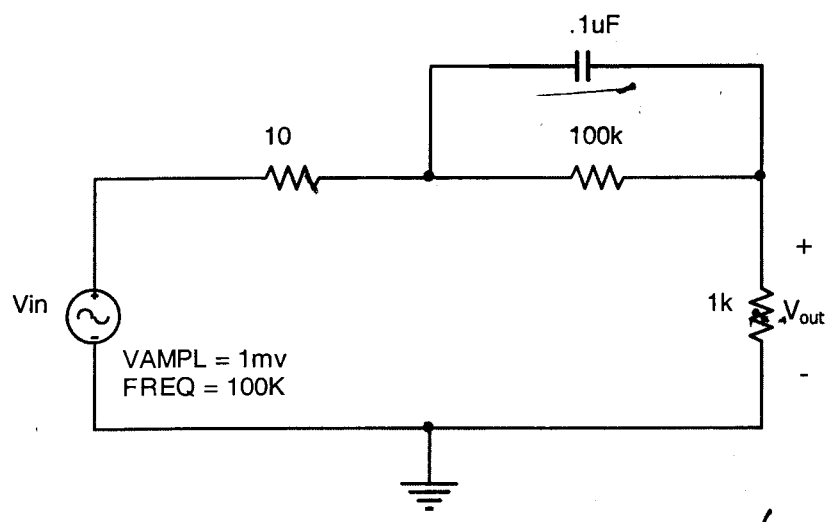b.) Find $V_{out}(t)$ in the circuit shown if $V_{in}(t) = 1mV \cos(200,000\pi t)$. (10pts)




$$Z_c(j200K\pi) = -j \frac{1}{\omega C} = -j \frac{1}{(200K\pi)(.1\mu F)} = \underline{-j16}$$

$$Z_p = (100K) \parallel (-j16) \approx -j16$$

$$V_{out} = \frac{1K}{1K + (10 - j16)} V_{in} = \frac{1K}{1010 - j16} V_{in}$$

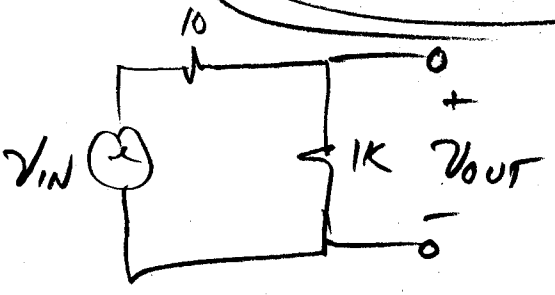$V_{out} \approx V_{in}$ (CAP \rightarrow short!)



$V_{out}(t)$	$1mV \cos(200K\pi t)$
--------------	-----------------------

$\approx V_{in}$!

Problem 3 (20pts)

Name

Solutions - *[Signature]*

Section Number (please circle one)

1

2

3

MTR

MWR



MTR

10-12

4-6

2-4

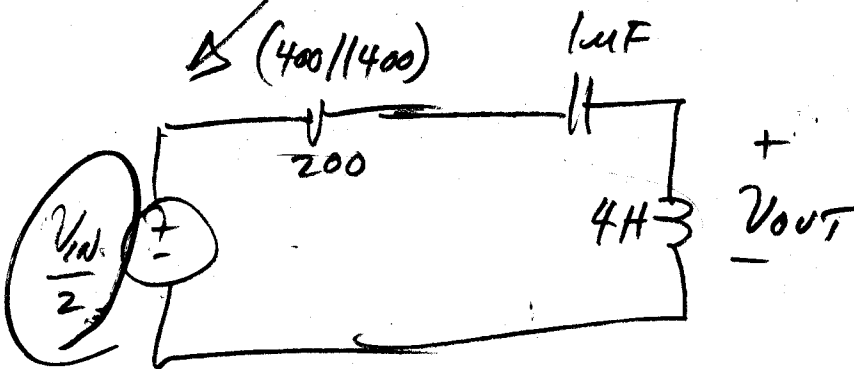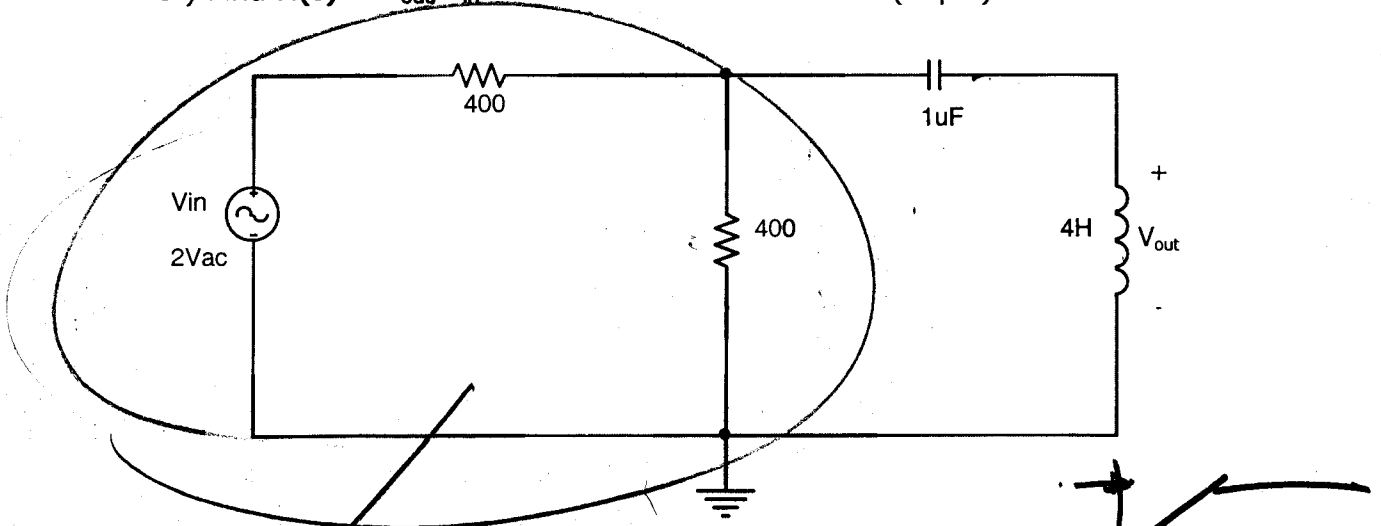a.) Find $H(s) = V_{out}/V_{in}$ for the circuit shown below. (10pts)



$$V_{out} = \frac{sL}{sL + R + \frac{1}{sC}} \left(\frac{V_{in}}{2} \right) = \frac{\frac{s}{2}}{\frac{s}{L}} \left[\frac{sL}{sL + R + \frac{1}{sC}} \right] \frac{V_{in}}{2}$$

$$V_{out} = \frac{\frac{1}{2} s^2}{s^2 + \frac{R}{L} s + \frac{1}{LC}} V_{in}$$

H(s)	$\frac{\frac{1}{2} s^2}{s^2 + 50s + (2.5 \times 10^5)}$
------	---

$$H(s) = \frac{\frac{1}{2} s^2}{s^2 + \left(\frac{R}{L}\right)s + \left(\frac{1}{LC}\right)} = \frac{\frac{1}{2} s^2}{s^2 + \frac{200}{4}s + \frac{1}{(4)(1\mu F)}}$$

$\frac{28 \mu s}{\text{---}}$ $\frac{2 \mu s^2}{\text{---}}$

Problem 3 (cont)

Name

Solutions - *[Signature]*

Section Number (please circle one)

1

2

3

MTR

MWR



MTR

10-12


4-6

2-4

b.) Sketch the asymptotic graphs of $|H(j\omega)|$ and $\Phi(j\omega)$ for the circuit shown. (10pts) (Please be sure to label and mark your axes as appropriate)

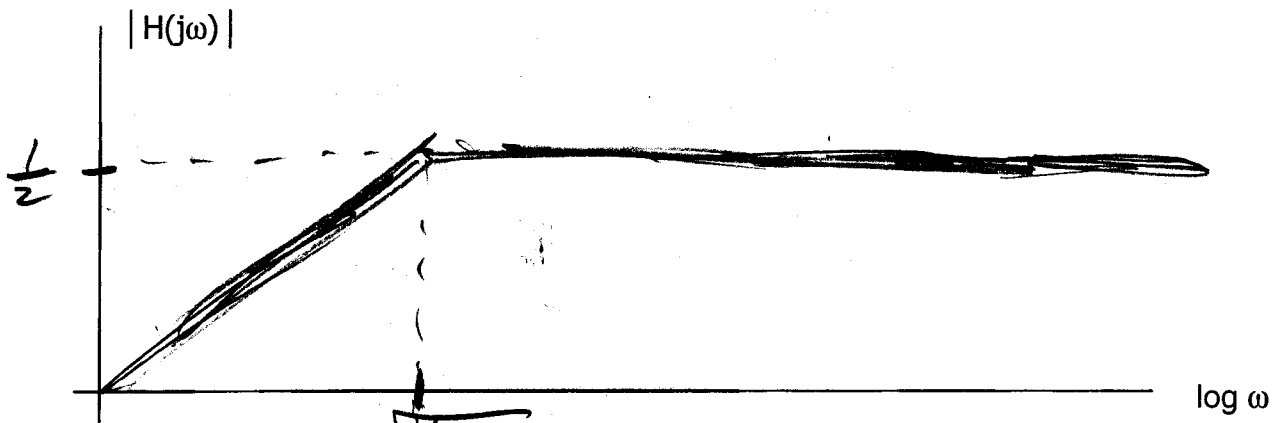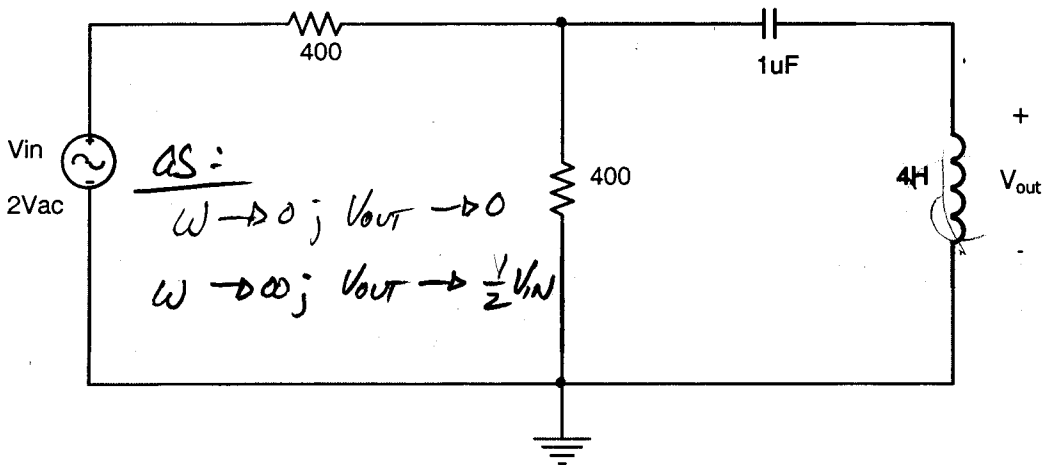
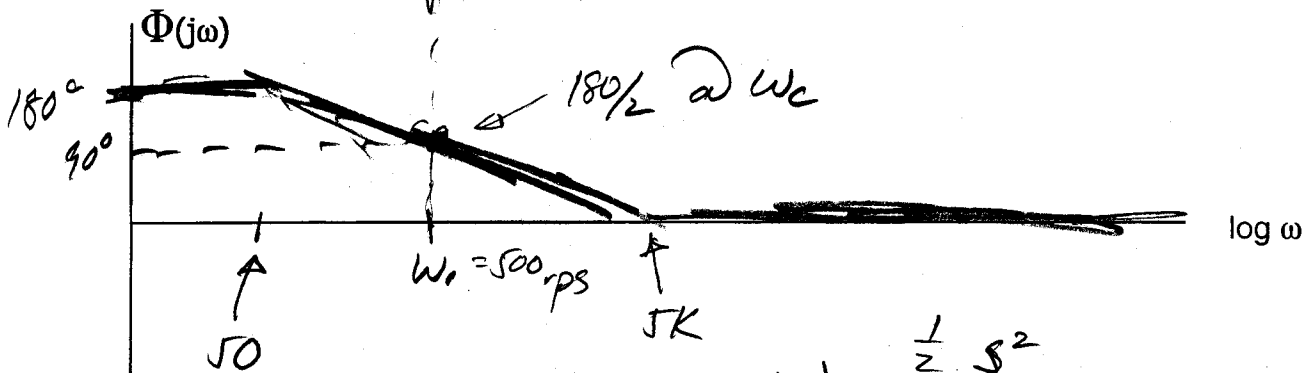
$$\omega_c = \sqrt{\frac{1}{LC}} = 500 \text{ ps}$$



$$H(s) = \frac{\frac{1}{2} s^2}{s^2 + 500s + (500)^2}$$

@ $\omega \rightarrow 0; \angle H \rightarrow 180^\circ$

$\omega \rightarrow \infty; \angle H \rightarrow 0^\circ$ ($\frac{1}{2}$)

Problem 4 (20pts)

Name

Solutions

Section Number (please circle one)

1

2


3

MTR
10-12

MWR
4-6

MTR
2-4

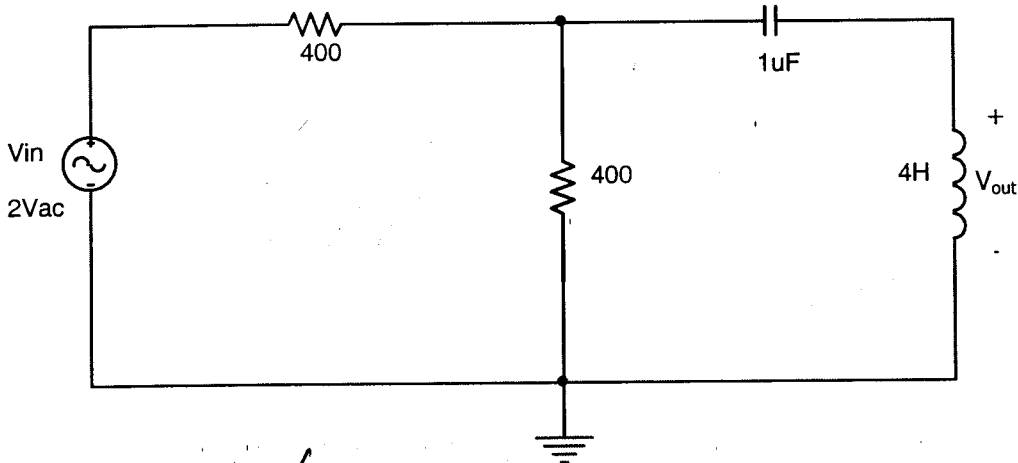a.) What frequency (ω_0) of V_{in} would cause the circuit shown below to resonate? (10pts) (Please justify your response)



$$\omega_0 = \frac{1}{\sqrt{LC}} = 500$$

ω_0	500
------------	-----

b.) What is the Q of the circuit shown above? (5pts)

$$Q = \frac{L}{2f} = \frac{\omega_0 L}{R_{eq}} = \frac{(500)(4)}{200}$$

(400 || 400)


Qseries

Q	10
---	----

c.) What is the magnitude $|V_{out}|$ of the circuit shown above at ω_0 ? (5pts)

$$|V_{out}| = Q \cdot \frac{|V_{in}|}{2} = 10 \left(\frac{2V}{2} \right)$$

$ V_{out} $	10V
-------------	-----

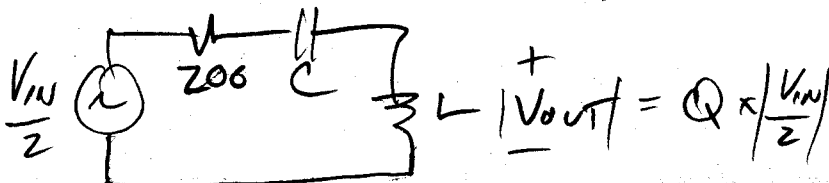


Problem 5 (20pts)

Name Solutions

Section Number (please circle one)

- | | | |
|----------|----------|----------|
| 1 | 2 | 3 |
| MTR | MWR | MTR |
| 10-12 | 4-6 | 2-4 |

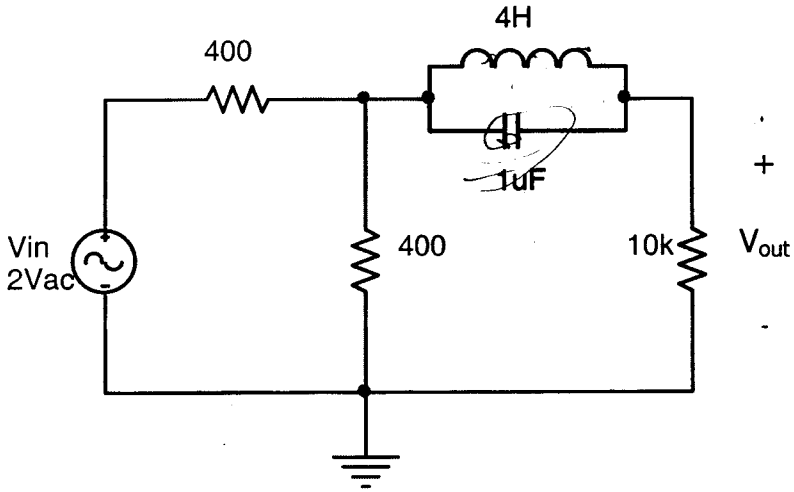a.) What kind of frequency response would the circuit shown have? (10pts)



(Please circle one and justify your response in the space provided below)

Bandpass filter	Lowpass filter	Highpass filter	Notch filter
-----------------	----------------	-----------------	---------------------

a) ω_0 :

resonance will occur between the L & C causing $Z_{eq} (Z_L || Z_C) \rightarrow \infty$.
Therefore, a) $\omega_0: V_{out} \rightarrow 0$

Problem 5 (cont)

Name Solutions - J

Section Number (please circle one)

1

2


3

MTR
10-12

MWR
4-6

MTR
2-4

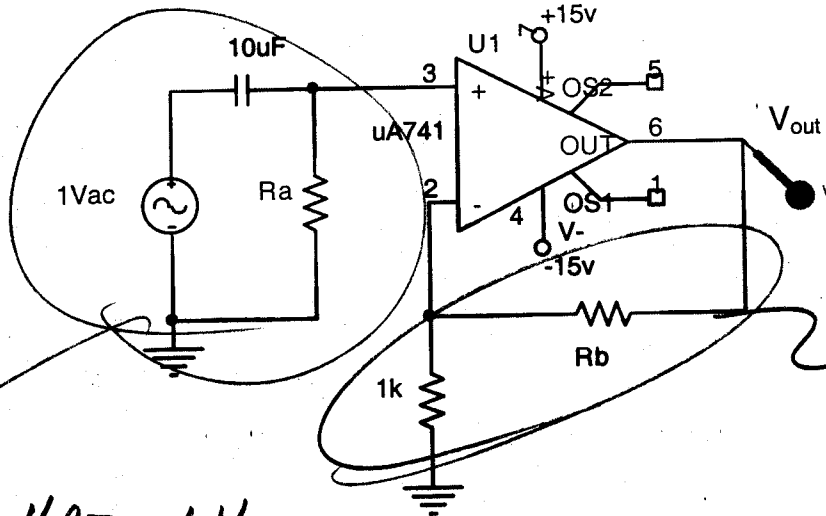b.) What values of **Ra** and **Rb** in the following circuit could produce the frequency plots shown on the following page? (10pts)



$$A_v = 1 + \frac{R_b}{1K}$$

HPF $\omega/\omega_c = 100 \text{ rps}$

$$A_{v_{MB}} \approx +6 \text{ dB} = 20 \log_{10} |A_{v_{MB}}| ; A_{v_{MB}} = 10^{(6/20)} \approx 2$$

$$R_b = (2 - 1) 1K = 1K$$

$$H(s) = \frac{R_a}{\frac{1}{sC} + R_a} = \frac{s}{s + \frac{1}{R_a C}}$$

\uparrow
 ω_c

$$\frac{1}{R_a(10\mu F)} = 100$$

$$R_a = \frac{1}{(100)(10\mu F)} = 1000 = 1K$$

Ra	1K
Rb	1K

Problem 5 (cont)

Name Solutions *[Signature]*

Section Number (please circle one)

1

2

3

MTR



MWR

MTR

10-12

4-6

2-4

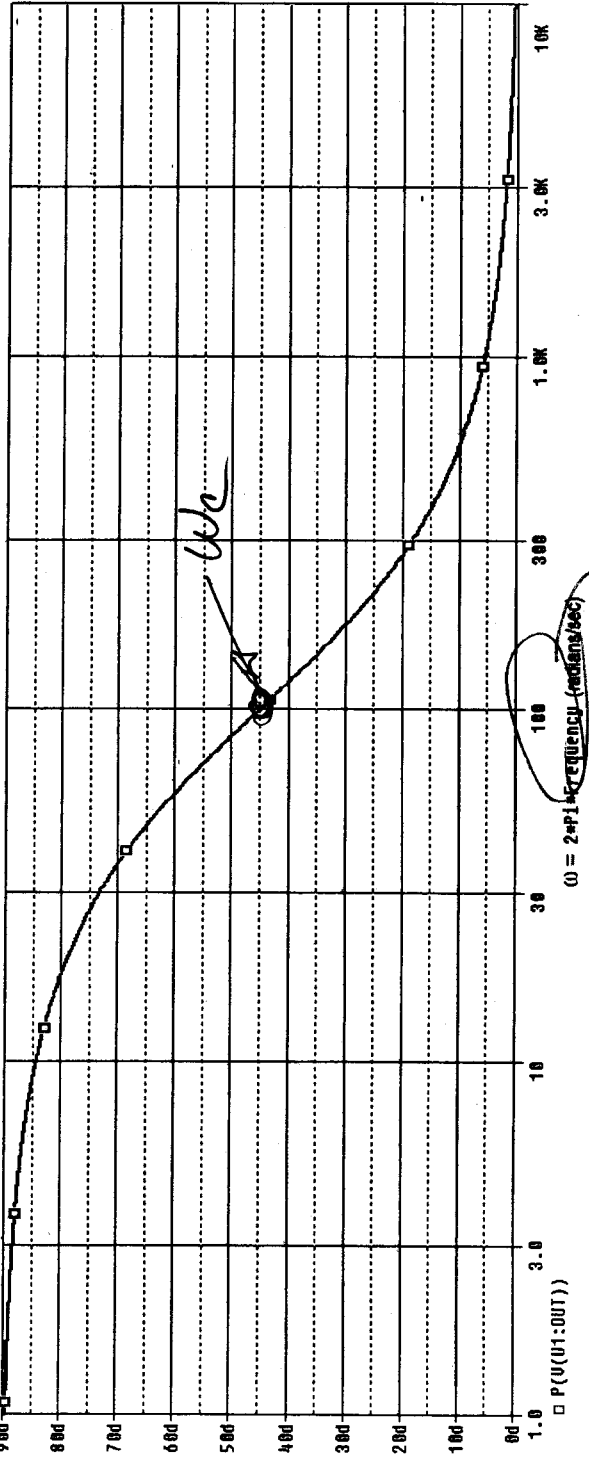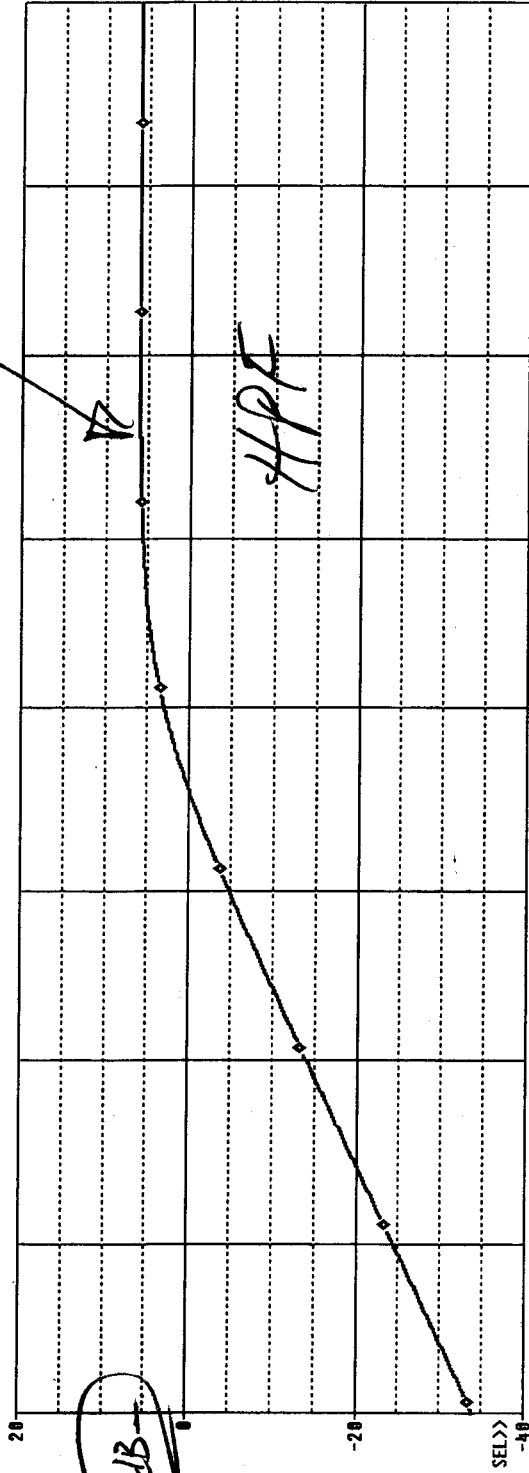

$\omega_c = 100 \text{ rps}$