

ECSE 2010
Electric Circuits
Final Exam
Fall 2005

Name _____

Section Number (please circle one)

1

MR
10-12
Kraft

2

MR
12-2
Millard

3

MR
4-6
Parsa


Please Note:

- Place all your answers in the spaces provided.
- You MUST show your work to receive any credit.
- Assume all resistances are in ohms, if not otherwise indicated.

Problem No.	Pts.	Score
1	20pts	
2	20pts	
3	20pts	
4	30pts	
5	20pts	
6	20pts	
7	20pts	
Total	150pts	

Problem 1 (20pts)


a) Find $|V_{out}|$ in the circuit shown. (10pts)

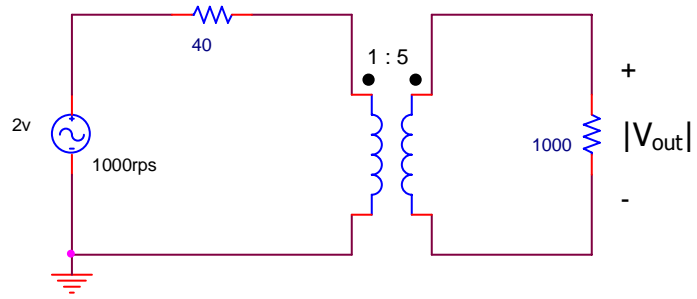

$ V_{out} $	
-------------	--

Problem 1 (cont)

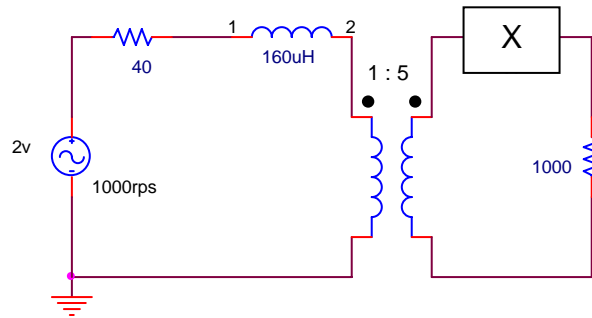
- b) Find a component X (both the component type and value) that would maximize the power delivered to the 1000 ohm resistor in the circuit shown. (10pts)



X-type	
Value	

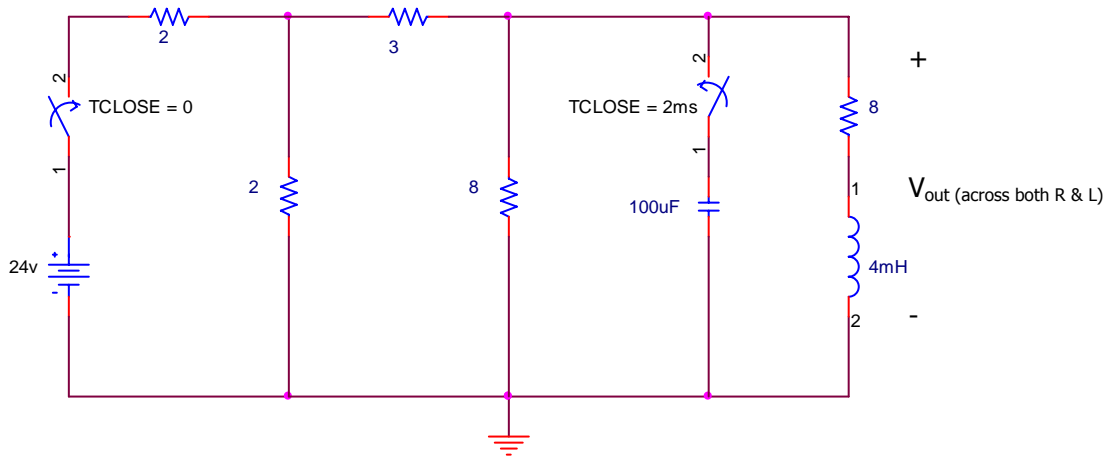
Problem 2 (20pts)

a.) Draw the circuit in the s-domain for $t \geq 2\text{ms}$. (5pts)



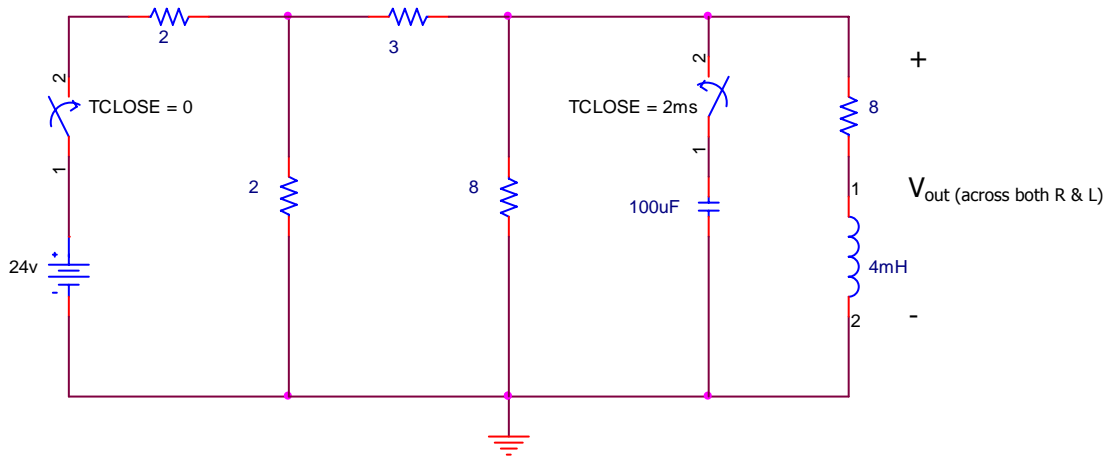Problem 2 (cont)

b.) Find $V_{out}(s)$ in the circuit shown for $t > 2\text{ms}$. (5pts)



$V_{out}(s)$	
--------------	--

Problem 2 (cont)

c.) Find $V_{\text{out}}(t)$ for $0 \leq t < 2\text{ms}$ (using the circuit shown in parts a & b). (5pts)

$V_{\text{out}}(t < 2\text{ms})$	
----------------------------------	--

d.) Sketch $V_{\text{out}}(t)$ for $t \geq 0$ (using the circuit shown in parts a & b). Show all pertinent points in time, including the appropriate time constants and voltage values (5pts)



Problem 3 (20pts)

The following three loads are connected across a $120V_{\text{rms}}$ 60Hz AC generator:

Load #1 has 800 VA and has a $\text{pf}_1 = .707$ **lagging**

Load #2 has 250 Watts and has a $\text{pf}_1 = .5$ **lagging**

Load #3 has -420 VARS and has a $\text{pf}_1 = 0$ **leading**

a) Determine the total apparent power of the three loads. (5pts)

$$|S|_{\text{total}} =$$

b) Determine the power factor of the combined loads. (5pts)

$$\text{pf}_{\text{combination}} =$$

Problem 3 (cont)

c) Determine the capacitance that will be necessary in order to make the overall $\text{pf} = 1.0$, assuming that the voltage across the load is to be kept at $120V_{\text{rms}}$. (5pts)


C =

d) Determine the difference in the current drawn from the generator (e.g the difference in the current drawn with and without power factor correction). (5pts)

I difference (I non-corrected - I corrected)	
---	--

Problem 4 (30pts)

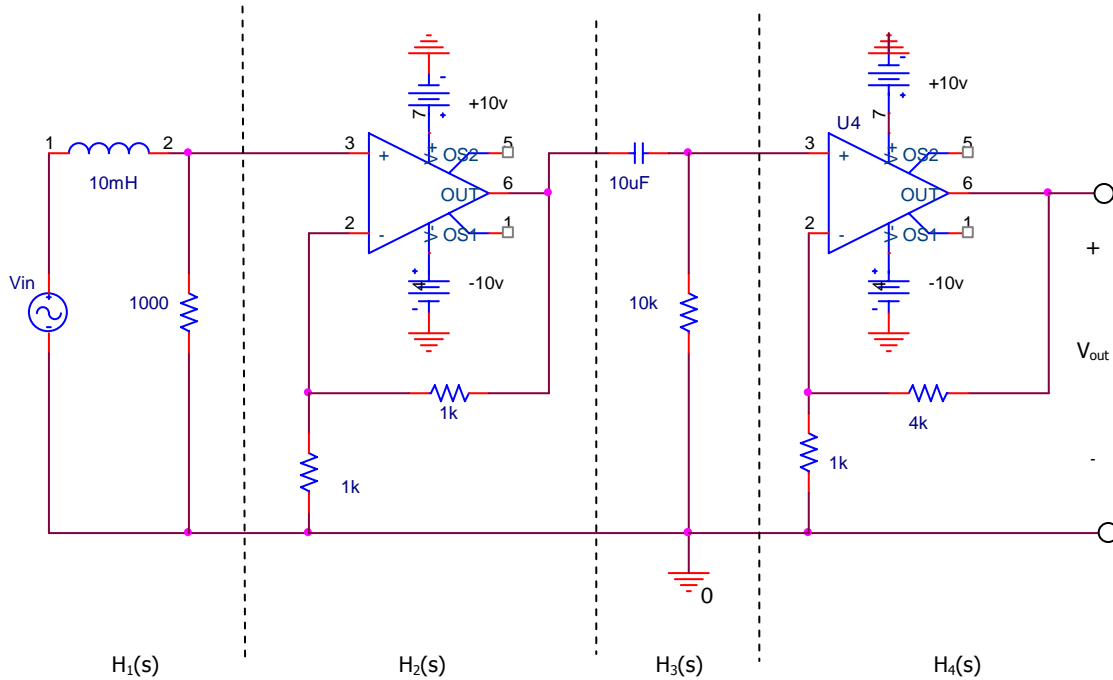a) Find $H_1(s)$, $H_2(s)$, $H_3(s)$, $H_4(s)$, and the overall transfer function $V_{out}/V_{in} = H(s) = H_1(s)H_2(s)H_3(s)H_4(s)$ for the circuit shown below. (10pts)



$H_1(s)$	
$H_2(s)$	
$H_3(s)$	
$H_4(s)$	
$H(s)$	

Problem 4 (cont)

b) Sketch the asymptotic graphs of $|H(j\omega)|_{db} = |V_{out}/V_{in}|$ and $\angle H(j\omega)$ for the circuit shown in part a on the previous page. Please clearly label your axes as appropriate. (10pts)



Problem 4 (cont)

c) It is desired to have an output sinusoid with an amplitude of 5v ($|V_{out}|=5v$) for an input $V_{in}(t)=A\cos(1k_{rps}t)$ volts (for the circuit shown in part a). What must the value of **A** be? (5pts)


A	
----------	--

d) What frequency (ω) will change an input that is $= 1\cos(\omega t)$ into an output $= 7.07\cos(\omega t+90)$ (using the circuit shown in part a)? Explain and justify your response. (5pts)

ω	
----------	--

Problem 5 (20pts)

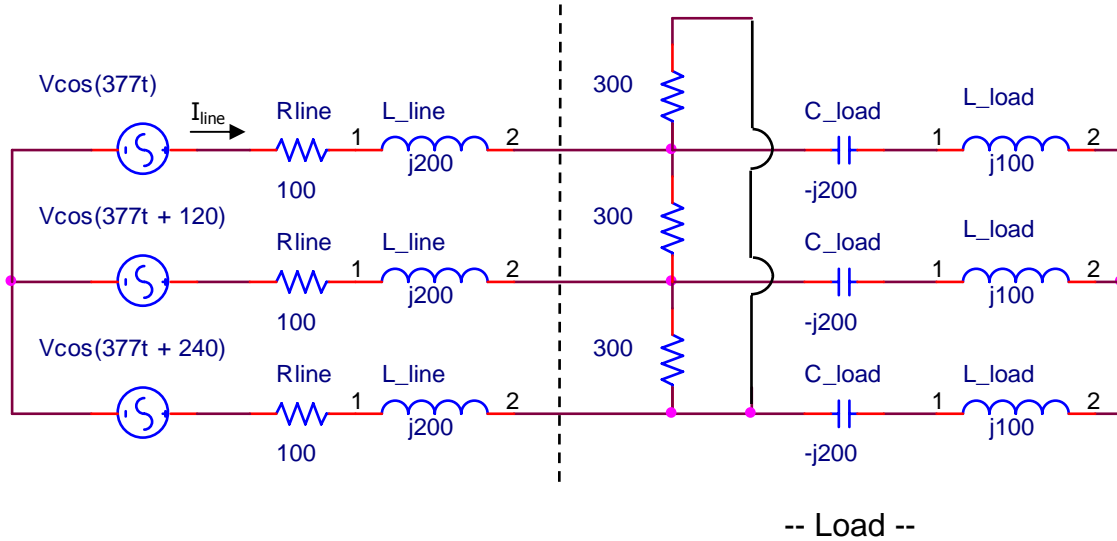a) Given the following 3 phase circuit, what is the equivalent single phase load impedance to the right of the dashed line? (5pts) (Please justify your response)




Z_{load}	
------------	--

b) What is the line current I_{line} (in rms) flowing in each line resistance (R_{line}) associated with the three phases if each of the phase voltages is $V_{\phi} = 15kV_{rms}$? (5pts)

I_{line}	
------------	--

Problem 5 (cont)

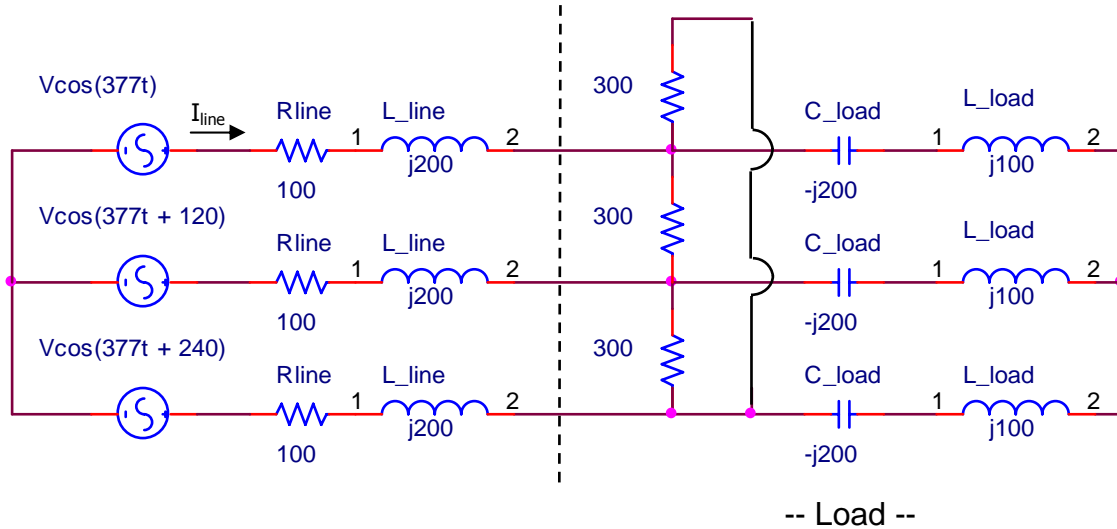c) What is the total average real power (in rms) dissipated by the three phases' line resistances (R_{line}) if each of the phase voltages is $V_{\phi} = 15kV_{rms}$? (5pts)





P_{line}	
------------	--

d) What is the efficiency of the transmission system, defined as: $P_{load-average}/P_{total} * 100\%$? (5pts)

Efficiency	
------------	--

Problem 6 (20pts)

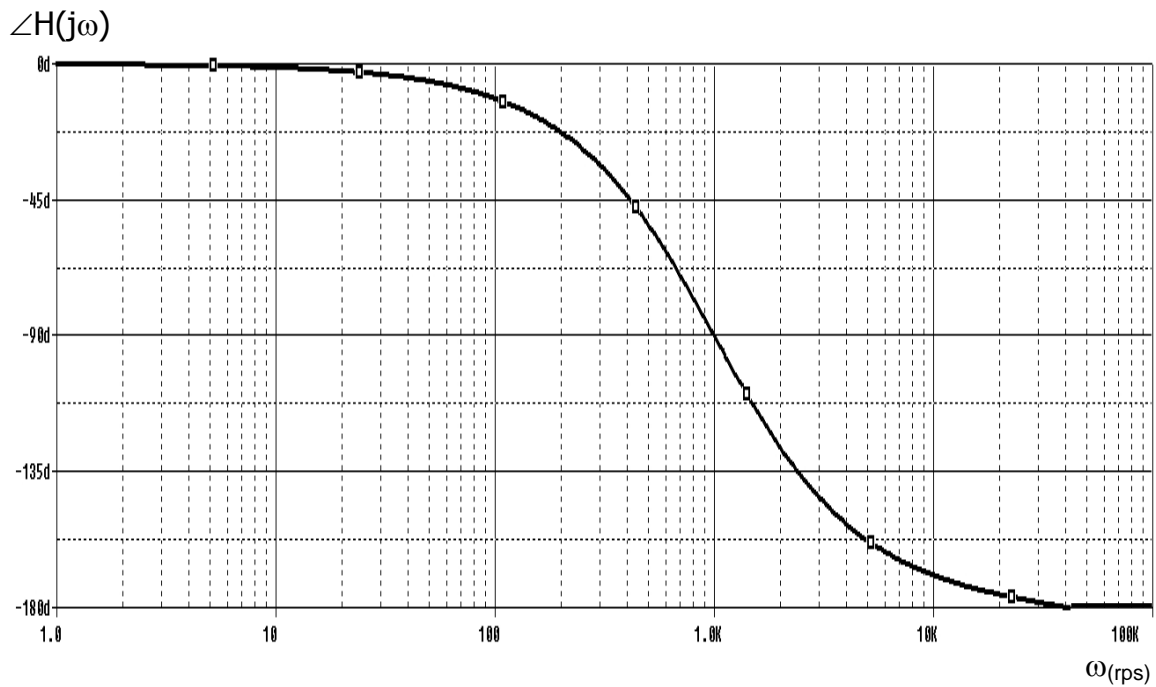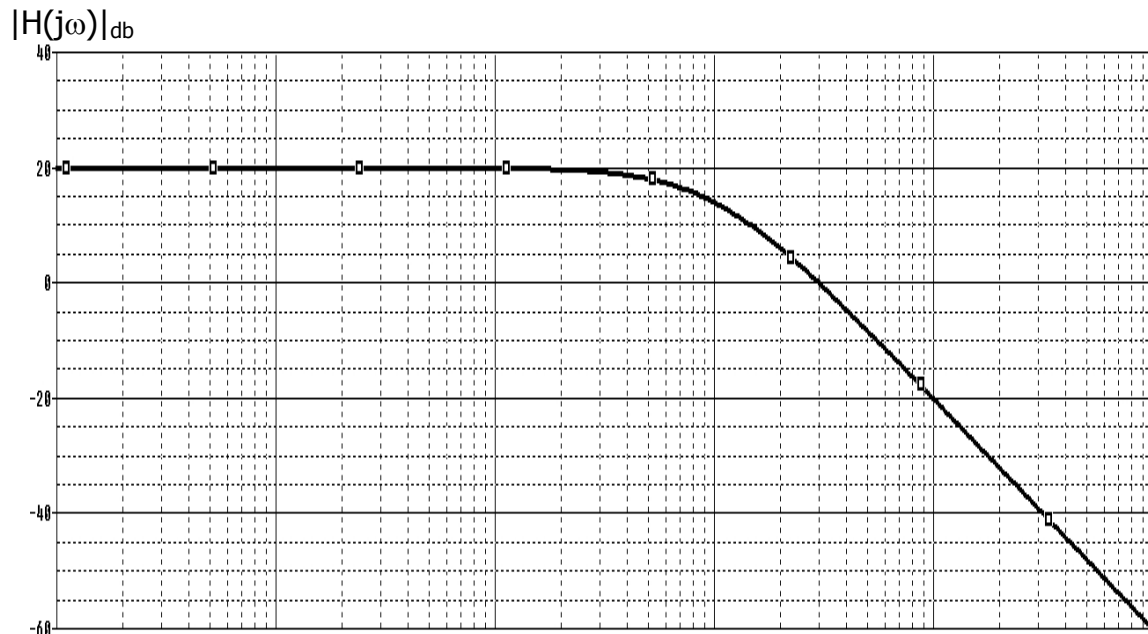- a) Given the plots below, find the cutoff frequency ω_{co} of the circuit that would produce the response shown. (5pts)




$\omega_{co} =$

Problem 6 (cont)

b) Design a circuit that would produce the Bode Plot given in part (a). Assume that you only have **one** capacitor, **one** inductor, **six** resistors and **two** op-amps available. Please provide values for your component choices and show your circuit schematic. Please specify and provide support for your component choices and circuit topology. (15pts)

Problem 7 (20pts)

a) Find $|V_{out}|$ for the circuit shown as a function of the gain (G) with $|V_{in}| = 10v$. Please note: the two circuits below are identical. (5pts)

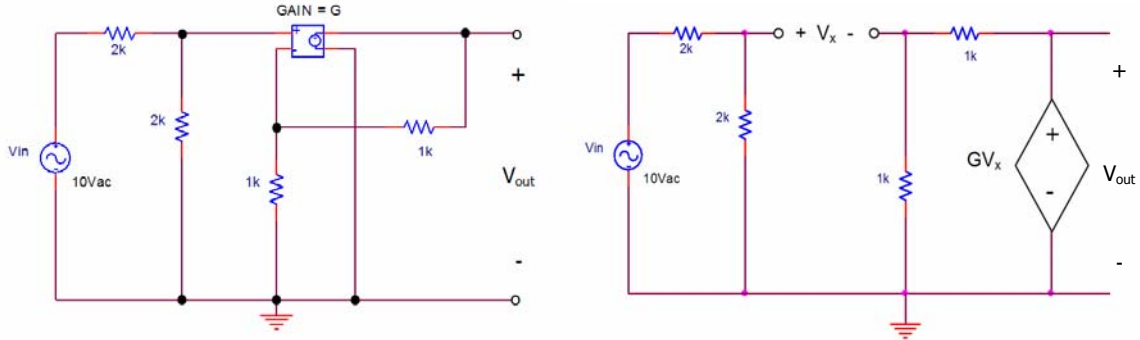


$ V_{out} $	
-------------	--

b) Find $V_{out}(t)$ in the circuit shown above if the gain $G=100,000$ and $V_{in}(t) = 10\cos(1000t + 30)$. (5pts)

$V_{out}(t)$	
--------------	--

Problem 7 (cont)

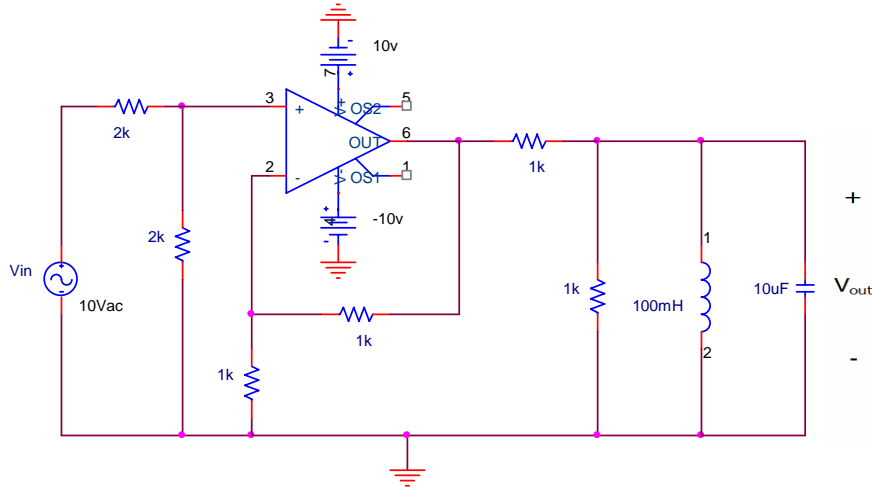c) Find $H(s) = V_{out}/V_{in}$ for the circuit shown below. Consider how your result could relate to that from part (b). (5pts)



$H(s) = V_{out}/V_{in}$	
-------------------------	--

d) Find V_{out} if $V_{in} = 10\cos(1000t)$ for the circuit shown above if the gain $G=100,000$. (5pts)

$V_{out}(t)$	
--------------	--

Extra space (if needed)

Name _____

Extra space (if needed)

Name _____

Laplace Transform Theorems

- | | |
|-----------------------------|--|
| 1. Definition | $L[f(t)] = F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt$ |
| 2. Linearity | $L[k_1 f(t_1) + k_2 f(t_2)] = k_1 F_1(s) + k_2 F_2(s)$ |
| 3. Time shift | $L[f(t - \tau)] = e^{-\tau s} F(s)$ |
| 4. Frequency Shift | $L[e^{-at} f(t)] = F(s + a)$ |
| 5. Scaling Theorem | $L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$ |
| 6. Differentiation Theorem | $L\left[\frac{df}{dt}\right] = sF(s) - f(0)$ |
| 7. Differentiation Theorem | $L\left[\frac{d^2 f}{dt^2}\right] = s^2 F(s) - sf(0) - \dot{f}(0)$ |
| 8. Differentiation Theorem | $L\left[\frac{d^n f}{dt^n}\right] = s^n F(s) - \sum_{k=1}^n s^{n-k} f^{(k-1)}(0)$ |
| 9. Integration Theorem | $L\left[\int f(\tau) d\tau\right] = \frac{F(s)}{s} + \frac{\int_{0^+} f(\tau) d\tau}{s}$ |
| 10. Final value theorem* | $f(\infty) = \lim_{s \rightarrow 0} sF(s)$ |
| 11. Initial value theorem** | $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$ |

* Provided all poles of $F(s)$ have negative real parts with the exception of possibly one pole at the origin.

** Provided $f(t)$ is continuous or has a step discontinuity at $t = 0$.

Laplace Transform of Time Functions

1.	$\delta(t)$	1
2.	$u(t)$	$1/s$
3.	$tu(t)$	$1/s^2$
4.	$\frac{1}{2!}t^2u(t)$	$1/s^3$
5.	$\frac{1}{(m-1)!}t^{m-1}u(t)$	$1/(s^m)$
6.	$e^{-at}u(t)$	$1/(s+a)$
7.	$te^{-at}u(t)$	$1/(s+a)^2$
8.	$\frac{1}{(m-1)!}t^{m-1}e^{-at}u(t)$	$1/(s+a)^m$
9.	$(1 - e^{-at})u(t)$	$a/[s(s+a)]$
10.	$\frac{1}{a}(at - 1 + e^{-at})u(t)$	$a/[s^2(s+a)]$
11.	$(1 - at)e^{-at}u(t)$	$s/(s+a)^2$
12.	$\sin(\omega t)u(t)$	$\omega/(s^2 + \omega^2)$
13.	$\cos(\omega t)u(t)$	$s/(s^2 + \omega^2)$
14.	$e^{-at} \cos(\omega t)u(t)$	$(s+a)/[(s+a)^2 + \omega^2]$
15.	$e^{-at} \sin(\omega t)u(t)$	$\omega/[(s+a)^2 + \omega^2]$
16.	$\left\{ 1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} [\sin(\omega_d t + \theta)] \right\} u(t)$	
	$\omega_d = \omega_n \sqrt{1-\zeta^2}; \quad \theta = \cos^{-1}(\zeta)$	
OR	$\left\{ 1 - e^{-\zeta\omega_n t} \left[\cos(\omega_d t) + \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_d t) \right] \right\}$	$\frac{\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$

Laplace Transform of Time Functions (cont)

$$F(s) = \frac{Bs + C}{s^2 + 2\alpha s + \omega_0^2}$$

$$L^{-1}[F(s)] = f(t)$$

17.

$$f(t) = Ae^{-\alpha t} \cos(\omega_d t + \phi), \text{ where}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \phi = \tan^{-1}\left(\frac{\alpha B - C}{\omega_d B}\right) \text{ and}$$

$$A = \sqrt{B^2 + \left(\frac{\alpha B - C}{\omega_d}\right)^2} = \frac{\sqrt{B^2 \omega_0^2 - 2\alpha BC + C^2}}{\omega_d}$$