

ECSE 2010
Electric Circuits
Exam 1
Spring 2006

Name

SOLUTIONS ~~ET~~

Section (please circle one)

MR
10-12
Millard

MR
2-4
Salama

MR
4-6
Kraft

Problem No.	Pts.	Score
1	20pts	X/re
2	20pts	X/re
3	20pts	X/20
4	20pts	X/20
5	20pts	X/20
Total	100pts	X/100





~~Handwritten notes:~~
Kraft
Rajish
He

Please Note:

- * Place all your answers in the spaces provided.
- * You MUST show your work to receive any credit.

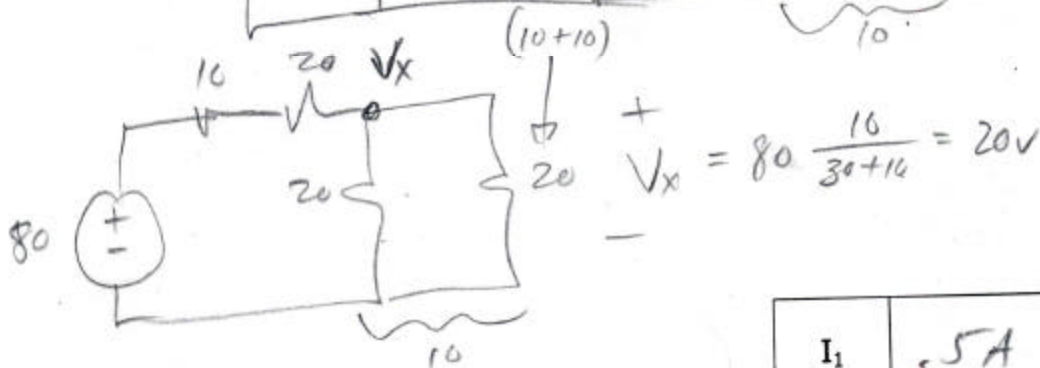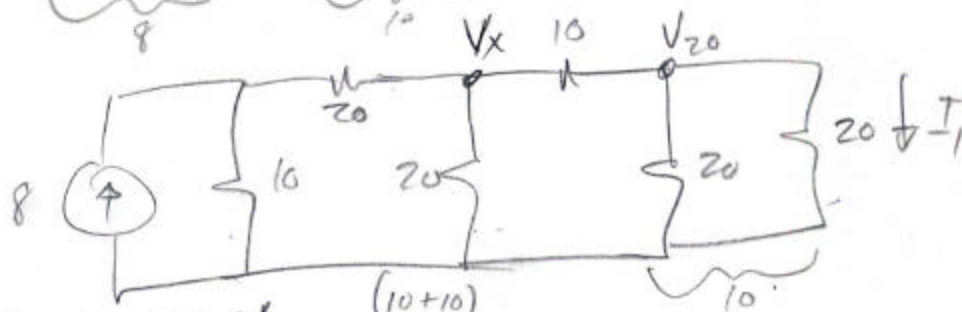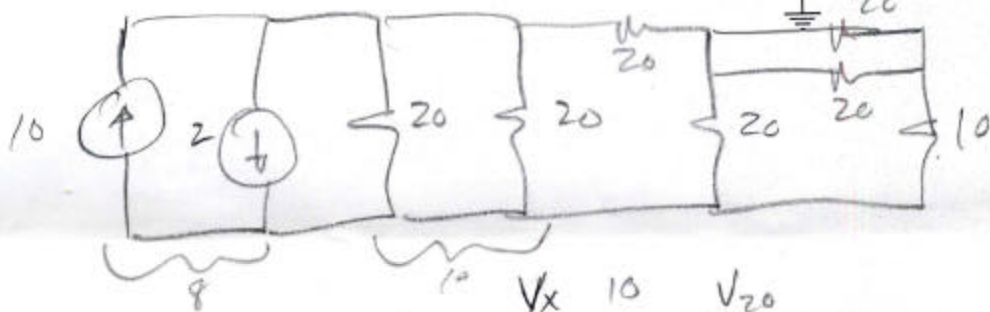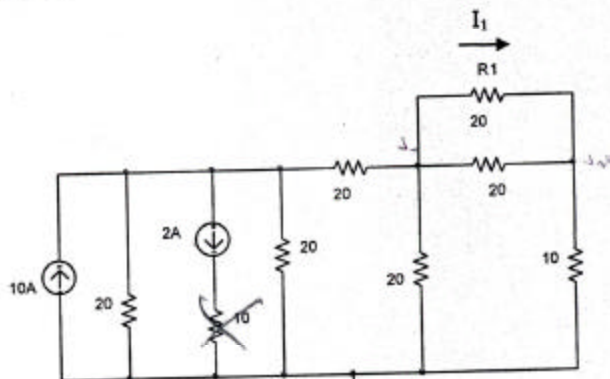Problem 1 (20pts)

a.) Find I_1 in the circuit shown. (10pts)



$$V_x = 80 \frac{10}{30+10} = 20V$$

I_1	$.5A$
-------	-------


$$V_{20} = \frac{1}{2} V_x = 10V$$

$$I_1 = \frac{V_{20}}{20} = \frac{10V}{20} = .5A$$

10pts
 ↓
 (5pts reduction)
 (5pts solving)

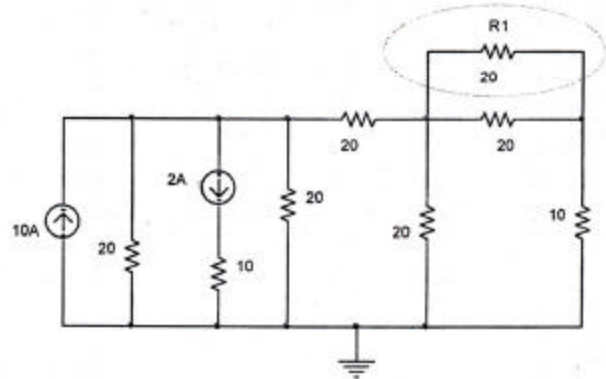Problem 1 (cont)

b.) Find the power absorbed by R_1 for in the circuit shown. (10pts)



$$V_{R_1} = V_{20} \text{ (from prior page)}$$

5pts

$$V_{R_1} = 10V$$

$$P_{R_1} = I_{R_1} \times V_{R_1} = -.5A \times 10V = 5W$$

OR

5pts



$$P_{R_1} = I_{R_1}^2 \times R = (.5)^2 \times 20$$

P_{R_1}	5W
-----------	----

10pts

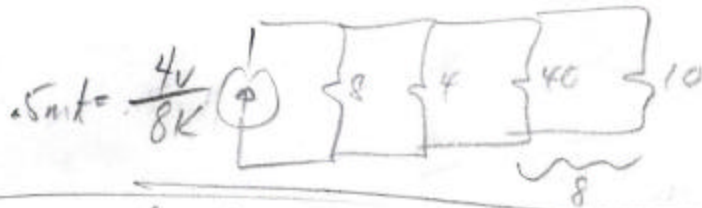
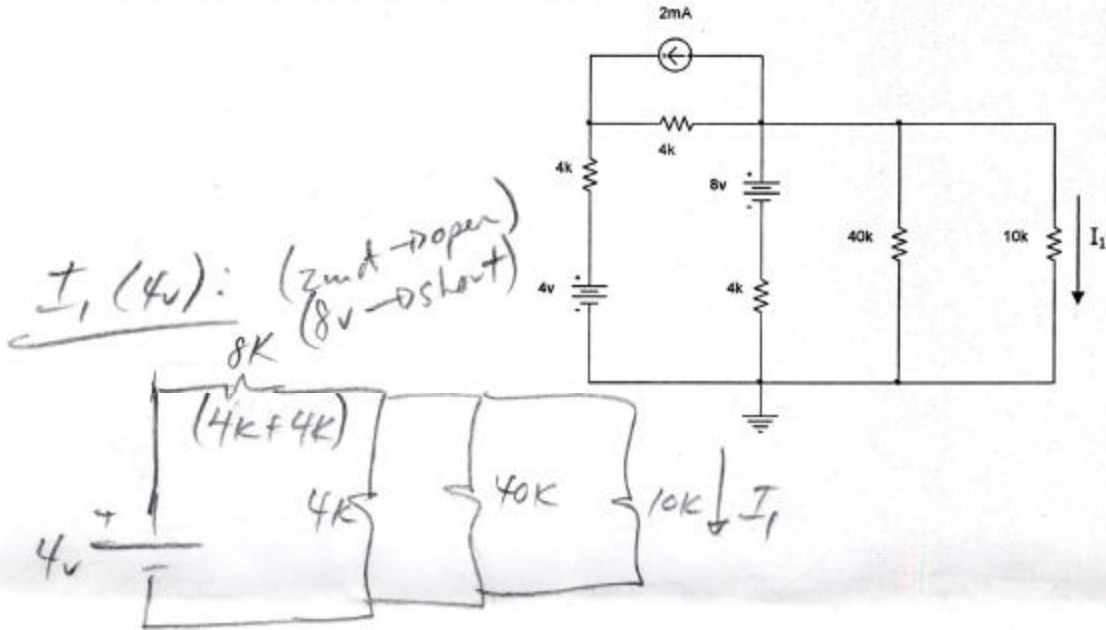
Problem 2 (20pts)

a.) Find I_1 (flowing through the 10k resistor) due to each of the sources using superposition for the circuit shown. (15pts)



$$V = .5 \times 2 = 1.0V$$

$$I_{14V} = \frac{1V}{10K} = 100 \mu A$$

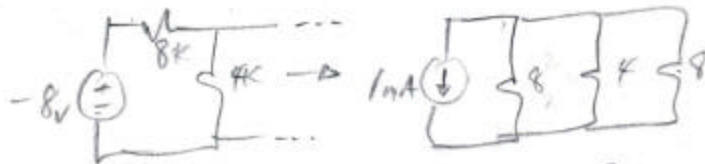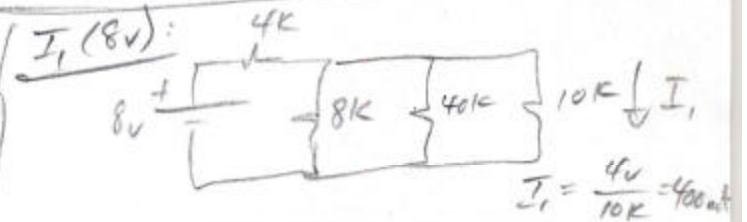


$$I_1 = \frac{-2V}{10K} = -200 \mu A$$

$I_1 (4V)$	100 μA	5pts
$I_1 (2mA)$	-200 μA	5pts
$I_1 (8V)$	400 μA	5pts

$$I_{TOT} = 300 \mu A$$

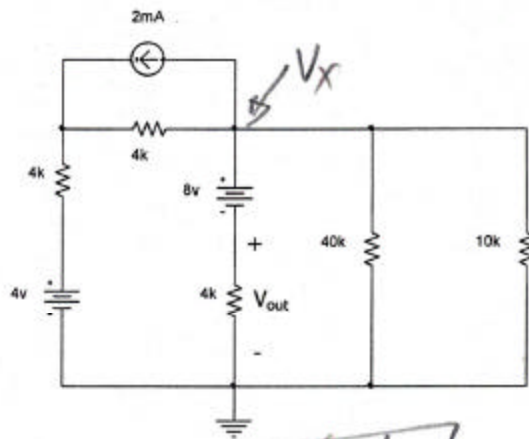Problem 2 (cont)

b.) Find V_{out} across the designated 4k resistor in the circuit shown. (5pts)




$$V_{out} = V_x - 8V \quad \text{[from part A]}$$
$$V_x = I_{10K} \times 10K = 300\mu A \times 10K = 3V \quad (3pts)$$
$$V_x = 3V - 8V = -5V \quad (2pts)$$


V_{out}	$-5V$	5pts
-----------	-------	------

Problem 4 (20pts)

Given the following circuit:

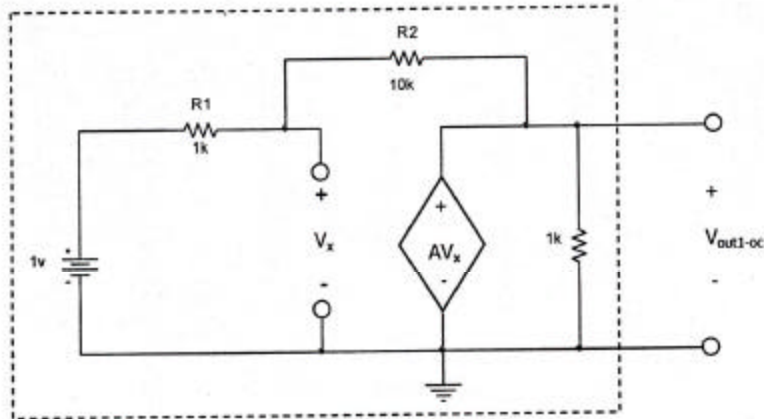

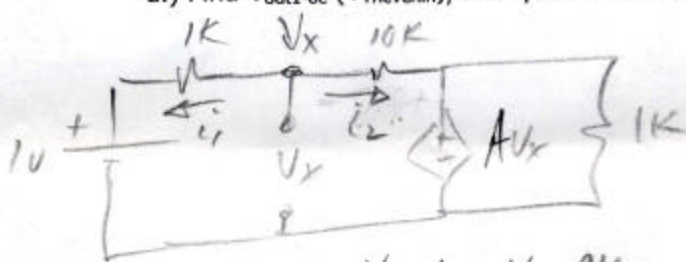a.) Find $V_{out1-oc}$ ($V_{Thevenin}$), the open circuit output voltage if $A=9$. (5pts)



$$10V_x - 10 + V_x - 9V_x = 0$$

$$2V_x = 10$$

$$V_x = 5V$$


$$V_{TH} = 9V_x = 45V$$

$$i_1 + i_2 = 0 \Rightarrow \frac{V_x - 1}{1K} + \frac{V_x - AV_x}{10K} = 0$$

$$10(V_x - 1) + V_x - AV_x = 0$$

V_{TH}	45V	(5pts)
----------	-----	--------

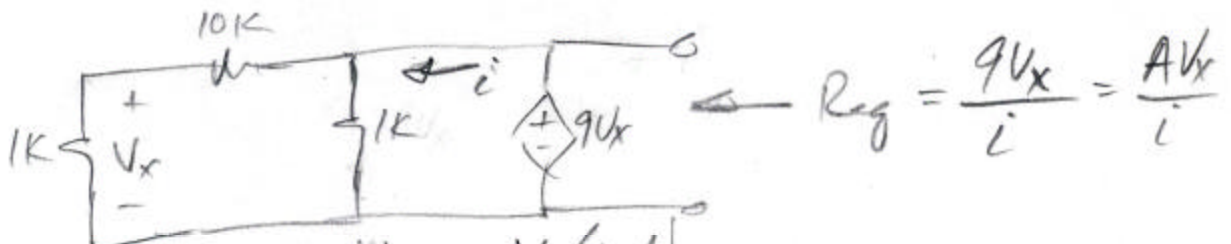b.) Find the equivalent resistance ($R_{Thevenin}$) that a multimeter would read across the two wires that exit the box if $A=9$. (5pts)




$$R_{eq} = \frac{9V_x}{i} = \frac{AV_x}{i}$$

$$i = \frac{AV_x}{1K} + \frac{V_x}{1K} = \frac{V_x(1+A)}{1K}$$

R_{TH}	900	(5pts)
----------	-----	--------

$$R_{eq} = \frac{AV_x}{V_x(1+A)} \times 1K = \frac{9}{10} \times 1000 = 900$$

Problem 4 (cont)

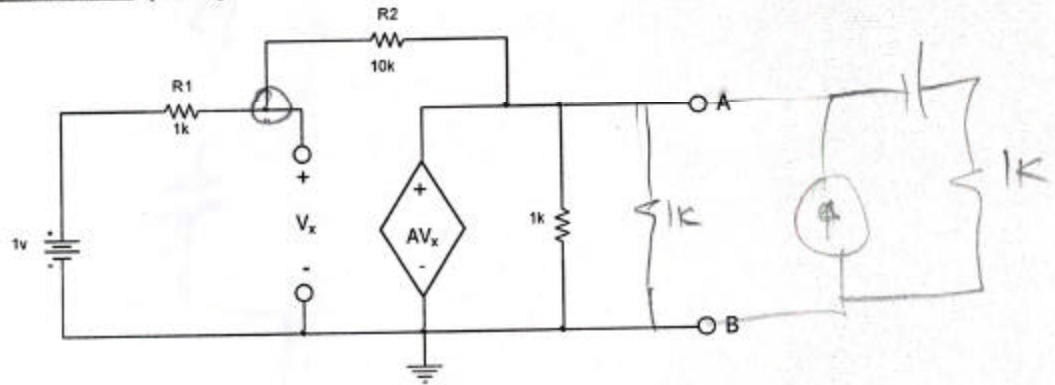

c.) Find V_{out2} if the following load network is connected to the output of the above circuit and $A=100,000$. (10pts)

@ V_x :

$$\frac{1V - V_x}{1k} = \frac{V_x - AV_x}{10k}$$

$$10(1 - V_x) = V_x - AV_x$$


$$10 - 10V_x = V_x - AV_x + 10V_x$$

$$11V_x - AV_x = 10$$

$$V_x(11 - A) = 10$$

$$V_x = \frac{10}{(11 - A)}$$
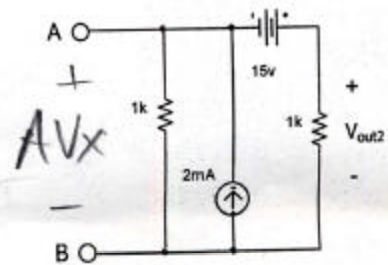
$$AV_x = \frac{10}{(11 - A)} \times A = \frac{10 \cdot 10^5}{11 - 10^5} \approx \underline{\underline{-10}} \text{ (8pts)}$$



$$V_{out} = AV_x + 15V$$


$$V_{out} = -10 + 15V$$

$$V_{out} = +5V \text{ (2pts)}$$

V_{out2}	$+5V$
------------	-------

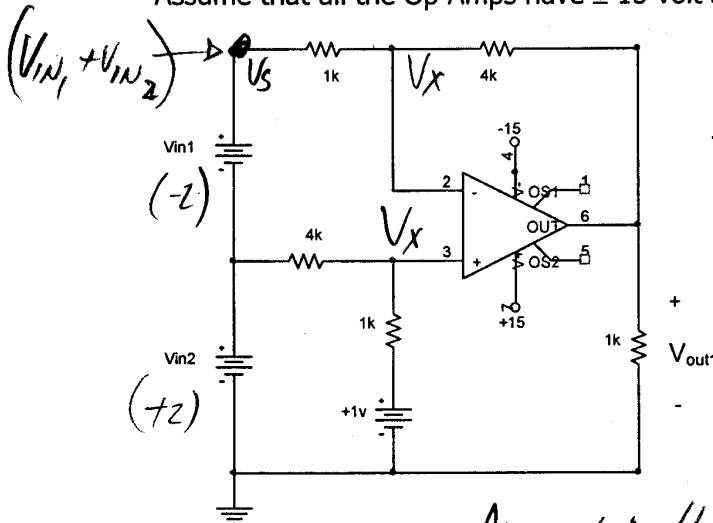Problem 5 (20pts)

Assume that all the Op Amps have ± 15 volt supplies for the following circuits.



a) V_x

$$\frac{V_{in2} - V_x}{4k} = \frac{V_x - 1V}{1k}$$

$$V_{in2} - V_x = 4V_x - 4$$

$$5V_x = V_{in2} + 4$$

$$V_x = \frac{V_{in2} + 4}{5} \quad (4pts)$$

negative feedback $(+ -)$

a.) Find V_{out1} in terms of V_{in1} and V_{in2} (shown the above circuit). (10pts)

a) V_x (on top)

$$\frac{(V_{in1} + V_{in2}) - V_x}{1k} = \frac{V_x - V_{out1}}{4k} \quad (4pts)$$

$$4(V_{in1} + V_{in2}) - 4V_x = V_x - V_{out1}$$

$$V_{out1} = V_x + 4V_x - 4(V_{in1} + V_{in2})$$

$$V_{out1} = 5V_x - 4(V_{in1} + V_{in2})$$


$$V_{out1} = 5\left(\frac{V_{in2} + 4}{5}\right) - 4(V_{in1} + V_{in2})$$

$$= -3V_{in2} - 4V_{in1} + 4 \quad (2pts)$$

V_{out1}	$-3V_{in2} - 4V_{in1} + 4$
------------	----------------------------

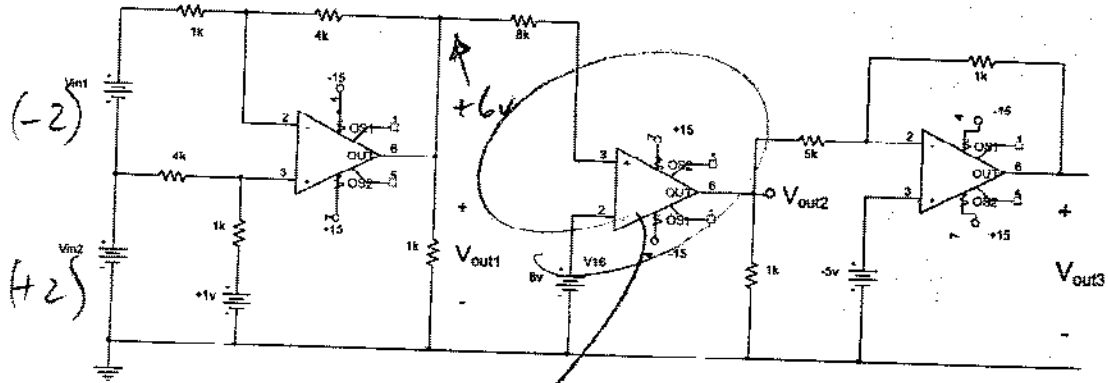Problem 5 (cont)

b.) Find the expression relating V_{out2} to V_{out1} . (5pts)



no neg. feedback! (3pts)

$$V_{out2} = (+\infty) \times V_B = (+\infty) \times (V_+ - V_-)$$

$$= (+\infty) \times (6 - 8) = (+\infty) \times (-2V)$$

$$\rightarrow -\infty \rightarrow -V_{cc}$$

V_{out2}	$-15V$	(2pts)
------------	--------	--------

c.) Find V_{out3} if $V_{in1} = -2V$ and $V_{in2} = +2V$ (using the circuit shown in part B above). (5pts)

$$\frac{V_{out2} - (-5)}{5K} = \frac{-5 - V_{out3}}{1K} \quad (4pts)$$

$$V_{out2} - 5 = -25 - 5V_{out3}$$

$$5V_{out3} = -25 - 5 - V_{out2}$$

$$V_{out3} = \frac{-30 - V_{out2}}{5} = \frac{-30 - (-15)}{5} = \frac{-15}{5} = -3V \quad (1pt)$$

V_{out3}	_____
------------	------------------