

ECSE 2010
Electric Circuits
Exam 2
Spring 2006

Name _____

Section (please circle one)

MR
10-12
Millard

MR
2-4
Salama

MR
4-6
Kraft

Please Note:


- Place all your answers in the spaces provided.
- You MUST show your work to receive any credit.
- Assume all resistances are in ohms, if not otherwise indicated.

Problem No.	Pts.	Score
1	20pts	
2	20pts	
3	20pts	
4	20pts	
5	20pts	
Total	100pts	

Problem 1 (20pts)

Name _____

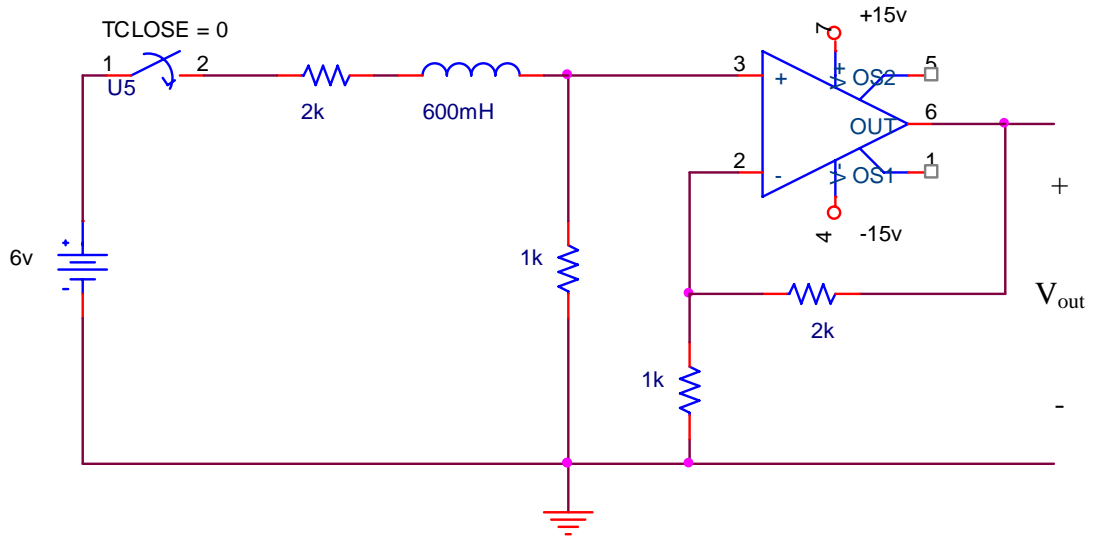a) Find the differential equation for $V_{out}(t)$ for the circuit shown below. (assume that the op-amp has the correct supplies).




$V_{out}(t)$	
--------------	--

Problem 1 (cont)

Name _____

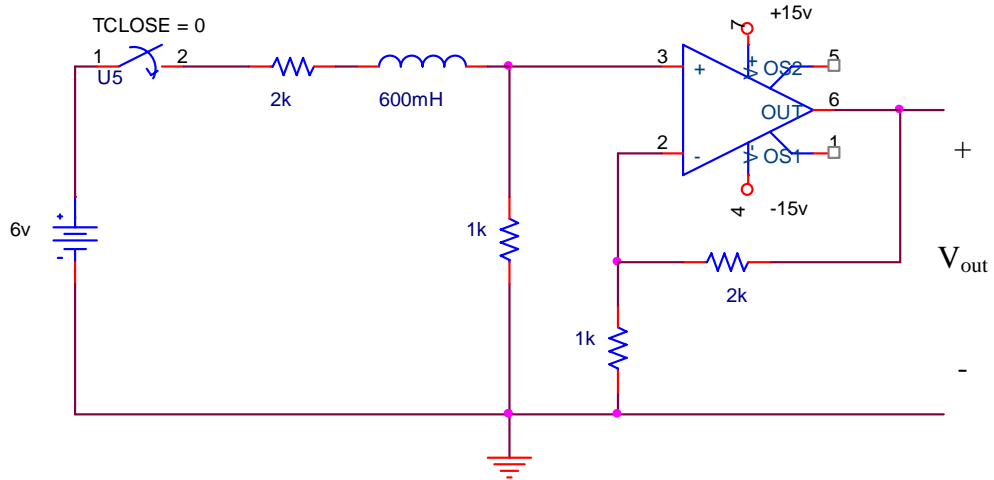b) Sketch the $V_{out}(t)$ for the circuit shown below including all pertinent values (e.g time constants, etc.).




$V_{out}(t)$



Problem 2 (20pts)

Name _____

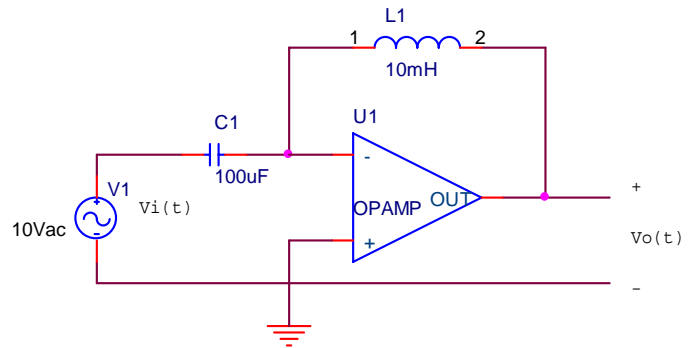a) For the circuit, find the differential equation relating $i_c(t)$ (the current in the capacitor) to $v_i(t)$ and the differential equation relating $i_L(t)$ (the current in the inductor) to $v_o(t)$. (assume that the op-amp has the correct supplies).



$i_c(t)$	
$i_L(t)$	

Problem 2 (cont)

Name _____

b) Find an expression for $v_o(t)$ in terms of $v_i(t)$ for the circuit shown in part a.

$v_o(t)$	
----------	--


c) What is $v_{out}(t)$ if the input is: $v_i(t) = 10\cos(1000t)$?

$v_o(t)$	
----------	--

Problem 3 (20pts)

Name _____

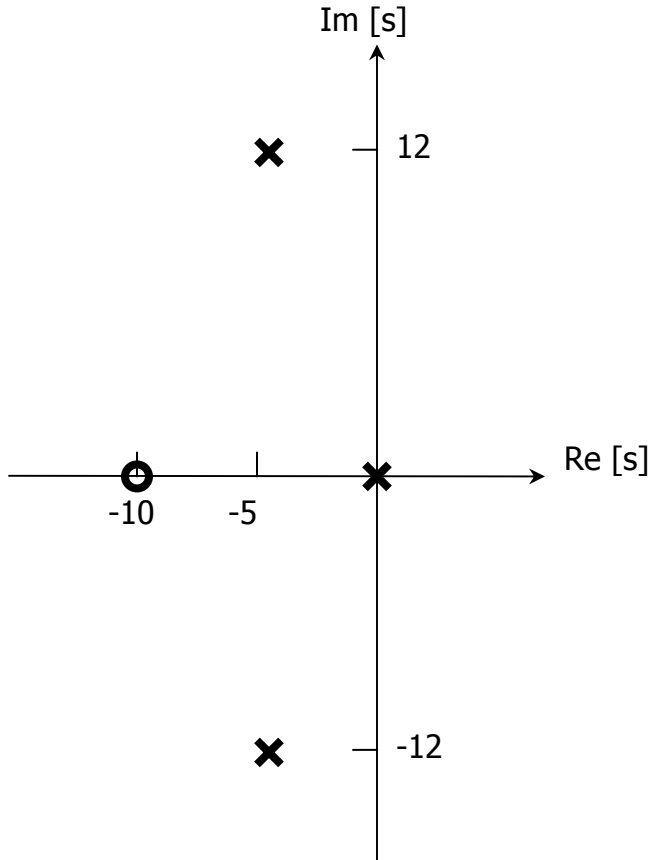a) The output $Y(s)$ of a circuit is the product of the input $X(s)$ and the network function $H(s)$. The $Y(s)$ for a circuit has the following pole/zero diagram. Find $Y(s)$ as a ratio of polynomials in s . (Ignore any scaling or gain values.)



Y(s)	
------	--

Problem 3 (cont)

Name _____

b) If $Y(s)$ is the output when $X(s)$ results from a unit step function $1u(t)$, classify the circuit's damping (please support your response):

OVERDAMPED	CRITICALLY DAMPED	UNDERDAMPED	OSCILLATOR
------------	-------------------	-------------	------------


c) Find the damping ratio ζ , for the circuit.

d) Find $y(t)$, the circuit's response and inverse Laplace transform of $Y(s)$, if $x(t)$ is still a unit step function $1u(t)$.

Problem 4 (20pts)

Name _____

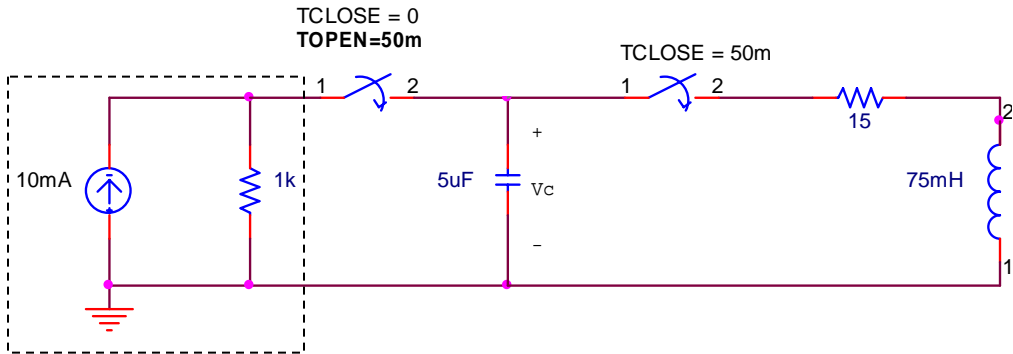a) For the circuit find an expression for $v_C(t)$ for $0 \leq t < 50\text{ms}$. Assume that $v_C(0^-) = 0\text{V}$ and the switches change state at $t=50\text{ms}$.



$v_C(t)$		$0 \leq t < 50\text{ms}$
----------	--	--------------------------

Problem 4 (cont)

Name _____

b) At time $t = 50\text{ms}$ the first switch opens and the second switch closes. Assuming the capacitor has charged to 10V at $t = 50\text{ms}$, find an expression for $v_C(t)$ for $t \geq 50\text{ms}$.

$v_C(t)$		$t \geq 50\text{ms}$
----------	--	----------------------

c) Find the differential equation relating $i_L(t)$ (the current in the inductor) for $t \geq 50\text{ms}$.

$i_L(t)$		$t \geq 50\text{ms}$
----------	--	----------------------


d) Classify the solution for $v_C(t)$ for $t \geq 50\text{ms}$. (circle one)

OVERDAMPED	CRITICALLY DAMPED	UNDERDAMPED	OSCILLATOR
------------	-------------------	-------------	------------

Problem 5 (20pts)

Name _____

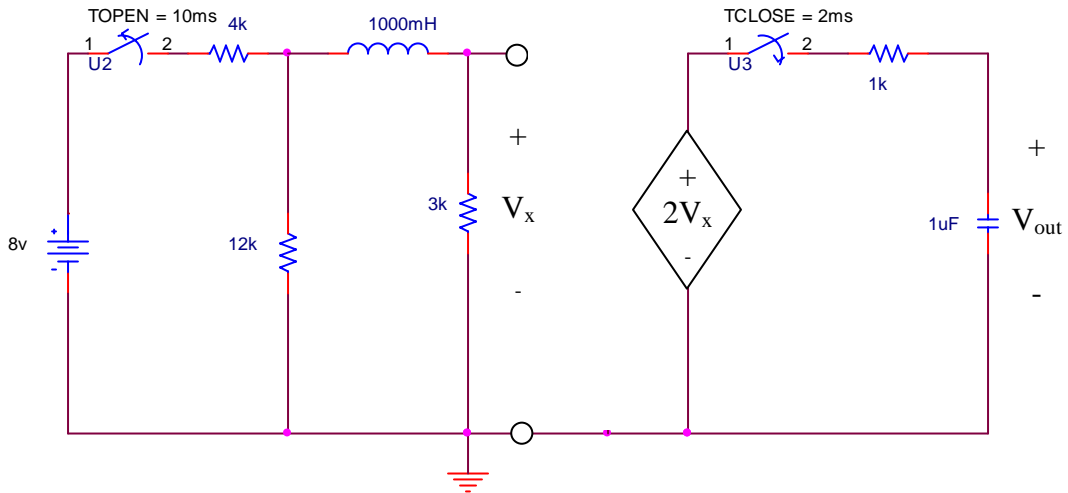a) Find the value of V_x at $t=3\text{ms}$, given the circuit shown.



V_x (3ms)	
----------------	--


b) Find V_x at $t = 10\text{ms}$.

V_x (10ms)	
-----------------	--

Problem 5 (cont)

Name _____

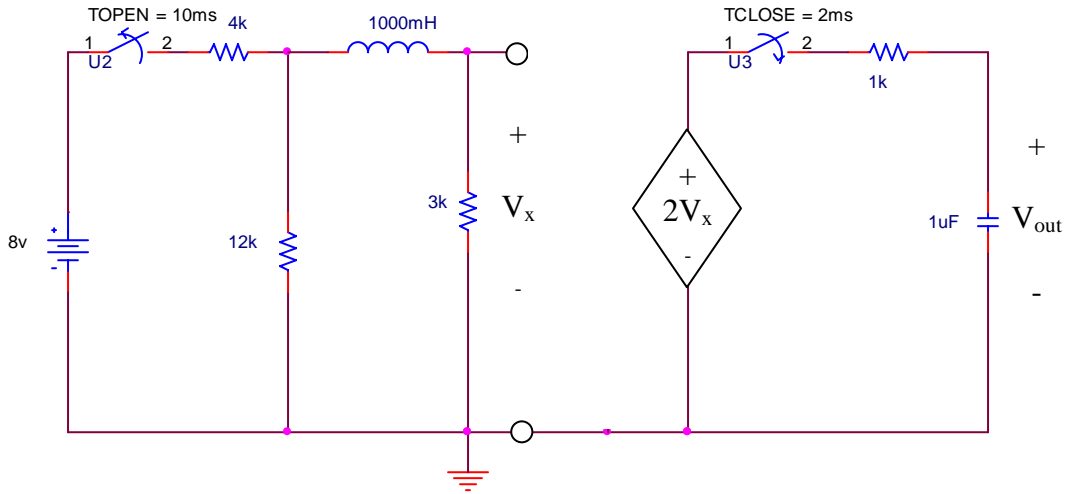c) Find the differential equation for $V_{out}(t)$ (for $20ms > t \geq 2ms$) given the circuit shown.



d) Find V_{out} at time $t = 10ms$.

V_{out} (10ms)	
---------------------	--

Extra space (if needed)

Name _____

Extra space (if needed)

Name _____