

ECSE 2010
Electric Circuits
Exam 2
Spring 2006

Name Solutions - D

Section (please circle one)

MR	MR	MR
10-12	2-4	4-6
Millard	Salama	Kraft

Please Note:


- Place all your answers in the spaces provided.
- You MUST show your work to receive any credit.
- Assume all resistances are in ohms, if not otherwise indicated.

Problem No.	Pts.	Score
1	20pts	
2	20pts	
3	20pts	
4	20pts	
5	20pts	
Total	100pts	

Problem 1 (20pts)

Name Solutions

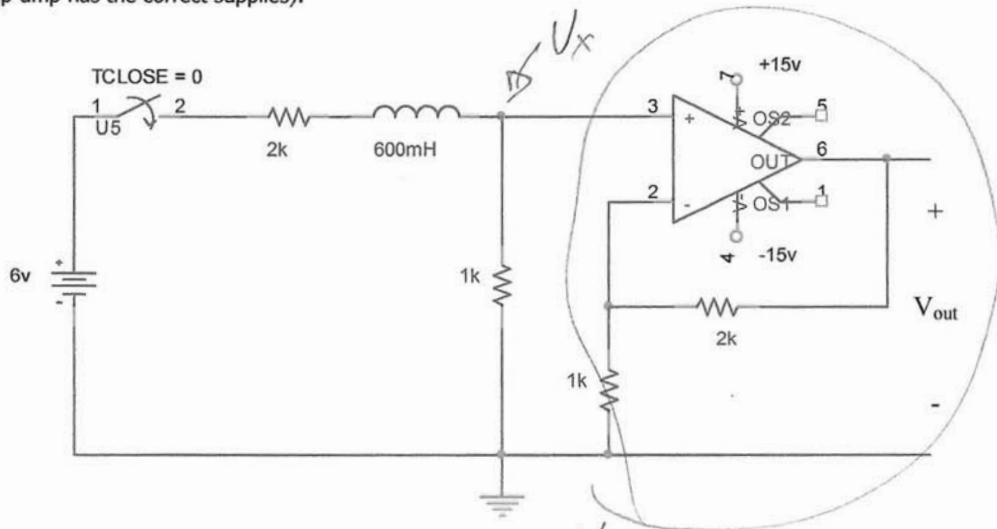a) Find the differential equation for $V_{out}(t)$ for the circuit shown below. (assume that the op-amp has the correct supplies).



$$\frac{V_{out}}{V_x} = A_v = 1 + \frac{2k}{1k} = 3$$

$$6u(t) - 2ki - L \frac{di}{dt} - 1ki = 0$$

$$L \frac{di}{dt} + 3ki = 6u(t)$$

$$\frac{di}{dt} + 5000i = 10u(t)$$

5pts $V_x = (1k) \cdot 2mA (1 - e^{-t/\tau})$

$$V_{out} = 3V_x = 6(1 - e^{-t/\tau})$$

$sI(s) + 5000I(s) = \frac{10}{s}$ (R/L)	$V_{out}(t)$	$6v(1 - e^{-5000t})u(t)$	15pts
--	--------------	--------------------------	-------

$$I(s) = \frac{10}{s(s+5000)}$$

$$I_{ss} = \frac{6}{3k} = 2mA$$



10pts $I_{initial} = 0$ $i(t) = 2mA(1 - e^{-t/\tau})$

$$\tau = \frac{L}{R} = \frac{.6}{3k} = .2ms$$

Problem 1 (cont)

Name Solutions

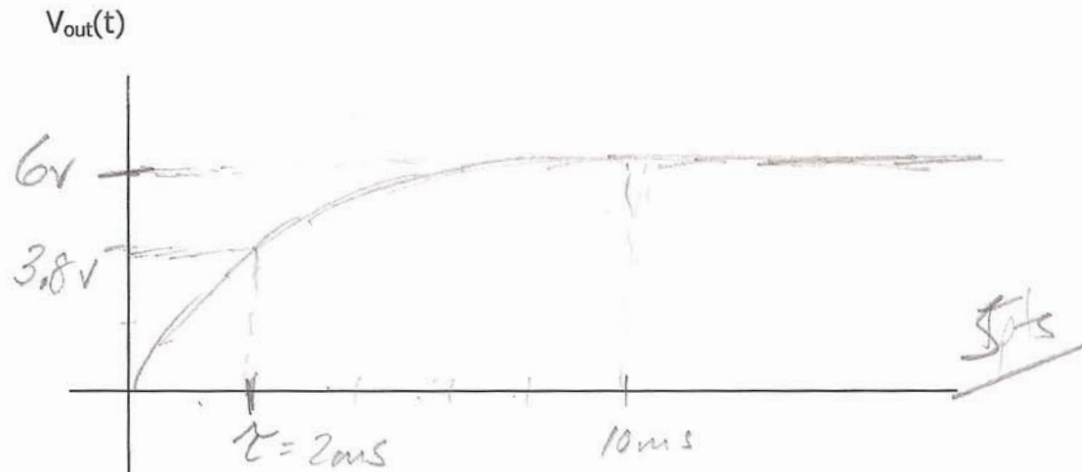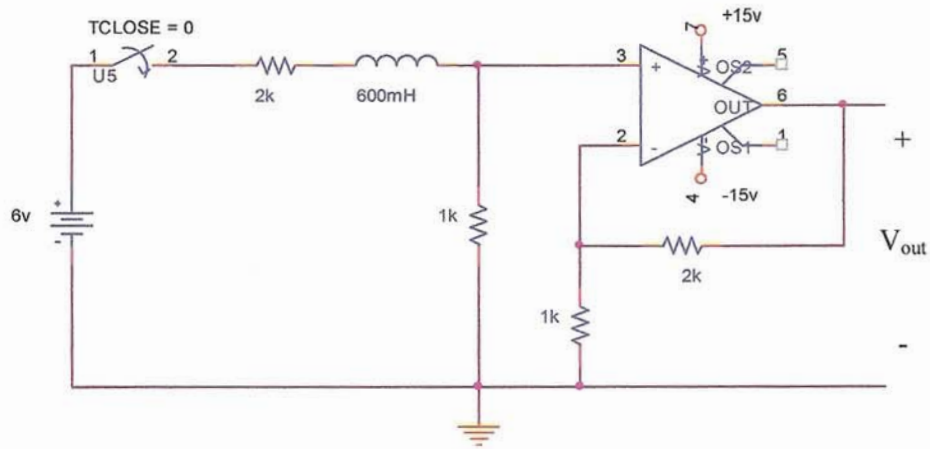b) Sketch the $V_{out}(t)$ for the circuit shown below including all pertinent values (e.g. time constants, etc.).



$$V(2ms) = 6(1 - e^{-1}) = 6(.63) = 3.78$$

$$V(10ms) \approx 6V$$

Problem 2 (20pts)


Name Solutions

a) For the circuit, find the differential equation relating $i_c(t)$ (the current in the capacitor) to $v_i(t)$ and the differential equation relating $i_L(t)$ (the current in the inductor) to $v_o(t)$. (assume that the op-amp has the correct supplies).

$$v_L(t) = L \frac{di_L}{dt}, \quad i_L = \frac{1}{L} \int v_L dt$$

$$i_C = C \frac{dv_C}{dt}$$
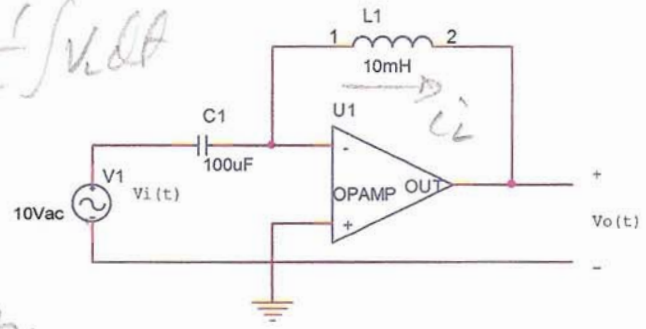
$$i_C = C \frac{d(v_i - 0)}{dt} = C \frac{dv_i}{dt}$$



$$i_L = \frac{1}{L} \int v_L dt = \frac{1}{L} \int (0 - v_{out}) dt$$

$$i_L = -\frac{1}{L} \int v_{out} dt$$

$i_C(t)$	$C \frac{dv_i}{dt}$	5pts
$i_L(t)$	$-\frac{1}{L} \int v_{out} dt$	5pts

Problem 2 (cont)

Name Solutions

b) Find an expression for $v_o(t)$ in terms of $v_i(t)$ for the circuit shown in part a.

$$i_c = i_L$$

$$C \frac{dv_{out}}{dt} = \frac{-1}{L} \int v_{out} dt$$

$$v_{out} = -LC \frac{d^2 v_i}{dt^2}$$

$v_o(t)$	$-LC \frac{d^2 v_i}{dt^2}$
----------	----------------------------

1/15

c) What is $v_{out}(t)$ if the input is: $v_i(t) = 10\cos(1000t)$?

$$\frac{dv_i}{dt} = -10(1000)\sin(1000t)$$

$$LC = .01 * 100\mu$$

$$LC = 10^{-6}$$

$$\frac{d^2 v_i}{dt^2} = -10(1000)^2 \cos(1000t)$$

$v_o(t)$	$10 \cos(1000t)$
----------	------------------

5/15


$$v_o(t) = -(-10 \overset{LC}{(1000)^2} \cos(1000t))$$

$$= +10 \cos(1000t)$$

Problem 3 (20pts)

Name _____

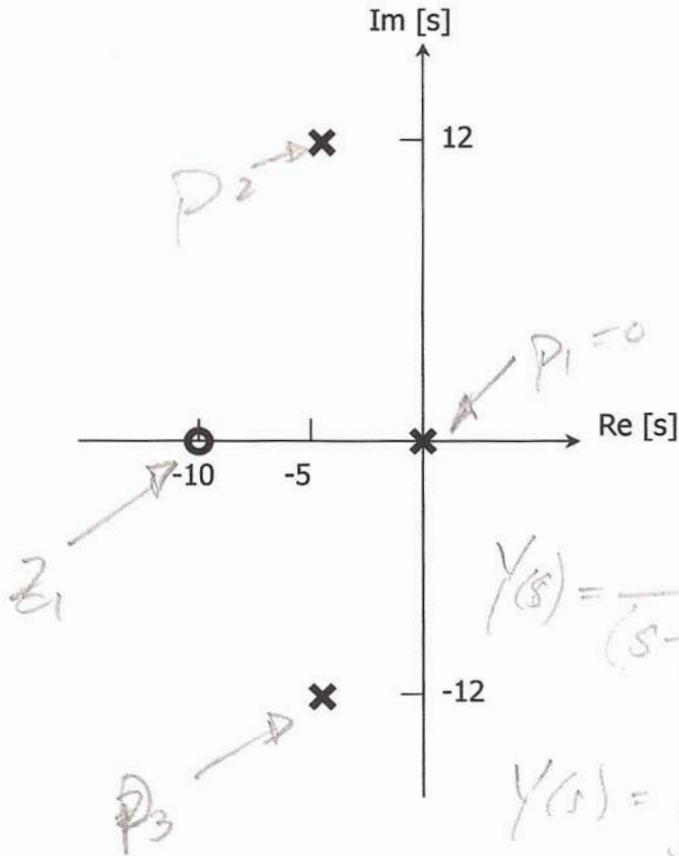a) The output $Y(s)$ of a circuit is the product of the input $X(s)$ and the network function $H(s)$. The $Y(s)$ for a circuit has the following pole/zero diagram. Find $Y(s)$ as a ratio of polynomials in s . (Ignore any scaling or gain values.)



$$Y(s) = \frac{s - z_1}{(s - p_1)(s - p_2)(s - p_3)}$$

$$Y(s) = \frac{(s + 10)}{s(s + 5 + j12)(s + 5 - j12)}$$

$$p_2 = -5 + j12$$

$$p_3 = -5 - j12$$

$$\beta = 12 = \sqrt{\omega_0^2 - \alpha^2}$$

$$\omega_0^2 = \beta^2 + \alpha^2 = 144 + 25 = 169$$

$Y(s)$	$\frac{s + 10}{s(s^2 + 10s + 169)}$
--------	-------------------------------------

(10pts)

Problem 3 (cont)

Name Solutions

b) If $Y(s)$ is the output when $X(s)$ results from a unit step function $1u(t)$, classify the circuit's damping (please support your response):

$\alpha^2 < \omega_0^2$

↓

OVERDAMPED	CRITICALLY DAMPED	UNDERDAMPED	OSCILLATOR
------------	-------------------	-------------	------------

(5 pts)

c) Find the damping ratio ζ , for the circuit.

$$\begin{cases} \omega_0 = \alpha \\ \zeta = \frac{\alpha}{\omega_0} = \frac{5}{13} \approx .4 \end{cases} \quad (3 \text{ pts})$$

d) Find $y(t)$, the circuit's response and inverse Laplace transform of $Y(s)$, if $x(t)$ is still a unit step function $1u(t)$.

$$X(s) = \frac{1}{s}$$

$$Y(s) = \frac{A_0}{s} + \frac{A_1}{(s+5+j12)} + \frac{A_1^*}{(s+5-j12)} \quad (2 \text{ pts})$$


$$y(t) = A_0 + 2A_1 e^{-\alpha t} \cos(\beta t + \phi)$$

$$y(t) = .06 + .08 e^{-5t} \cos(12t - 135^\circ)$$

Problem 4 (20pts)

Name Solutions

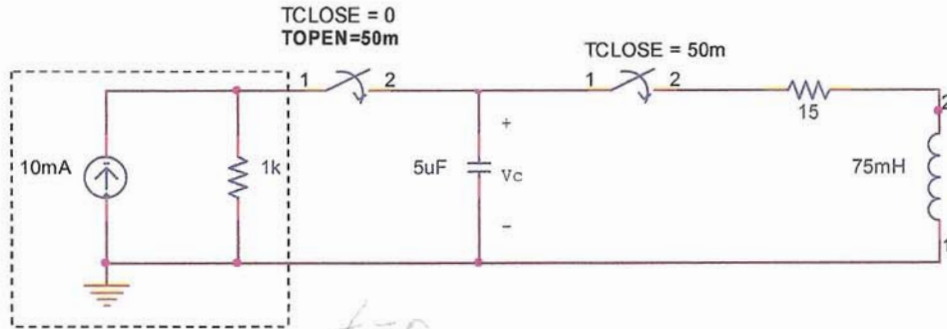a) For the circuit find an expression for $v_c(t)$ for $0 \leq t < 50\text{ms}$. Assume that $v_c(0^-) = 0\text{V}$ and the switches change state at $t=50\text{ms}$.



$$10 - RC \frac{dv_c}{dt} - v_c = 0$$

$$\tau = (1k)(5\mu F)$$

$$\tau = 5\text{ms}$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{10}{RC} u(t)$$

$$v_{c,ss} = 10\text{V}; v_{c,INT} = 0$$

$$v_c(t) = v_{ss} + (v_{INT} - v_{ss}) e^{-t/\tau}$$

$$v_c(t) = 10 + (0 - 10) e^{-t/5\text{ms}}$$

$$\tau = 5\text{ms}$$

$v_c(t)$	$10(1 - e^{-t/5\text{ms}}) u(t)$	$0 \leq t < 50\text{ms}$
----------	----------------------------------	--------------------------

8pts

Problem 4 (cont)

Name Solutions

b) At time $t = 50\text{ms}$ the first switch opens and the second switch closes. Assuming the capacitor has charged to 10V at $t = 50\text{ms}$, find an expression for $v_c(t)$ for $t \geq 50\text{ms}$.

Series RLC: $2\alpha = \frac{R}{L}$ $\omega_0^2 = \frac{1}{LC} = 2.7 \times 10^6$
 $\frac{1}{LC}$
 $\frac{s^2 + \frac{R}{L}s + \frac{1}{LC}}$
 $\alpha = \frac{R}{2L} = \frac{15}{2(0.075)} = 100$
 $\alpha^2 = (100)^2 = 10^4$ $\alpha^2 \ll \omega_0^2$

$v_c(t)$	$10e^{-100t} \cos(\beta t + \phi)$	$t \geq 50\text{ms}$
----------	------------------------------------	----------------------

1pts

$\beta = \sqrt{\omega_0^2 - \alpha^2} \approx \omega_0 = 1640$

c) Find the differential equation relating $i_L(t)$ (the current in the inductor) for $t \geq 50\text{ms}$.

$i_L(t) = -i_c = -C \frac{dv_c}{dt}$ (1pt)
 $i_L(t) = -C \frac{dv_c(t)}{dt} = -C \left[(-1000e^{-100t} \cos(1640t + \phi) - 16400e^{-100t} \sin(1640t + \phi)) \right]$ (1pt)

$i_L(t)$		$t \geq 50\text{ms}$
----------	--	----------------------

2pts

d) Classify the solution for $v_c(t)$ for $t \geq 50\text{ms}$. (circle one)


OVERDAMPED	CRITICALLY DAMPED	<u>UNDERDAMPED</u>	OSCILLATOR
------------	-------------------	--------------------	------------

5pts

Problem 5 (20pts)


Name Solutions

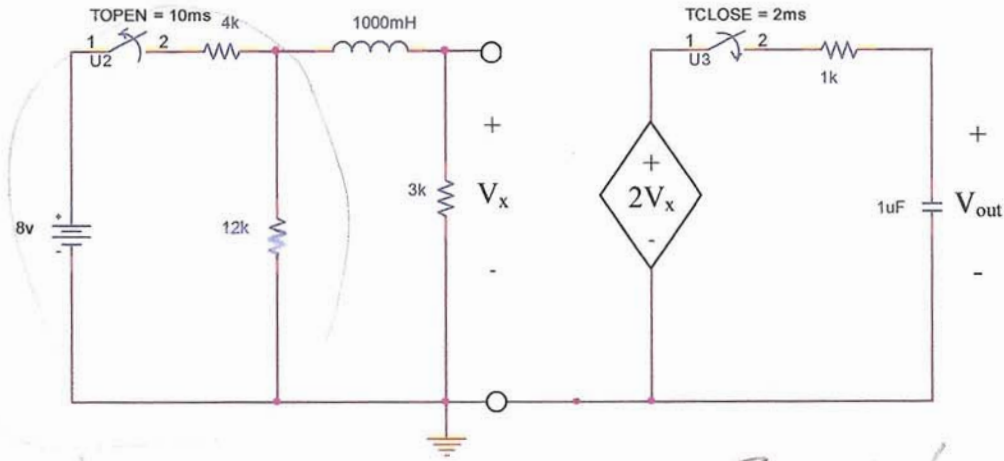a) Find the value of V_x at $t=3\text{ms}$, given the circuit shown.



Theremin \rightarrow 3k

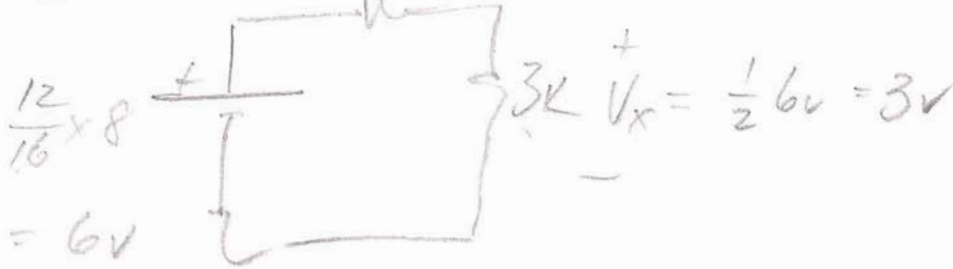$\tau = 5 \cdot \frac{1}{6k} = \frac{5}{6000} < 2\text{ms}$



$\frac{12}{16} \times 8 = 6\text{V}$

$i = \frac{1}{6k} = 0.00017$

V_x (3ms)	3v
----------------	----

5pts

b) Find V_x at $t = 10\text{ms}$.

$i_L(10^-) = \frac{6\text{V}}{6k} = 1\text{mA}$

$i_L(0^+) = i_L(0^-) = 1\text{mA}$

$V_x = 3k \cdot 1\text{mA} = 3\text{V}$


V_x (10ms)	3v
-----------------	----

5pts

Problem 5 (cont)

Name Solutions

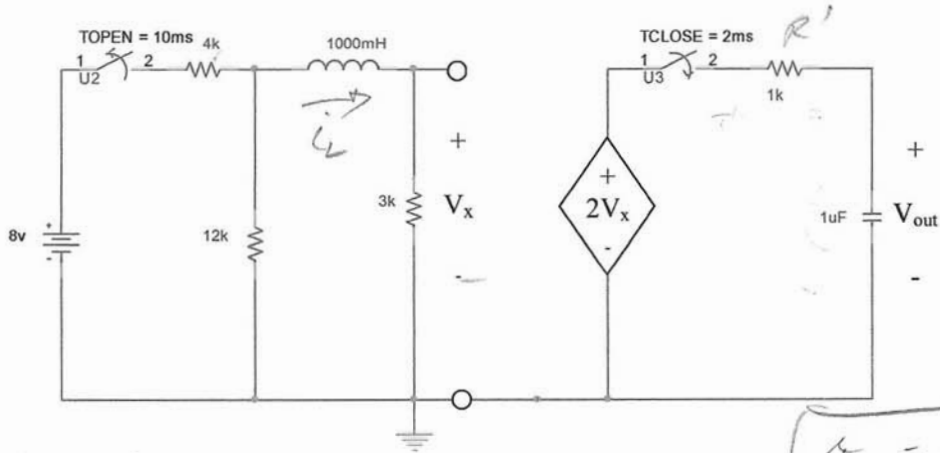c) Find the differential equation for $V_{out}(t)$ (for $20ms > t \geq 2ms$) given the circuit shown.



for $2ms < t < 10ms$

$$i_L = 1mA, V_x = 3V; \underline{2V_x = 6V}$$

$$6V - iR' - V_{out} = 0$$

$$6V - R'C \frac{dV_{out}}{dt} - V_{out} = 0$$

$$\frac{dV_{out}}{dt} + \frac{1}{R'C} V_{out} = \frac{6}{R'C}$$

$$\tau_{RC} = 1ms$$

$$\tau_{LR} = \frac{L}{R} = \frac{1}{15k} \ll \tau_{RC}$$


for $10ms < t < 20ms$

$$R'C \frac{dV_{out}}{dt} + V_{out} = 0$$

$$\frac{dV_{out}}{dt} + \frac{1}{R'C} V_{out} = 0$$

(5pts)

d) Find V_{out} at time $t = 10ms$.

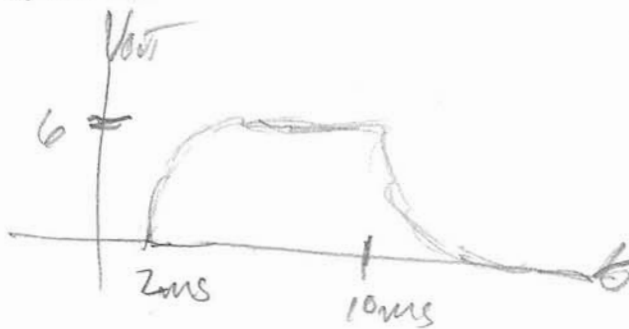

V_{out} (10ms)	6V
---------------------	----

5pts