

ECSE 2010
Electric Circuits
Final Exam
Fall 2007

Name _____

Section (please circle one)

10-12
Millard

12-2
Zhang


Please Note:

- Place all your answers in the spaces provided.
- You MUST show your work to receive any credit.
- Assume all resistances are in ohms, if not otherwise indicated.

Problem No.	Pts.	Score
1	20pts	
2	20pts	
3	20pts	
4	30pts	
5	20pts	
6	30pts	
7	20pts	
Total	160pts	

Problem 1 (20pts)

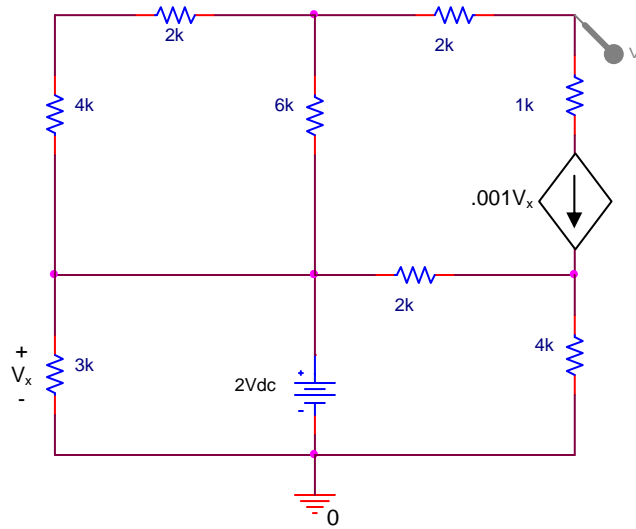
a) Find the voltage at the marker shown in the circuit below. (10pts)



V_{marker}	
---------------------	--

Problem 1 (cont)

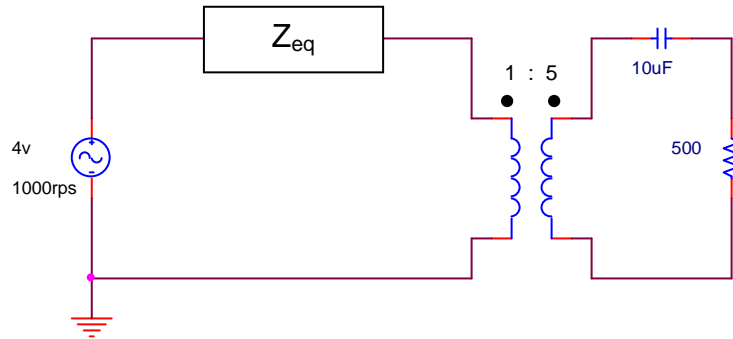
b) Find Z_{eq} , both the value and component type(s), that would maximize the power delivered to the 500 ohm resistor in the circuit shown. (10pts)



Z_{eq}	
Component(s) (and values)	

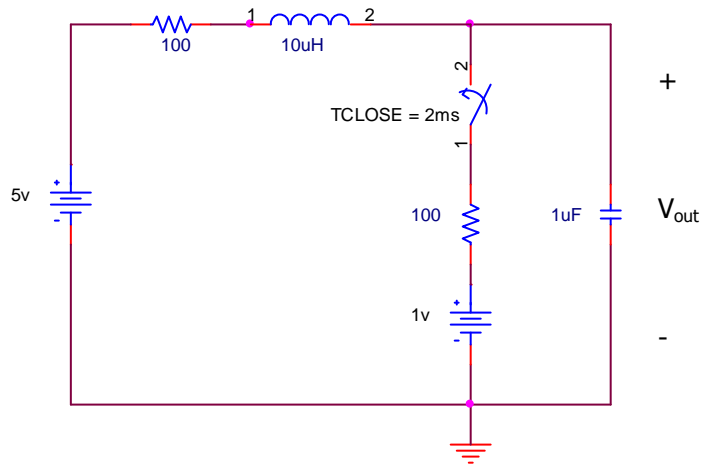Problem 2 (20pts)


a.) Draw the circuit in the s-domain and find the damping coefficient (ζ) of the circuit for $0 < t < 2\text{ms}$. (5pts)



ζ	
---------	--

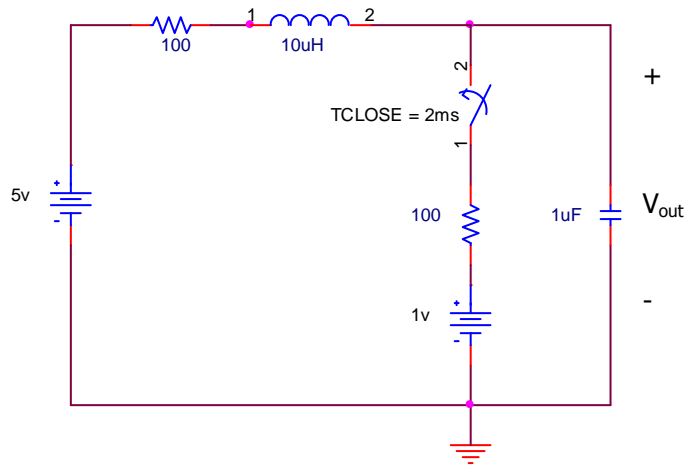Problem 2 (cont)

b.) What circuit modification could you make that would cause the circuit to produce a critically damped response for $0 < t < 2\text{ms}$, assuming that the initial conditions were zero at $t < 0$? Please explain your answer. (5pts)



Problem 2 (cont)

c.) Find $V_{out}(s)$ for $t > 2ms$ (using the circuit shown in parts a & b). Remember that the Laplace transform of $u(t) = 1/s$. Please note: You do **NOT** have to find $V_{out}(t)$. (5pts)

$V_{out}(s)$ ($t > 2ms$)	
-------------------------------	--

d.) **Sketch** $V_{out}(t)$ for all $t \geq 0$. Show all pertinent points in time, including the appropriate time constants and voltage values (5pts)



Problem 3 (20pts)

The following three loads are connected across a $120V_{\text{rms}}$ 60Hz AC generator:

Load #1 has 900 VA and has -636 VARS

Load #2 has 364 Watts and has a $\text{pf}_1 = .5$ **lagging**

Load #3 has 875 VA and has a $\text{pf}_1 = 0$ **lagging**

a) Determine the total apparent power of the three loads. (5pts)

$$|S|_{\text{total}} =$$

b) Determine the power factor of the combined loads. (5pts)

$$\text{pf}_{\text{combination}} =$$

Problem 3 (cont)

c) Determine the capacitance that will be necessary in order to make the overall $\text{pf} = 1.0$, assuming that the voltage across the load is to be kept at 120V_{rms} . (5pts)


C =

d) Determine the difference in the current drawn from the generator (e.g the difference in the current drawn with and without power factor correction). (5pts)

I difference (I non-corrected - I corrected)	
---	--

Problem 4 (30pts)

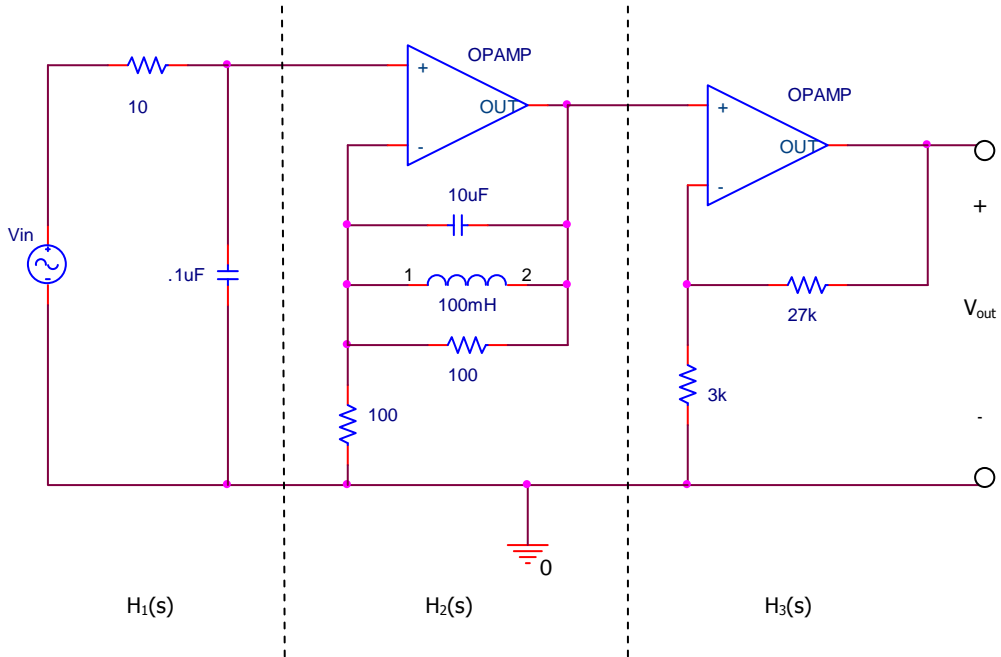a) Find $H_1(s)$, $H_2(s)$, $H_3(s)$, and the overall transfer function $V_{out}/V_{in} = H(s) = H_1(s)H_2(s)H_3(s)$ for the circuit shown below. (10pts)



$H_1(s)$	
$H_2(s)$	
$H_3(s)$	
$H(s)$	

Problem 4 (cont)

b) Sketch the asymptotic graphs of $|H(j\omega)|_{db} = |V_{out}/V_{in}|$ and $\angle H(j\omega)$ for the circuit shown in part a on the previous page. Please clearly label your axes as appropriate. (10pts)



Problem 4 (cont)

c) It is desired to have an output sinusoid with an amplitude of 20v for an input $V_{in}(t) = A \cos(50_{\text{rps}}t)$ volts (for the circuit shown in part a). What must the value of **A** be? (5pts)


A	
----------	--

d) What frequency (ω) will change an input that is $= 1 \cos(\omega t)$ into an output $= 7.07 \cos(\omega t - 45)$ (using the circuit shown in part a)? Explain and justify your response. (5pts)

ω	
----------	--

Problem 5 (20pts)

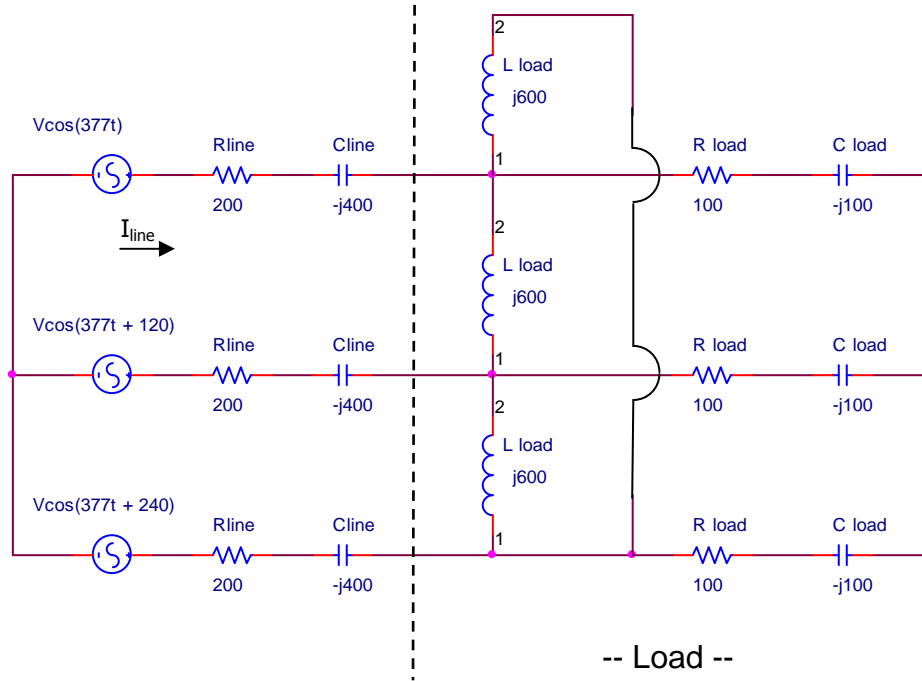a) Given the following 3 phase circuit, what is the equivalent single phase load impedance to the right of the dashed line? (5pts) (Please justify your response)




Z_{load}	
------------	--

b) What is the line current I_{line} (in rms) flowing in each line resistance (R_{line}) associated with the three phases if each of the phase voltages is $V_{\phi} = 56.6kV_{rms}$? (5pts)

I_{line}	
------------	--

Problem 5 (cont)

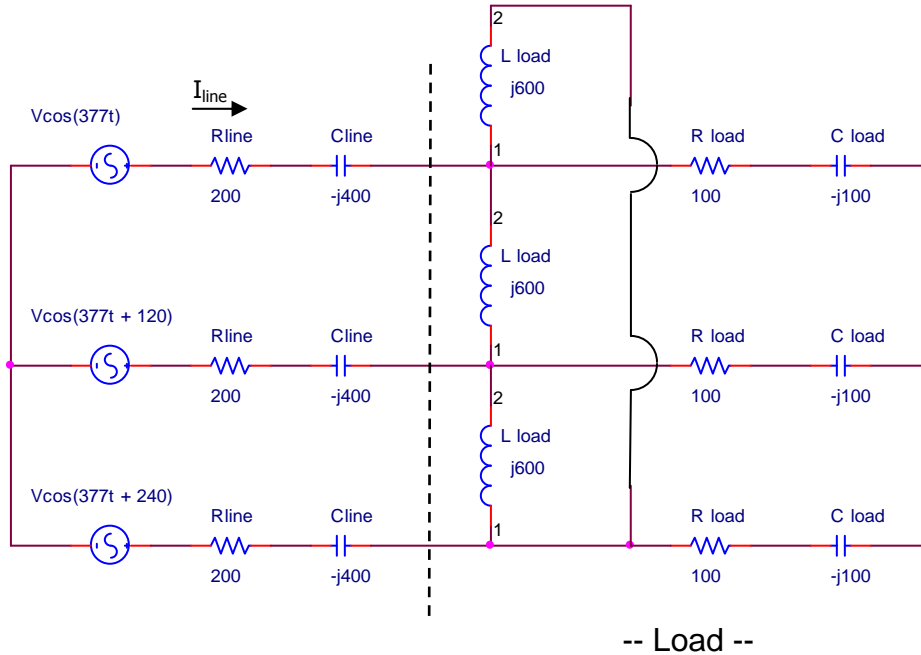c) What is the total average real power (in rms) dissipated by the three phases' line resistances (R_{line}) if each of the phase voltages is $V_{\Phi} = 56.6kV_{rms}$? (5pts)




P_{line}	
------------	--

d) What is the efficiency of the transmission system, defined as: $P_{load-average}/P_{total} * 100\%$? (5pts)

Efficiency	
------------	--

Problem 6 (30pts)

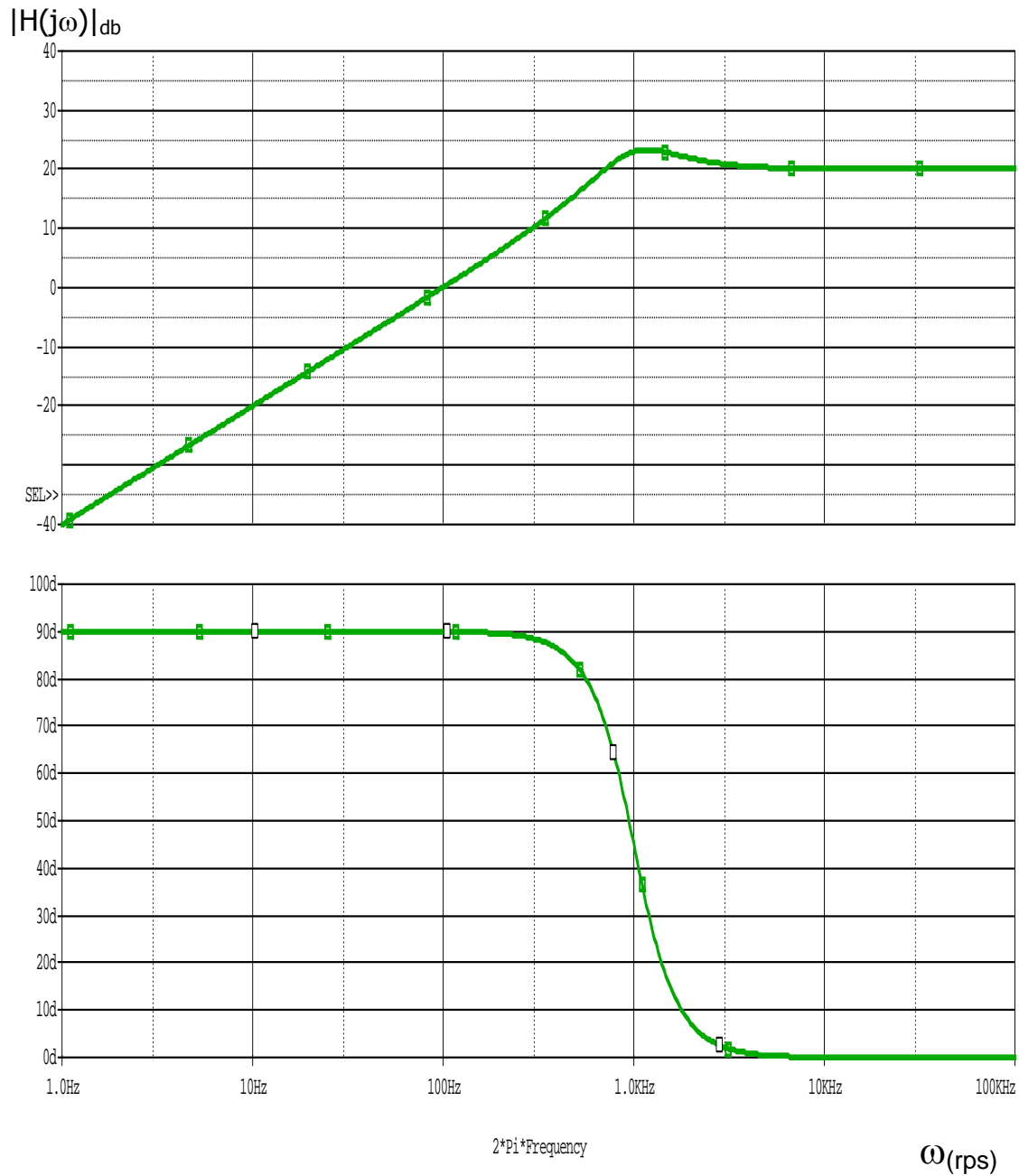- a) Given the plots below, find the cutoff frequency ω_{co} of the circuit that would produce the response shown. (5pts)



$\omega_{co} =$

Problem 6 (cont)

b) Design a circuit that would produce the Bode Plot given in part (a). Assume that you only have **one** capacitor, **one** inductor, **six** resistors and **two** op-amps available. Please provide values for your component choices and show your circuit schematic. Please specify and provide support for your component choices and circuit topology. (Note: you don't have to use all the components). (15pts)

Problem 6 (cont)


c) Develop $H(s)$ for the circuit you designed in part b. (5pts)

$H(s)$	
--------	--

d) **briefly** justify that it produces the graphs shown in part a. (5pts)

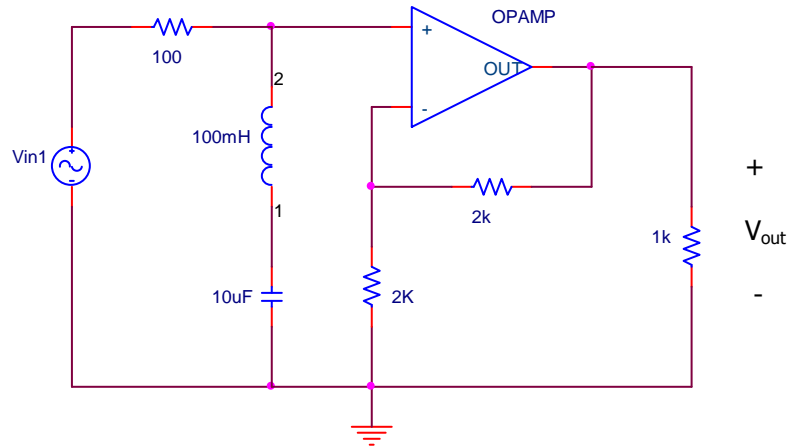Problem 7 (20pts)


a.) Find $V_{out}(t)$ for the circuit below, if the circuit is being driven by an input signal $V_{in}(t) = 10\cos(\omega_0 t)$ where ω_0 is the resonant frequency. Please briefly justify your response. (5pts)



$V_{out}(t)$	
--------------	--

Problem 7 (cont)

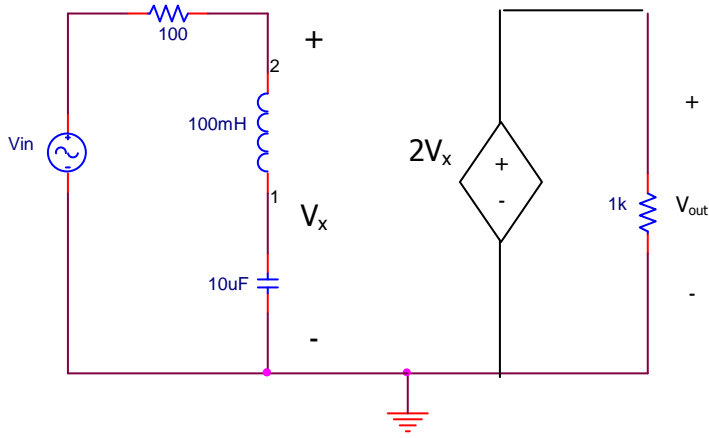b) Find $V_{out}(s)$ in terms of $V_{in}(s)$ for the circuit shown below. (Note: V_x is across both the inductor and the capacitor.) Please show your work for credit. (10pts)



$V_{out}(s)$	
--------------	--

c) Briefly discuss the relationship of the circuit shown in part b to that which is shown in part a. (5pts)

Extra space (if needed)

Name _____

Extra space (if needed)

Name _____