


ECSE 2010
Electric Circuits
Exam 1
Spring 2007

Name

Solutions 

Section (please circle one)

MR
10-12
Millard

MR
2-4
Abouzeid


Problem No.	Pts.	Score
1	20pts	X/20
2	20pts	X/20
3	20pts	X/20
4	20pts	X/20
5	20pts	X/20
Total	100pts	X/100

Please Note:

- * Place all your answers in the spaces provided.
- * You MUST show your work to receive any credit.

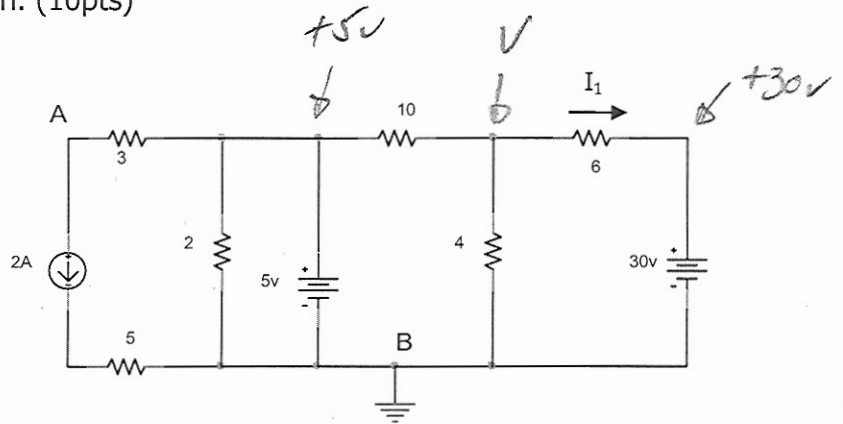Problem 1 (20pts)

a.) Find I_1 in the circuit shown. (10pts)



KCL @ V:

$$\frac{V-5}{10} + \frac{V}{4} + \frac{V-30}{6} = 0 \quad (5pts)$$

$$I_1 = \frac{V-30}{6} \quad (5pts)$$

X60

$$6V - 30 + 15V + 10V - 300 = 0 ; \quad 2.4V - 12 + 6V + 4V - 120 = 0$$

$$12.4V = 132$$

$$31V = 330$$

$$V = \frac{330}{31} = 10.65$$

$$V = \frac{132}{12.4} \approx 10.65$$

$$I_1 = \frac{\frac{330}{31} - 30}{6} = -3.225A$$


$$\approx -3.23$$

I_1	$-3.23A$
-------	----------

Problem 1 (cont)

b.) Find the voltage V_{AB} in the circuit shown. (10pts)

$$V_B = 0v$$

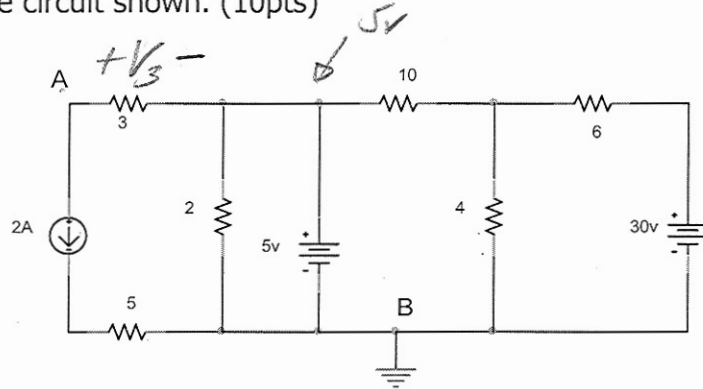


$$V_3 = -2A \times 3 = -6v$$

$$V_A = 5v + (-6v) = -1v$$


V_{AB}	$-1v$
----------	-------

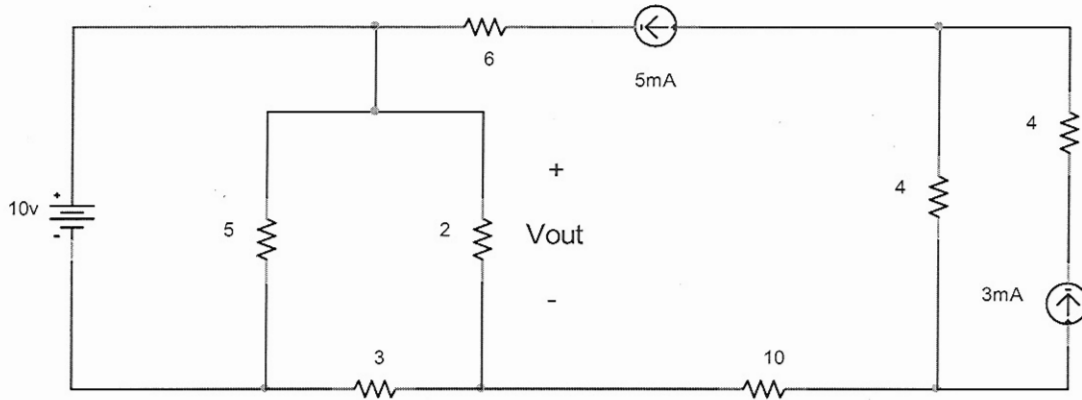Problem 2 (20pts)

a.) Find the voltage V_{out} across the $2\text{k}\Omega$ resistor due to each of the sources using superposition for the circuit shown. (15pts)




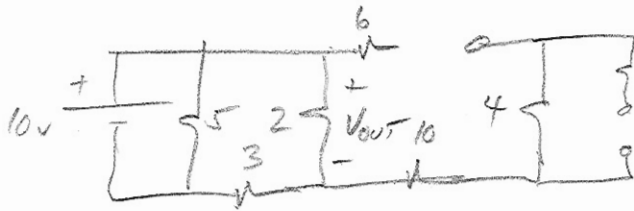$V(10v)$ $5mA \rightarrow \text{open}$
 $3mA \rightarrow \text{open}$



$$V_{out} = 10 \times \frac{2k}{5k} = 4v$$

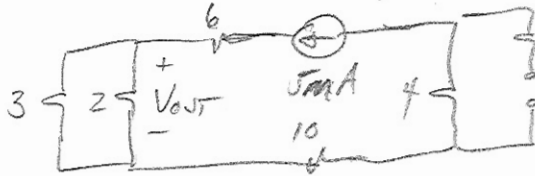$V(5mA)$ $10v \rightarrow \text{short}$
 $3mA \rightarrow \text{open}$



$$V_{out} = I_2 \times Z = \left(5mA \frac{3k}{5k}\right) \times 2k = 6v$$


$V(3mA)$ $I=0$



$V_{out} (10v)$	4v
$V_{out} (3mA)$	6v
$V_{out} (5mA)$	0v

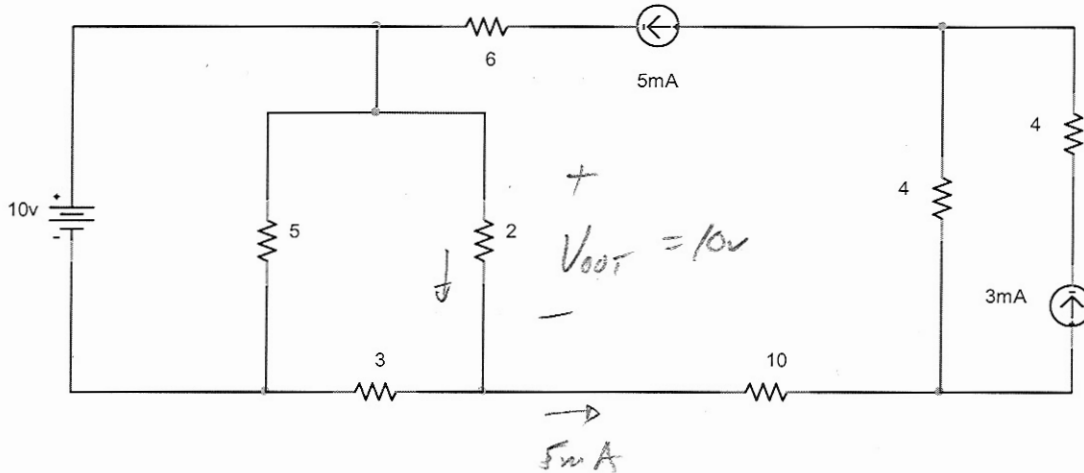Problem 2 (cont)

b.) Find the power delivered to the 5, 6, and the 3ohm resistors. (5pts)



$$P_5 = \frac{V^2}{R} = \frac{(10)^2}{5k} = 20mW$$

$$P_6 = I^2 R = (5mA)^2 6k = 150mW$$

$$P_3 = VI = 0I = 0$$

$P_{5\text{-ohm}}$	20 mW
$P_{6\text{-ohm}}$	150 mW
$P_{3\text{-ohm}}$	0


Problem 3 (20pts)

Find V_{out} for the circuit shown (where the probe is located with respect to ground) using your choice of either mesh or nodal analysis. Please show all your work.

$\partial V_1:$

$$I_x + \left(\frac{V_1 - V_0}{2k}\right) + \left(\frac{V_1 - 2}{5k}\right) = 0$$
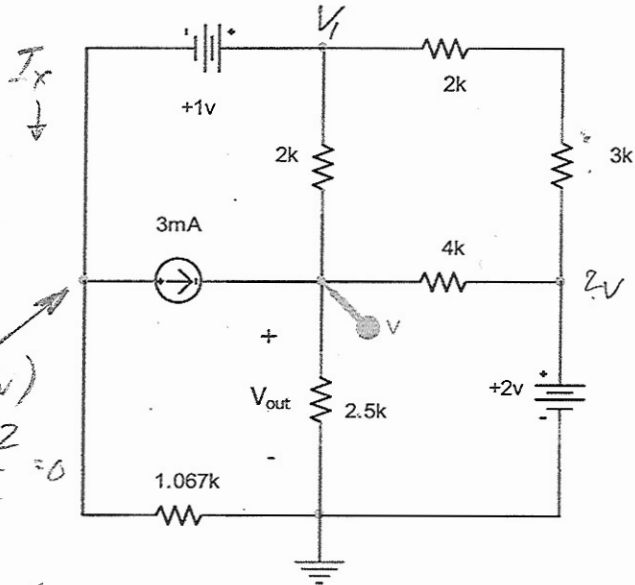
$$3mA + \frac{(V_1 - 1V)}{1.067k} + \frac{V_1 - V_0}{2k} + \frac{V_1 - 2}{5k} = 0$$



$$15 + 4.69(V_1 - 1) + 2.5(V_1 - V_0) + V_1 - 2 = 0$$

$$I_x = 3mA + \frac{(V_1 - 1V)}{1.067k}$$

$$V_1(4.69 + 2.5 + 1) + V_0(-2.5) = (-15 + 4.69 + 2)$$

$\partial V_0:$

$$8.19V_1 - 2.5V_0 = -8.31$$

$$-3mA + \frac{V_0}{2.5k} + \frac{V_0 - 2}{4k} + \frac{V_0 - V_1}{2k} = 0$$

$$-12 + 1.6V_0 + V_0 - 2 + 2V_0 - 2V_1 = 0$$

$$-2V_1 + 4.6V_0 = 14$$

$$-1.086 + 2.5V_0 = 7.6$$

$$7.104V_1 = -7.1$$

$$V_1 \approx -1$$


$$V_{out} = \frac{(14 + 2)}{4.6} = 3.08 \approx 3V$$

2 equations
2 unknowns

V_{out}	3V
-----------	----

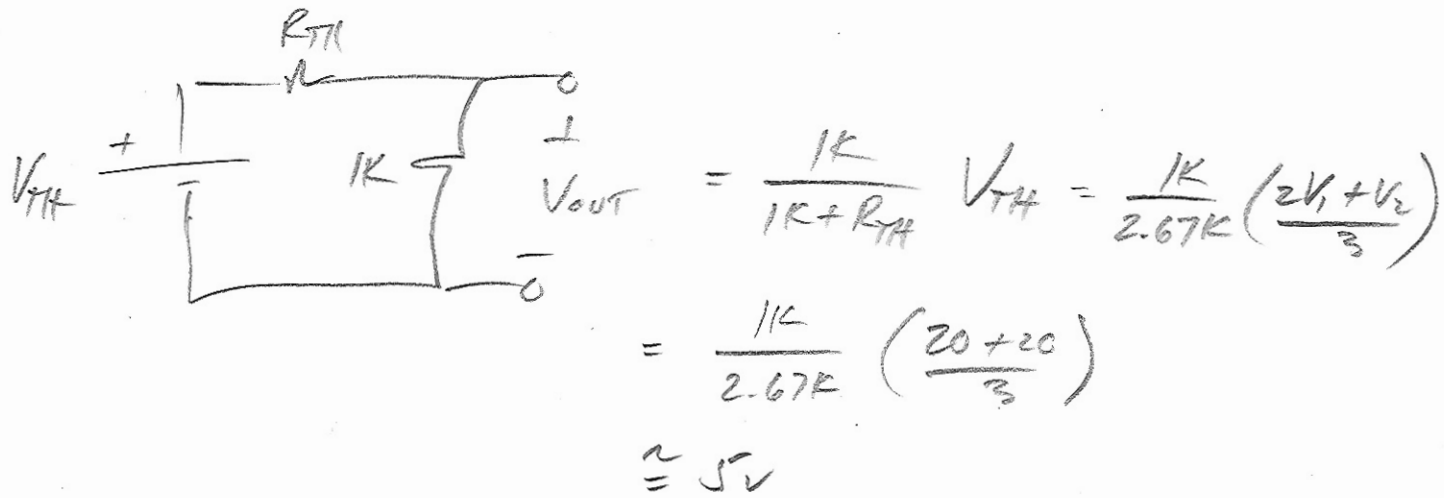Problem 4 (cont)

b.) Find V_{out} across the 1k resistor if $V_1 = 10v$ and $V_2 = 20v$. (5pts)



V_{out}	5V
-----------	----

c.) Determine the power supplied by the 10v source. (5pts)

$$\frac{V_x - 10}{1K} + \frac{V_x - 20}{2K} + \frac{V_x - 5}{1K} = 0$$

$$2V_x - 20 + V_x - 20 + 2V_x - 10 = 0$$

$$5V_x = 50$$

$$V_x = 10$$

$$I_{10v} = \frac{V_1 - V_x}{1K} = \frac{10 - 10}{1K}$$


P_{10v}	0w
-----------	----

$$I_{10v} = \frac{0}{1K} = 0!$$

$$P = VI = 10 \times 0 = 0w.$$

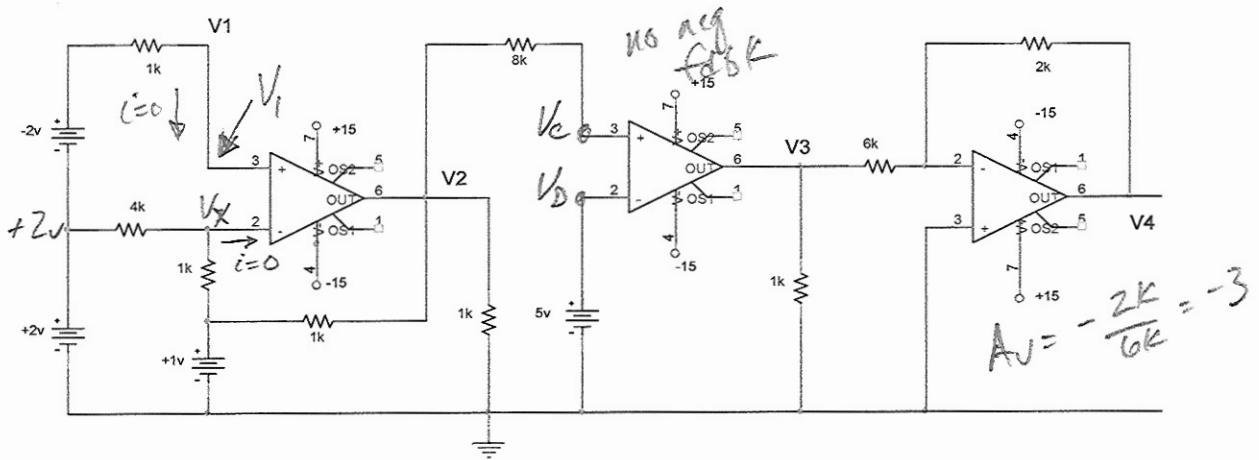Problem 5 (20pts)

Assume that all the Op Amps have ± 15 volt supplies for the following circuits.



a.) Find V_1 and V_2 in the above circuit. (10pts)

$$V_1 = +2V + (-2V) = 0V$$

$$V_x = 1V + (2-1) \frac{1K}{1K+4K} = 1.2V$$

$$V_x \neq V_1 \quad (\text{not in linear mode})$$

$$\text{Thus } V_2 \rightarrow \pm V_{cc} = \pm 15V$$

* Credit should be given for any reasonable response.


* most likely:

$$V_2 = (V_x - V_1) \times (+\infty) \rightarrow \underline{\underline{+15V}}$$

V_1	0
V_2	$\pm 15V$

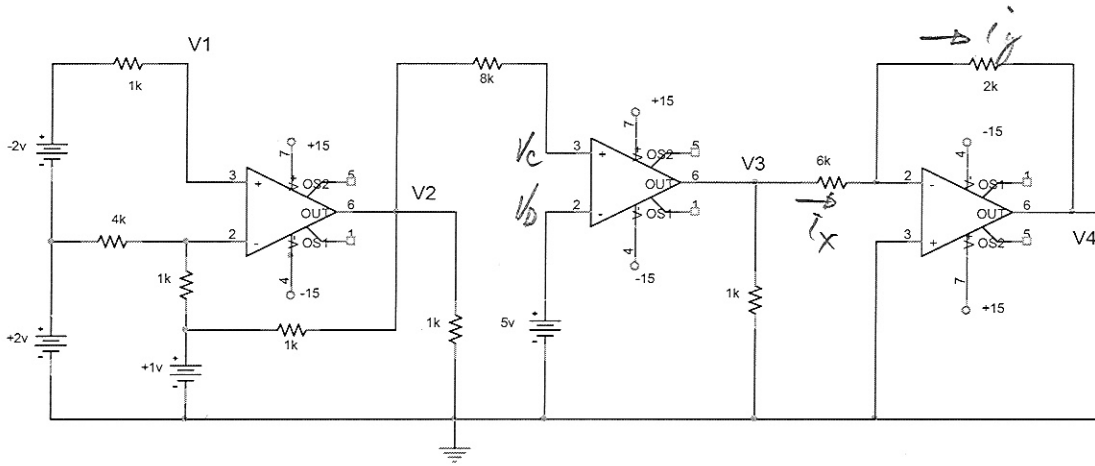Problem 5 (cont)

b.) Find V3 and V4 in the circuit (the same circuit as part a). (10pts)



If $V_2 = -15V$

$V_c = V_+ = \pm 15V$

$V_D = V_- = 5V$

$V_{DIFF} = V_+ - V_- = +10 / -20$

$V_{DIFF} \times (\infty) \rightarrow \pm \infty \rightarrow \pm 15V$

$i_x = i_y ; \frac{V_3}{6K} = \frac{-V_4}{2K}$

$V_4 = -\frac{2}{6} V_3 = -\frac{1}{3} V_3$

$V_4 = \frac{+1}{3} (\pm 15) = \pm 5V$

V3	$\pm 15V$
V4	$\pm 5V$