

ECSE 2010
Electric Circuits
Exam 2
Spring 2007

Name _____

Section (please circle one)

MR
10-12
Millard

MR
2-4
Abouzeid


Problem No.	Pts.	Score
1	10pts	
2	25pts	
3	25pts	
4	20pts	
5	20pts	
Total	100pts	

Please Note:

- * Place all your answers in the spaces provided.
- * You MUST show your work to receive any credit.
- * **Assume ALL sources are turned ON at $t=0$, unless noted otherwise.**

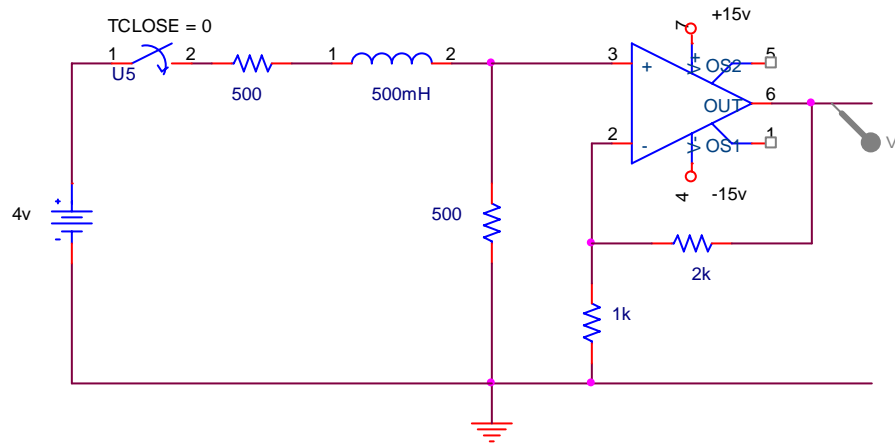Problem 1 (10pts)


Find an expression for $V(t)$ in the circuit shown for $t \geq 0$ (at the output of the Op Amp).



$V(t)$	
--------	--

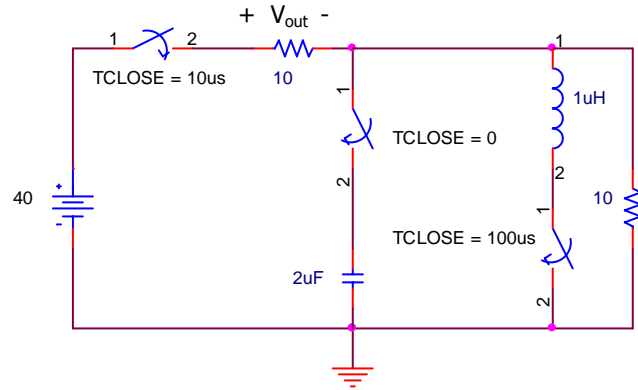Problem 2 (25pts)


a.) Find V_{out} (across the 10 ohm resistor) at each of the times indicated for the circuit shown, assuming that no energy was stored before $t=0$. (15pts)



$V_{out} (10\mu s^+)$	
$V_{out} (100\mu s^+)$	
$V_{out} (500\mu s^+)$	



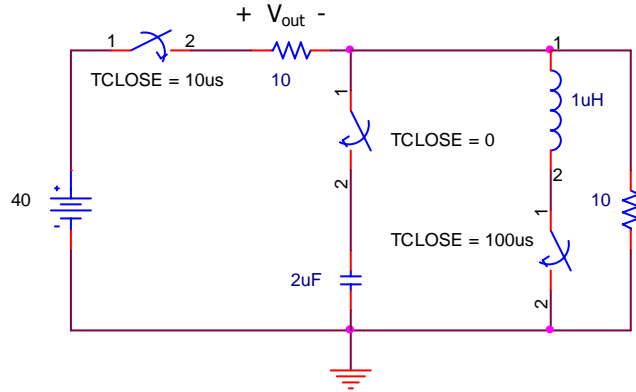
Problem 2 (cont)

b.) Sketch $V_{out}(t)$ (across the 10ohm resistor) for $0 \leq t < 500\mu s$; showing **ALL** pertinent values at the critical points in time (e.g. time constants). (10pts)




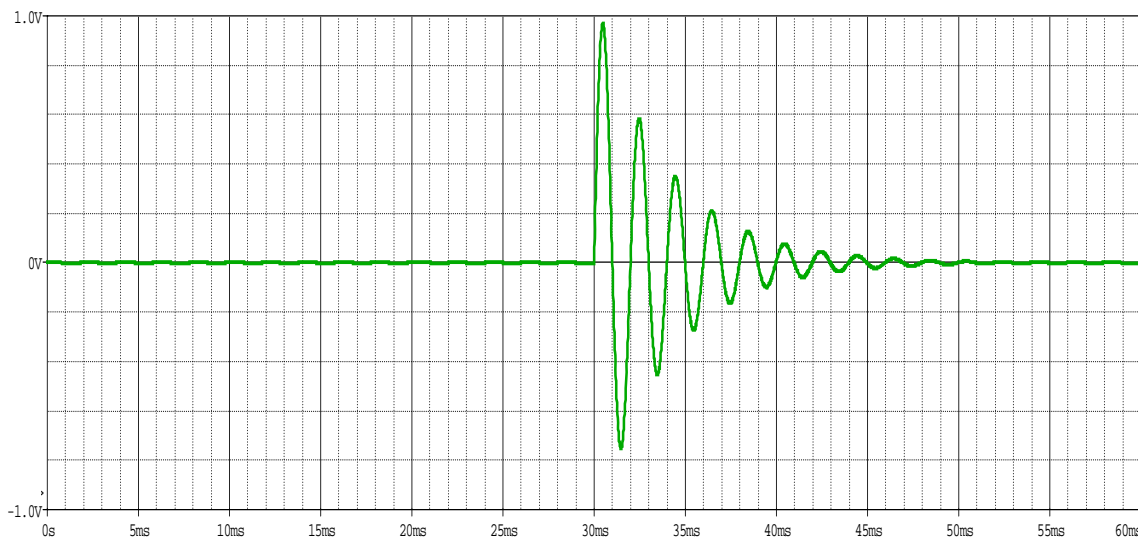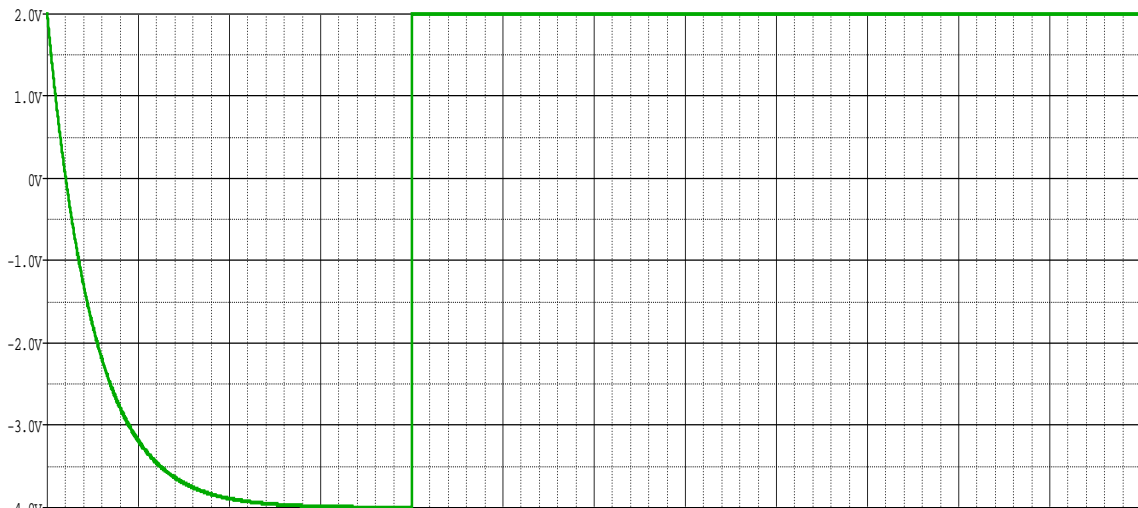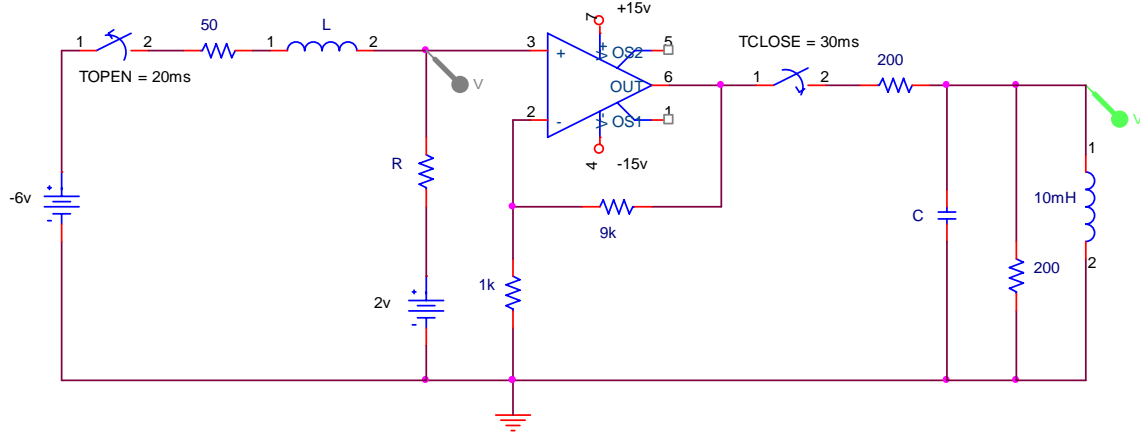Problem 3 (25pts)

Given the corresponding plots that result from the voltage markers in circuit shown; find the values of the circuit's components (L, R, and C).



Problem 3 (cont)

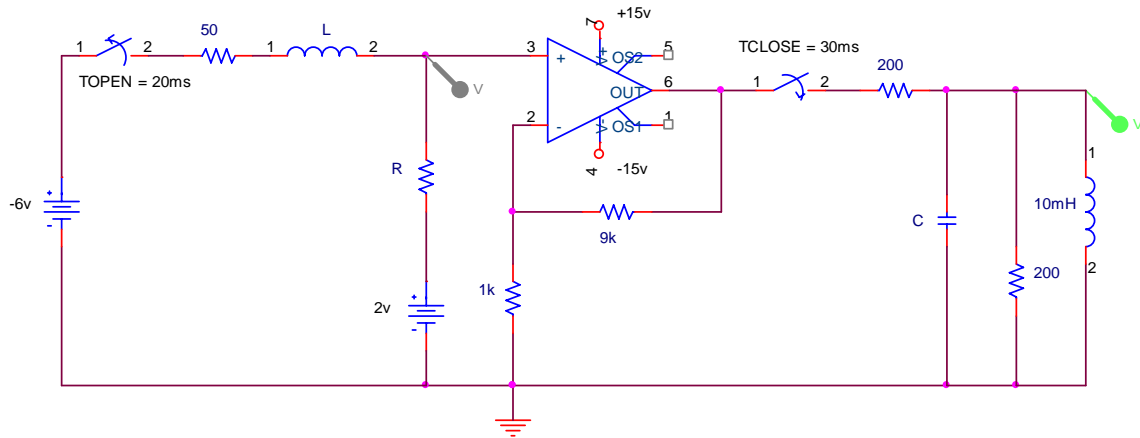

R (5pts)	
L (10pts)	
C (10pts)	


Problem 4 (20pts)

Name _____

A circuit has an output voltage whose Laplace transform is:

$$V_o(s) = \frac{200s}{(s^2 + 12s + 20)(s + 20)}$$

 a.) Sketch $V_o(t)$ for the circuit. (10pts)




Problem 4 (cont)

Name _____

Given:
$$V_o(s) = \frac{200s}{(s^2 + 12s + 20)(s + 20)}$$

 b.) Sketch the pole/zero diagram of $V_o(s)$. (5pts)




c.) Find the initial value of $V_o(t)$ as $t \rightarrow 0$. (5pts)

$V_o(t)$	
----------	--

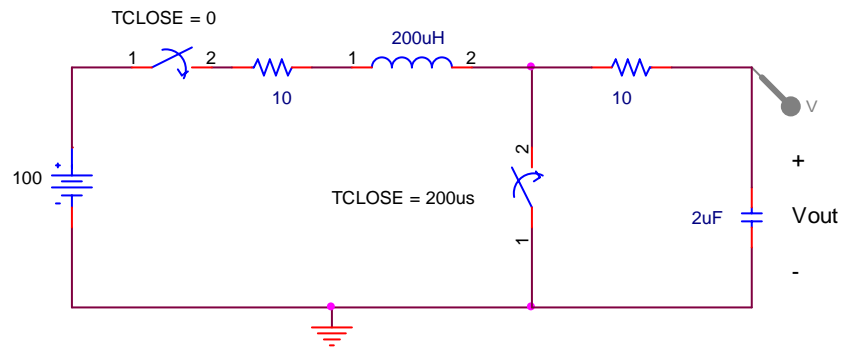Problem 5 (20pts)


- a.) Assume there is no stored energy in the L or C prior to $t=0$. Find $V_{out}(t)$ (across the capacitor) in the circuit shown for $t > 200\mu s$. (5pts)



$V_{out}(t)$	
--------------	--

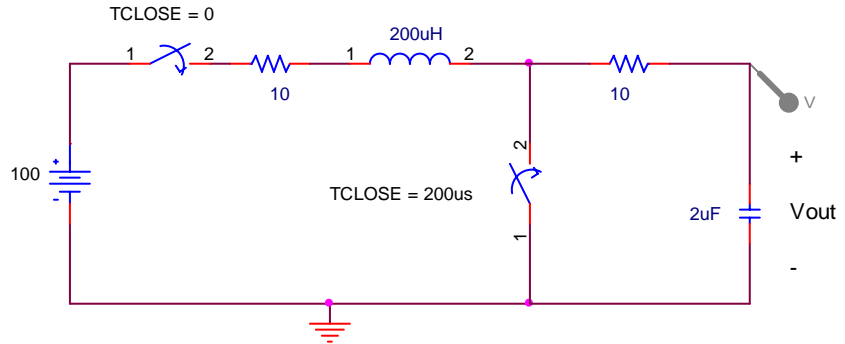Problem 5 (cont)

b.) Find the response type (over, critically, or under) and $V_{out}(t)$ (across the capacitor) in the circuit shown for $t < 200\mu s$. (15pts)



Type	
$V_{out}(t)$	

Extra space (if needed)

Name _____

Extra space (if needed)

Name _____

Laplace Transform Theorems

- | | |
|-----------------------------|--|
| 1. Definition | $L[f(t)] = F(s) = \int_{0^-}^{\infty} f(t)e^{-st} dt$ |
| 2. Linearity | $L[k_1 f(t_1) + k_2 f(t_2)] = k_1 F_1(s) + k_2 F_2(s)$ |
| 3. Time shift | $L[f(t - \tau)] = e^{-\tau s} F(s)$ |
| 4. Frequency Shift | $L[e^{-at} f(t)] = F(s + a)$ |
| 5. Scaling Theorem | $L[f(at)] = \frac{1}{a} F\left(\frac{s}{a}\right)$ |
| 6. Differentiation Theorem | $L\left[\frac{df}{dt}\right] = sF(s) - f(0)$ |
| 7. Differentiation Theorem | $L\left[\frac{d^2 f}{dt^2}\right] = s^2 F(s) - sf(0) - \dot{f}(0)$ |
| 8. Differentiation Theorem | $L\left[\frac{d^n f}{dt^n}\right] = s^n F(s) - \sum_{k=1}^n s^{n-k} f^{(k-1)}(0)$ |
| 9. Integration Theorem | $L\left[\int f(\tau) d\tau\right] = \frac{F(s)}{s} + \frac{\int_{0^-}^{0^+} f(\tau) d\tau}{s}$ |
| 10. Final value theorem* | $f(\infty) = \lim_{s \rightarrow 0} sF(s)$ |
| 11. Initial value theorem** | $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$ |

* Provided all poles of $F(s)$ have negative real parts with the exception of possibly one pole at the origin.

** Provided $f(t)$ is continuous or has a step discontinuity at $t = 0$.

Laplace Transform of Time Functions

1. $\delta(t)$	1
2. $u(t)$	$1/s$
3. $tu(t)$	$1/s^2$
4. $\frac{1}{2!}t^2u(t)$	$1/s^3$
5. $\frac{1}{(m-1)!}t^{m-1}u(t)$	$1/(s^m)$
6. $e^{-at}u(t)$	$1/(s+a)$
7. $te^{-at}u(t)$	$1/(s+a)^2$
8. $\frac{1}{(m-1)!}t^{m-1}e^{-at}u(t)$	$1/(s+a)^m$
9. $(1-e^{-at})u(t)$	$a/[s(s+a)]$
10. $\frac{1}{a}(at-1+e^{-at})u(t)$	$a/[s^2(s+a)]$
11. $(1-at)e^{-at}u(t)$	$s/(s+a)^2$
12. $\sin(\omega t)u(t)$	$\omega/(s^2+\omega^2)$
13. $\cos(\omega t)u(t)$	$s/(s^2+\omega^2)$
14. $e^{-at}\cos(\omega t)u(t)$	$(s+a)/[(s+a)^2+\omega^2]$
15. $e^{-at}\sin(\omega t)u(t)$	$\omega/[(s+a)^2+\omega^2]$
16. $\left\{1 - \frac{1}{\sqrt{1-\zeta^2}}e^{-\zeta\omega_n t}[\sin(\omega_d t + \theta)]\right\}u(t)$	
$\omega_d = \omega_n\sqrt{1-\zeta^2}; \theta = \cos^{-1}(\zeta)$	
OR $\left\{1 - e^{-\zeta\omega_n t} \left[\cos(\omega_d t) + \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_d t) \right] \right\}$	$\frac{\omega_n^2}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$

$$F(s) = \frac{Bs + C}{s^2 + 2\alpha s + \omega_0^2}$$

$$L^{-1}[F(s)] = f(t)$$

17.

$$f(t) = Ae^{-\alpha t} \cos(\omega_d t + \phi), \text{ where}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \phi = \tan^{-1}\left(\frac{\alpha B - C}{\omega_d B}\right) \text{ and}$$

$$A = \sqrt{B^2 + \left(\frac{\alpha B - C}{\omega_d}\right)^2} = \frac{\sqrt{B^2 \omega_0^2 - 2\alpha BC + C^2}}{\omega_d}$$