

ECSE 2010
Electric Circuits
Exam 3
Spring 2008

Name Solutions - Don

Section (please circle one)

10-11

11-12


Problem No.	Pts.	Score
1	20pts	
2	30pts	
3	10pts	
4	25pts	
5	15pts	
Total	100pts	

Please Note:

- All your answers must be placed in the spaces provided.
- You **MUST** show your work to receive any credit.
- Assume ALL sources are turned ON at $t=0$, unless noted otherwise.
- **The Laplace transform of $10u(t) = 10/s$.**

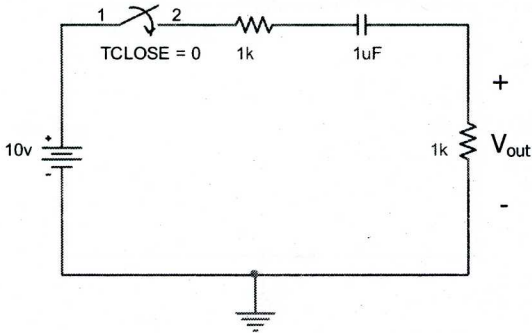Problem 1 (20pts)

a.) The switch is open for a long time before closing at $t = 1\text{ms}$ in the circuit shown below. Find $V_{\text{out}}(s)$ for $t \geq 1\text{ms}$ and sketch $V_{\text{out}}(t)$ for $t \geq 0$. (10pts)



$$V_{\text{input}}(s) = \frac{10}{s} \quad V_{\text{out}} = V_{\text{OSS}} + (V_{\text{OIN}} - V_{\text{OSS}}) e^{-t/\tau}$$


$$V_o(s) = \frac{1k}{2k + \frac{1}{sC}} \cdot \frac{\frac{3}{2k}}{\frac{3}{2k}}$$

$$V_o(s) = \frac{\frac{3}{2}}{s + \frac{1}{2kC}}$$

$V_{\text{out}}(s)$	$\frac{s/2}{s + \frac{1}{2kC}} \times \frac{10}{s}$
---------------------	---


$$\frac{3/2}{s + 500} \times \frac{10}{s}$$

$$\frac{5}{87500}$$

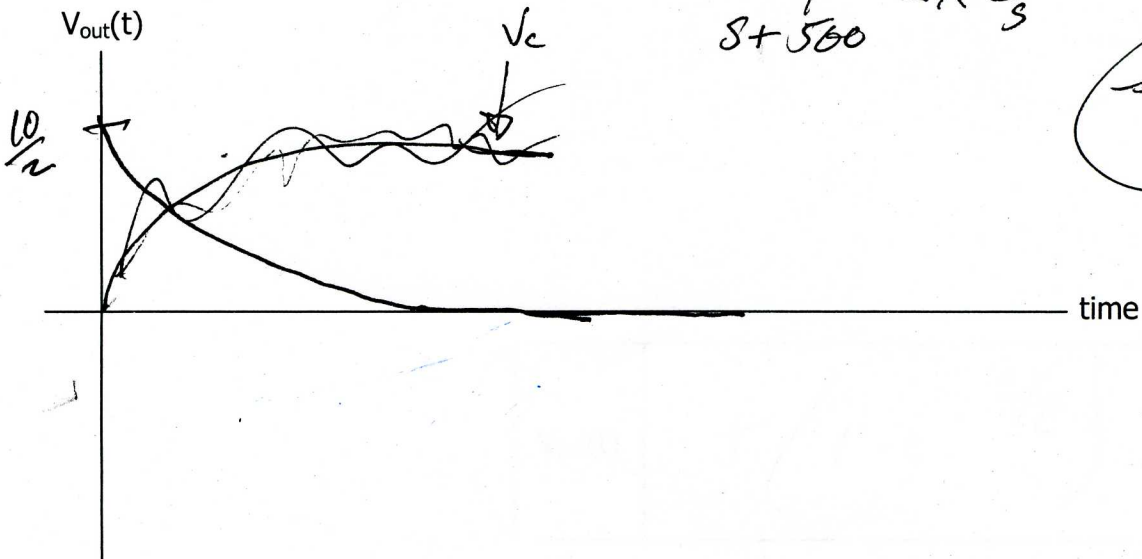

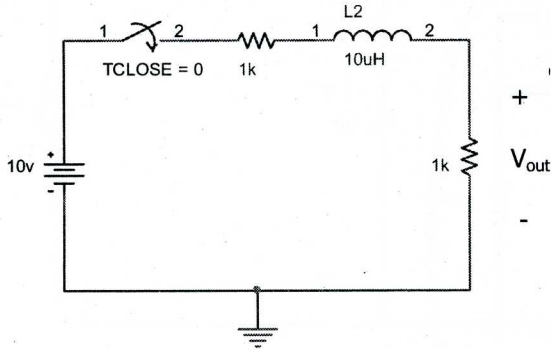
Problem 1 (cont)

b.) Find $V_{out}(t)$ for $t \geq 0$ given the circuit shown below, showing all pertinent values. (10pts) NOTE THIS IS A DIFFERENT CIRCUIT THAN PART A.




$V_{\text{ass}} = 5$
 $V_{\text{INIT}} = 0$

$$V_R = 5 + (0 - 5)e^{-t/\tau}$$

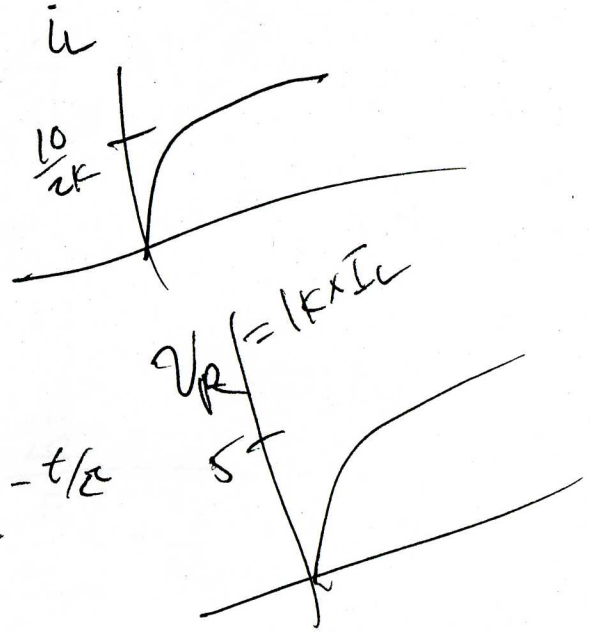

$V_{out}(t)$	$5 \left(1 - e^{-t/\tau} \right)$
--------------	------------------------------------

Problem 2 (30pts)

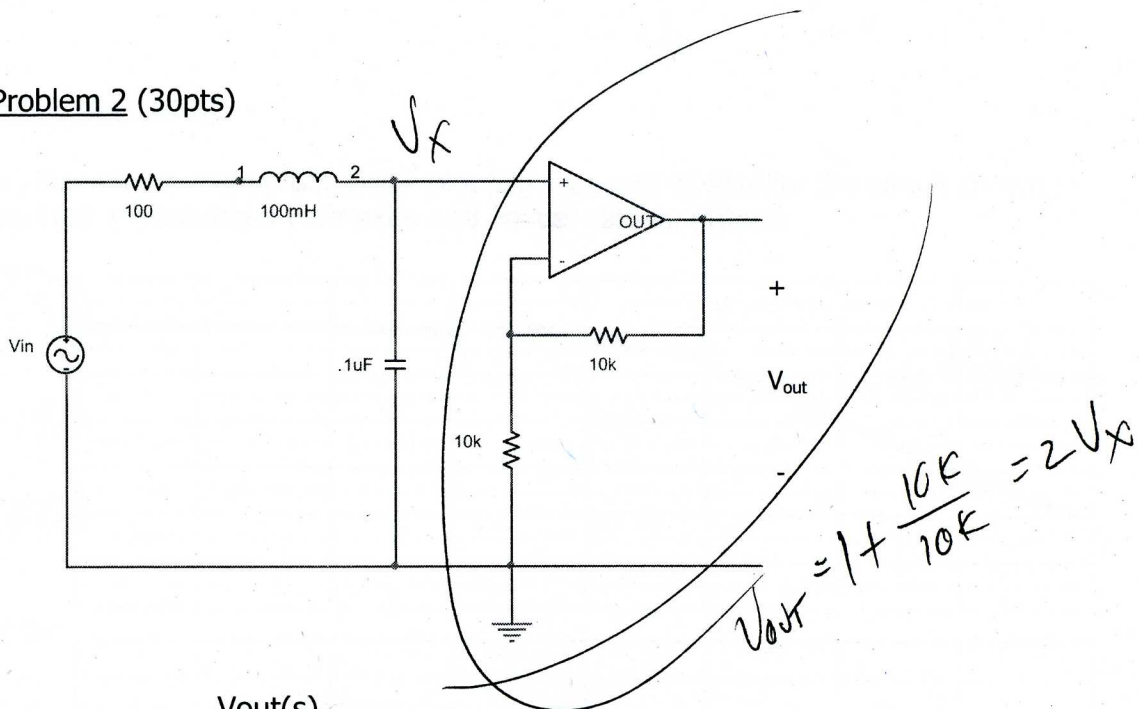

a.) Find $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$ for the above circuit. (10pts)

$$\frac{V_x}{V_{in}} = \frac{\frac{1}{sL}}{\frac{1}{sC} + R + sL} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$V_{out} = 2V_x ; H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{2 \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$


$H(s)$	$\frac{2 \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$
--------	--

10pts

$$\frac{2 (10,000)^2}{s^2 + 1000s + (10,000)^2}$$

Problem 2 (cont)

b.) Sketch the asymptotic Bode plot $|H(j\omega)|_{dB}$ and $\Phi H(j\omega)$ for the circuit shown in part (a). Please label your axes and critical values. (10pts)

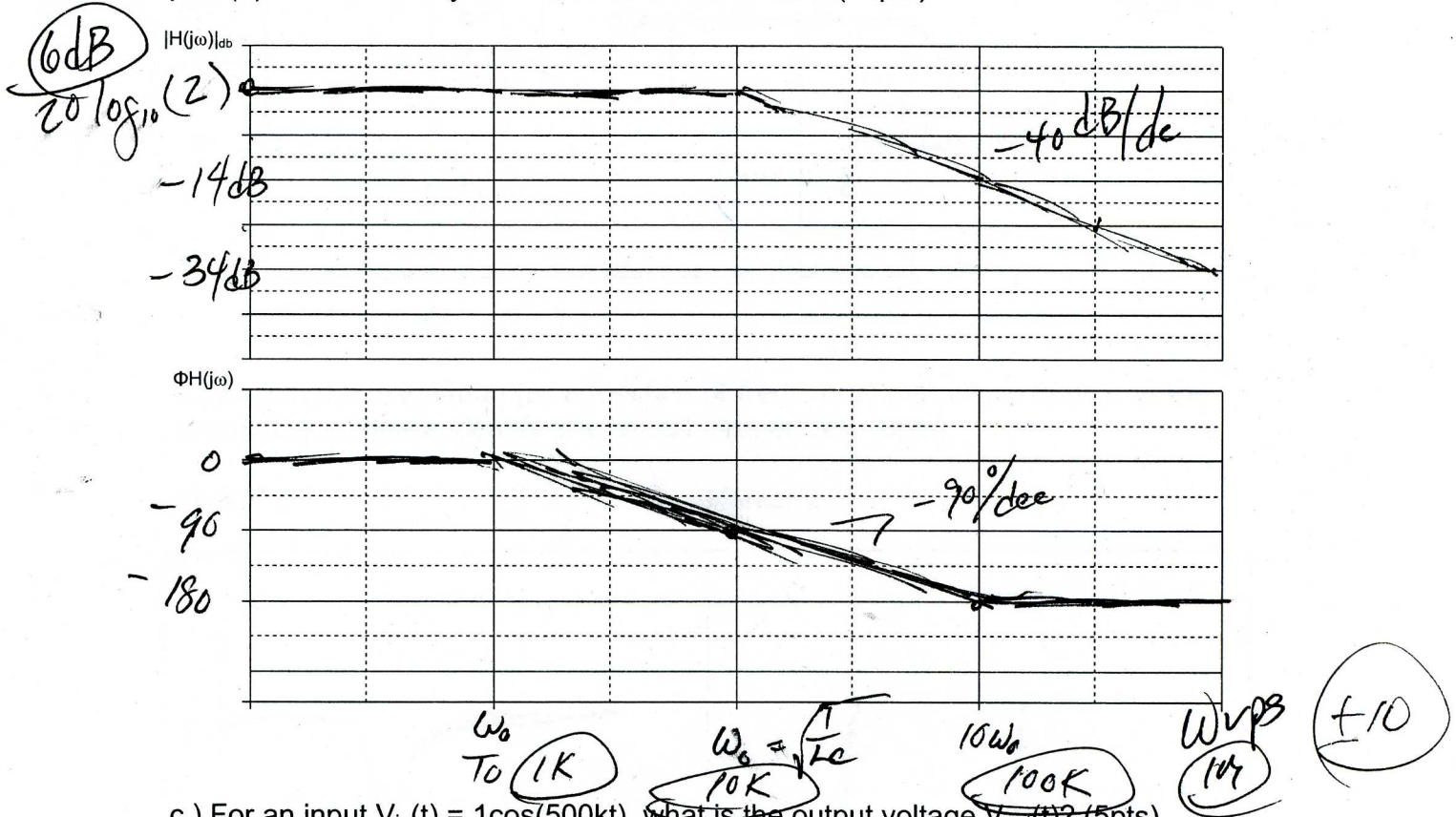

c.) For an input $V_{in}(t) = 1\cos(500kt)$, what is the output voltage $V_{out}(t)$? (5pts)

$|H(j500k)| \sim .06$

~~$\angle H(j500k) = 180$~~

	+2 +1 +2
$V_{out}(t)$	$.06 \cos(500kt - 180^\circ)$

(15)

d.) For an input $V_{in}(t) = 1\cos(1kt)$, what is the output voltage $V_{out}(t)$? (5pts)


$|H(j1k)| = 2$

~~$\angle H(j1k) = 0$~~

	+2 +1 +2
$V_{out}(t)$	$2 \cos(1kt)$

(15)

Problem 3 (10pts)

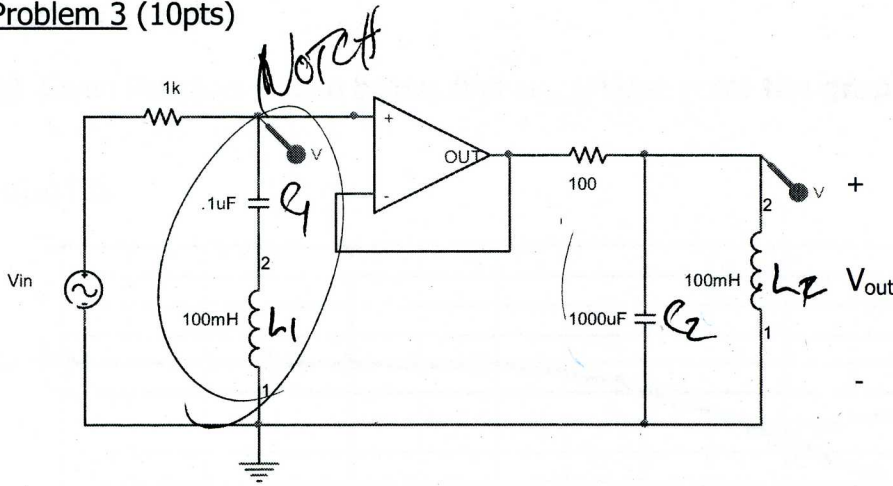


a.) Sketch the magnitude (as a function of frequency) that would appear at the two markers. Please identify any critical frequencies. (6pts)

Marker 1

x3

Marker 2

x2

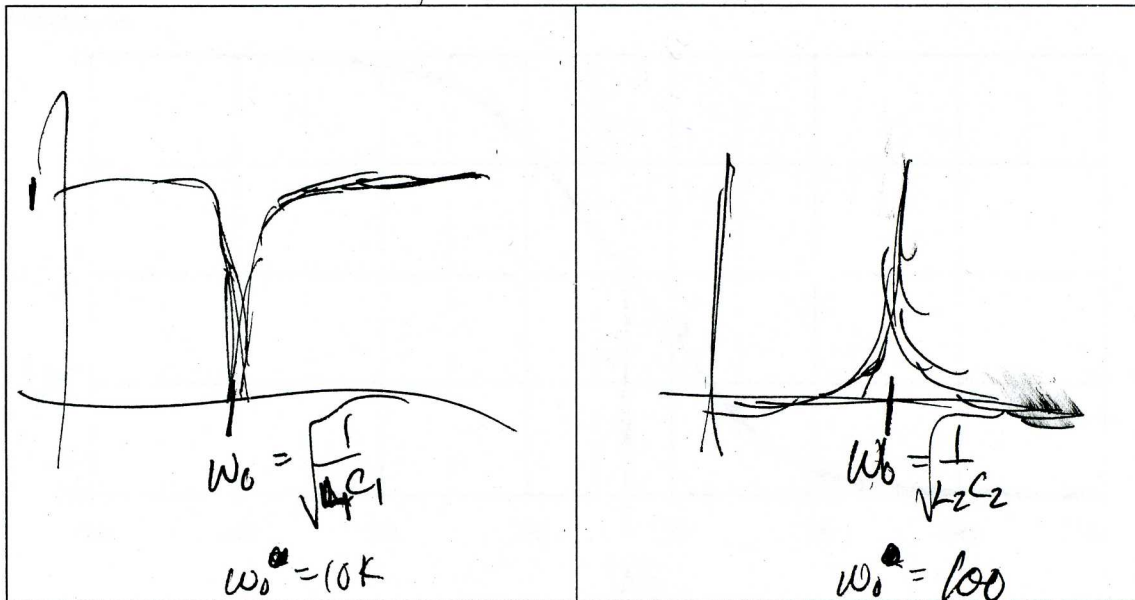

b.) What is $V_{out}(t)$ for $V_{in}(t) = 1\cos(\omega_0 t)$, where ω_0 is the resonant frequency? Please justify your response. (4pts)

x2 ⊗ If it is ω_0 for #1 →
 then $V_{out} = 0$

x2 ⊗ If it is ω_0 for #2
 then $V_{out} = V_{in}$

$$\omega_{01}^2 =$$

$$\omega_{02}^2 = 10K$$

