

Exam-01

1. Consider a transmission line (T-line) with length $\ell > 2\lambda$ that is terminated with a load $Z_L = (1/2) Z_0$.
 - (a) Draw, with amplitudes properly scaled, a (i) forward-propagating voltage wave and (ii) backward-propagating voltage wave for a lossless T-line.
 - (b) Draw a (i) forward-propagating voltage wave and (ii) backward-propagating voltage wave for a lossy T-line.
 - (c) Next consider that $Z_{\text{Load}} = 0$ and $\ell = 5/4 \lambda$. For a lossless T-line, draw the resulting standing voltage wave and indicate the locations of nodes and antinodes.
2. Consider and plot a coordinate system in the complex plane with the abscissa (horizontal axis) “Re” and the ordinate (vertical axis) “j Im”.
 - (a) Plot the points of the attenuation constant α for a (i) lossless, (ii) weakly lossy, and (iii) strongly lossy transmission line for a sinusoidal wave propagating on the line.
 - (b) Plot the points of the propagation constant γ for a (i) lossless, (ii) weakly lossy, and (iii) strongly lossy transmission line for the wave.
 - (c) Plot the point of γ if the wave would propagate in free space (vacuum).
 - (d) Next plot a new complex coordinate system. Assume that the T-line is terminated by an (i) open circuit (OC) and (ii) short circuit (SC). Plot the point of the voltage reflection coefficient Γ for each case.
 - (e) The T-line is now terminated by a capacitor. Plot the point of the voltage reflection coefficient Γ for (i) $\omega \rightarrow 0$, (ii) $\omega \rightarrow \infty$, and (iii) a finite ω .
3. A lossless transmission line (T-line) with a characteristic impedance of $Z_0 = 50 \Omega$ consumes 30 mA when a sinusoidal signal of 1.0 V is applied to its input. Assume that the T-line’s input impedance, Z_{Input} , and characteristic impedance, Z_0 , are purely resistive.
 - (a) What is the input impedance, Z_{Input} , of the T-line?
 - (b) Assume that the sinusoidal signal propagating on the T-line has a wavelength of 30 cm and that the length of the T-line is 1.5 m. What is the voltage reflection coefficient, Γ , at the end of the T-line?
 - (c) What is the load impedance, Z_{Load} , of the T-line?
4. Are the following statements (i) true, (ii) false, or (iii) impossible to determine due to lack of information?
 - (a) A T-line with length $\ell = \lambda/4$ acts as a short circuit (SC) at its input side.
 - (b) In the context of T-lines, “improving the conductance G' ” means “reducing the numerical value of G' ”.
 - (c) The G' of a coaxial T-line can be reduced by replacing the dielectric material between the center conductor and the outer conductor with vacuum.
 - (d) The phase constant β of a lossless transmission line increases with the frequency of the propagating wave.