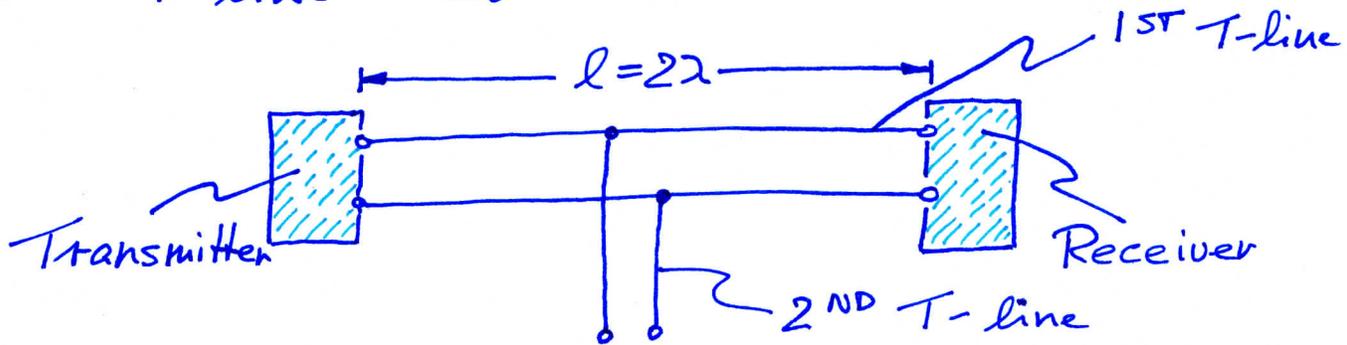


Exam - 01 - Solution

Q1

1ST T-line $Z_0 = 50 \Omega$ $l = 2\lambda$ 2ND T-line $Z_0 = 50 \Omega$

(a)

(b) 2ND T-line is lossless $l = \frac{1}{4}\lambda$

OC (open circuit) termination

Signal change at receiver = ?

2ND T-line has length $\frac{1}{4}\lambda$ so that signal travels distance $\frac{1}{2}\lambda$ (forward & backward).

Termination = OC

$$\Rightarrow \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1 - Z_0/Z_L}{1 + Z_0/Z_L} = 1$$

↳ Phase shift $\Delta\phi = 0$

$$\text{Total phase shift} = \pi + 0 = \pi$$

↳ Termination
↳ Due to distance $\frac{1}{2}\lambda$

 \Rightarrow Destructive interference. \Rightarrow Voltage at beginning of 2ND T-line is zero. \Rightarrow $\frac{\lambda}{4}$ line acts as a short circuit.

⇒ Signal at Receiver will be zero or strongly attenuated.

(c) There will not be a significant change at the receiver. The 2ND T-line is lossy, so that no standing-wave effect occurs. (We note that the Receiver signal will be somewhat smaller due to the 2ND T-line being in parallel with the 1ST T-line.)

(d) The 2ND T-line is very short, has a phase shift π (SC termination) so that destructive interference results.

⇒ Signal at Receiver will be zero or will strongly decrease.

Q2 $f = 1 \text{ GHz}$

$\lambda = 10 \text{ cm}$

(a) Phase velocity $\underline{v_{ph}} = \frac{\lambda}{T} = \lambda f = 0.1 \text{ m} \cdot 10^9 \frac{1}{\text{s}}$
 $= \underline{10^8 \frac{\text{m}}{\text{s}}}$

(this is about $\frac{1}{3}$ of c where $c = 3 \times 10^8 \frac{\text{m}}{\text{s}}$)

$\alpha = 0$ since the T-line is lossless

$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.1 \text{ m}} = \underline{20\pi \frac{1}{\text{m}}} = \underline{62.8 \frac{1}{\text{m}}}$

$\gamma = \alpha + j\beta = 0 + j 62.8 \frac{1}{\text{m}} = \underline{j 62.8 \frac{1}{\text{m}}}$

(b) Inductance per unit length = $L' = ?$

For a lossless T-line, we have

$\beta = \omega \sqrt{L' C'}$ or $\beta^2 = \omega^2 L' C'$


$\Rightarrow \underline{L'} = \frac{\beta^2}{\omega^2 C'} = \frac{(62.8 \frac{1}{\text{m}})^2}{(2\pi \cdot 10^9 \frac{1}{\text{s}})^2 \cdot 150 \times 10^{-12} \frac{\text{F}}{\text{m}}}$
 $= \frac{62.8^2 \frac{1}{\text{m}} \text{ m} \text{ s}^2}{(2\pi \times 10^9)^2 \cdot 150 \times 10^{-12} \text{ A} \cdot \text{s}} = 666 \times 10^{-9} \frac{\text{Vs}}{\text{A}} \frac{1}{\text{m}}$
 $= \underline{666 \frac{\text{nH}}{\text{m}}}$

(c) In order to improve the transmission line (T-line), I would propose to...

- * Use a better insulator between the inner and outer conductor of the coaxial line
- * Use a larger-cross-section metal conductor for the inner and/or outer conductor
- * Use a more conductive metal material, e.g. Ag, for the inner and/or outer conductor.

Q3 Transmission line termination

(a)

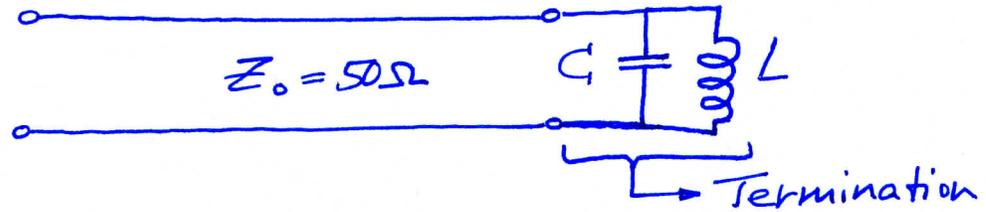

$$\begin{aligned}
 Z_L &= \left(\frac{1}{j\omega C} \right) \parallel (j\omega L) \\
 &\quad \downarrow \text{parallel} \\
 &= \frac{\frac{1}{j\omega C} \cdot j\omega L}{\frac{1}{j\omega C} + j\omega L} = \frac{j\omega L}{1 + j^2 \omega^2 LC} \\
 &= \frac{j\omega L}{1 - \omega^2 LC}
 \end{aligned}$$

(b) For $f = 0 \text{ Hz} \Rightarrow Z_L = 0$

$$\Rightarrow \underline{\underline{\Gamma}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \underline{\underline{-1}}$$

For $f = \infty \text{ Hz} \Rightarrow Z_L = 0$

$$\Rightarrow \underline{\underline{\Gamma}} = \underline{\underline{-1}}$$

For $\omega = 100 \text{ MHz} = 10^8 \text{ Hz}$

$$\begin{aligned}
 \Rightarrow Z_L &= \frac{j \cdot 10^8 \frac{1}{5} \cdot 10^{-8} \frac{\text{Vs}}{\text{A}}}{1 - 10^{16} \frac{1}{5^2} \cdot 10^{-8} \frac{\text{Vs}}{\text{A}} \cdot 10^{-8} \frac{\text{As}}{\text{V}}} \\
 &= \frac{j \Omega}{1 - 1} = \infty
 \end{aligned}$$

$$\begin{aligned}
 L &= 10 \text{ nH} \\
 &= 10^{-8} \frac{\text{Vs}}{\text{A}}
 \end{aligned}$$

$$\begin{aligned}
 C &= 10 \text{ nF} \\
 &= 10^{-8} \frac{\text{As}}{\text{V}}
 \end{aligned}$$

$$\Rightarrow \underline{\underline{\Gamma}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \underline{\underline{1}}$$

- * At $\omega = 0 \text{ Hz}$, the load is a short circuit (due to inductor). Therefore $\Gamma = -1$
- * At $\omega = \infty \text{ Hz}$, the load is a short circuit (due to capacitor). Therefore $\Gamma = -1$
- * At $\omega = 100 \text{ MHz} = \frac{1}{\sqrt{LC}}$, i.e. at resonance frequency, $Z_L = \infty$ so that $\Gamma = 1$

(c) When adding a resistive load, R , the voltage reflection coefficient Γ decreases in magnitude. That is, by adding a resistive load, impedance matching is improved.

Q4 (a) T-line: $l = \frac{7}{4}\lambda \Rightarrow 2l = \frac{14}{4}\lambda = \frac{7}{2}\lambda$ (7)

OC $\Rightarrow \Gamma = 1 \Rightarrow$ Phase shift = $\Delta\phi = 0$

Total phase shift = $\frac{7}{2}\lambda \frac{2\pi}{\lambda} + 0 = 7\pi \Rightarrow \pi$

\Rightarrow Destructive interference \Rightarrow Input behaves like a SC \Rightarrow True

(b) True

Transmission line is lossy \Rightarrow Wave is attenuated \Rightarrow No interference \Rightarrow Effect at input side is minimal.