

Exam-01

-
1. Consider a 1st $50\ \Omega$ transmission line (T-line), transmitting a sinusoidal signal with wavelength λ , having a length of $\ell = 2\lambda$, with an impedance-matched transmitter at one end and an impedance-matched receiver at the other end. Next we connect a 2nd $50\ \Omega$ T-line to the middle point of the 1st T-line. The 2nd T-line has various lengths and terminations.
 - (a) Draw the experimental setup and label all objects appropriately.
 - (b) Assume that the 2nd T-line is lossless, has a length of $\ell = (1/4)\lambda$, and is terminated by an OC (open circuit). Describe how the signal at the receiver changes when connecting the 2nd T-line.
 - (c) Assume that the 2nd T-line is lossy (so that the signal strength is negligible after having propagated for a length of $\ell = 10\lambda$), has a length of $\ell = 20\lambda$, and terminated by an SC (short circuit). Describe how the receiver signal changes when connecting the 2nd T-line.
 - (d) Assume that the 2nd T-line is lossless, has a length of $\ell = (1/100)\lambda$, and is terminated by an SC. Describe how the receiver signal changes when connecting the 2nd T-line.

 2. A sinusoidal 1 GHz wave propagating on a transmission line (T-line) has a wavelength of $\lambda = 10\text{ cm}$. Assume that the T-line is lossless and has a capacitance per unit length of $C' = 150\text{ pF/m}$.
 - (a) Calculate the phase velocity v_{phase} , attenuation constant α , phase constant β , and propagation constant γ ?
 - (b) Calculate the inductance per unit length, L' , of the T-line.
 - (c) Next, consider a different coaxial T-line; it is found to be too lossy for a certain application. You are charged with re-designing the T-line. Which specific design changes would you propose in order to improve the T-line?

 3. The termination of a $50\ \Omega$ transmission line (T-line) consists of a capacitor ($C = 10\text{ nF}$) in a parallel circuit to an inductor ($L = 10\text{ nH}$).
 - (a) Draw the electrical circuit of the termination. Calculate the impedance of the termination (symbolic expression).
 - (b) Determine the voltage reflection coefficient Γ at the angular frequencies $\omega = 2\pi f = 0\text{ Hz}$, 100 MHz , and $\infty\text{ Hz}$. Explain the results in your own words.
 - (c) Assume that a resistor R , in parallel to C and L , is added to the load. For $\omega = 100\text{ MHz}$, qualitatively describe how the voltage reflection coefficient Γ changes.

 4. Are the following statements (*i*) true, (*ii*) false, or (*iii*) impossible to determine due to lack of information?
 - (a) A lossless transmission line with length of $7/4\lambda$ that is terminated by an open circuit has a voltage node at its front end that acts like a short circuit.
 - (b) For very long lossy T-lines, there is no or little effect of the termination (Z_{Load}) on the input side of the T-line.