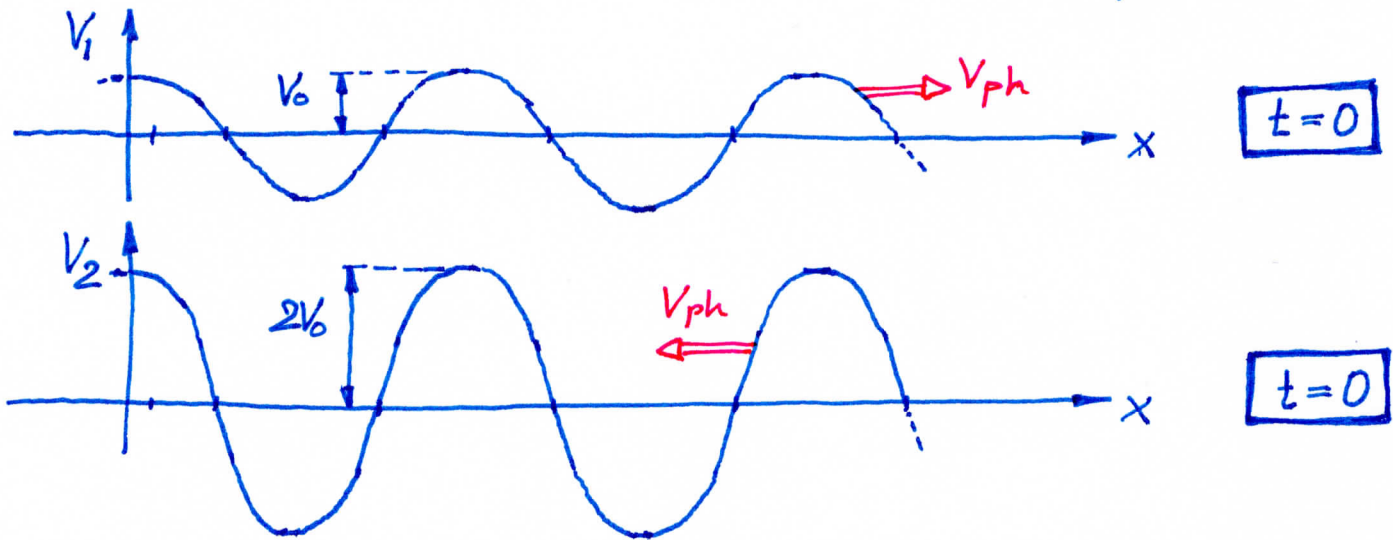


Transmission LinesProblem 1

(a) 1st wave: $V_1(x,t) = V_0 \cos(\beta x - \omega t)$ $\left\{ \begin{array}{l} \text{Forward propagating} \\ \text{Amplitude } V_0 \end{array} \right.$

2nd wave: $V_2(x,t) = 2V_0 \cos(\beta x + \omega t)$ $\left\{ \begin{array}{l} \text{Backward propagating} \\ \text{Amplitude } 2V_0 \end{array} \right.$



(b) $V = V_1 + V_2$

$$= V_0 \cos(\beta x - \omega t) + V_0 \cos(\beta x + \omega t) + V_0 \cos(\beta x + \omega t)$$

Using the trigonometric formula, one obtains:

$$V = \underbrace{2 \cos \beta x \cos \omega t}_{\text{Standing wave}} + \underbrace{V_0 \cos(\beta x + \omega t)}_{\text{Backward propagating wave}}$$

(c) The resulting wave is a superposition of (i) a standing wave and (ii) a backward moving wave. The resulting wave does not have nodes.

(d) α = Attenuation constant

$1/\alpha$ = Length after which the amplitude of the wave has decreased to $e^{-1} = 1/e$ of its initial value.

$1/\alpha$ has the units of length (meters)


Problem 2

$$C' = 2 \text{ nF/m}$$

$$L' = 10 \text{ nH/m}$$

$$f = 100 \text{ MHz}$$

(a) Lumped circuit model

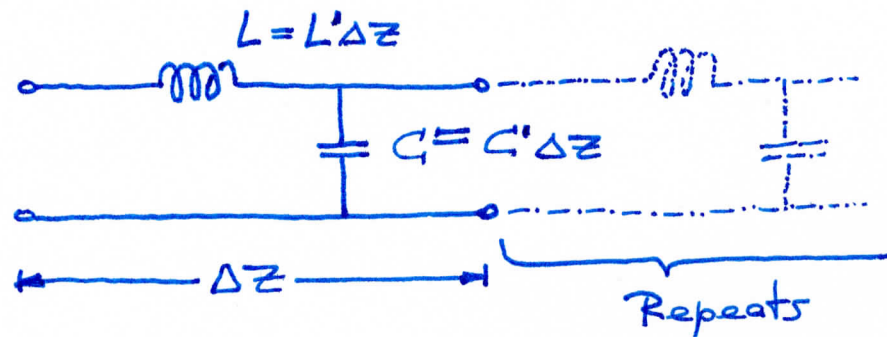

$$\text{Phase constant of wave} = \beta = \frac{2\pi}{\lambda} = \omega \sqrt{L' C'}$$

$$\beta = 2\pi \cdot 100 \times 10^6 \frac{1}{\text{s}} \sqrt{10 \times 10^{-9} \frac{\text{Vs}}{\text{Am}} \cdot 2 \times 10^{-9} \frac{\text{As}}{\text{Vm}}}$$

$$= 2\pi \cdot 10^{-1} \sqrt{20} \frac{1}{\text{m}} = 2\pi \cdot 0.447 \frac{1}{\text{m}} = 2.81 \frac{1}{\text{m}}$$

$$\beta = \frac{2\pi}{\lambda} \Rightarrow \underline{\underline{\lambda}} = \frac{2\pi}{\beta} = \frac{2\pi}{2.81} \text{ m} = \underline{\underline{2.24 \text{ m}}}$$

(b) Phase velocity in free space = $\underline{\underline{c}} = \underline{\underline{3 \times 10^8 \frac{\text{m}}{\text{s}}}}$

Phase velocity on transmission line = $\underline{\underline{v_{ph}}}$

$$v_{ph} = \frac{\lambda}{T} = \lambda f = 2.24 \text{ m} \cdot 10^8 \frac{1}{\text{s}} = \underline{\underline{2.24 \times 10^8 \frac{\text{m}}{\text{s}}}}$$

(c) Wires become resistive due to aging.

Insulator still in perfect condition.

Attenuation of wave:

$$V(x) = V_0(x=0) e^{-\alpha x}$$

$$V(x_0) = V_0(x=0) \left(\frac{1}{2}\right)$$

↳ 50%

$$\Rightarrow e^{-\alpha x_0} = \frac{1}{2} \quad \Rightarrow \quad -\alpha x_0 \underbrace{\ln e}_1 = \ln \frac{1}{2}$$

$$\Rightarrow \underline{\alpha} = \frac{-1}{x_0} \ln \frac{1}{2} = \frac{-1}{500\text{m}} \ln \frac{1}{2} = \underline{\underline{0.00139 \frac{1}{\text{m}}}}$$

(d) $R' \neq 0$ (Wires have become resistive)


$G' = 0$ (Insulator is perfect)

Problem 3

$$V(x,t) = V_0 \sin(\beta x - \omega t)$$

Transmission line with length l and wave impedance Z_0 . Termination with L .

(a)

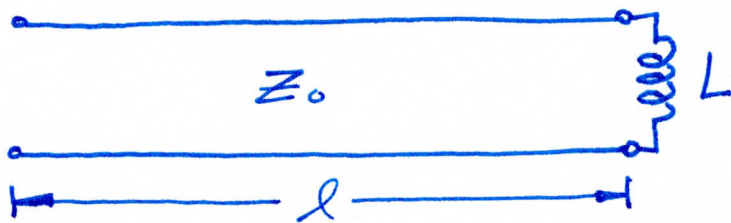

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j\omega L - Z_0}{j\omega L + Z_0}$$

(b)

$$\Gamma = \frac{(j\omega L - Z_0)(j\omega L - Z_0)}{(j\omega L + Z_0)(j\omega L - Z_0)} = \frac{(j\omega L - Z_0)^2}{(j\omega L)^2 - Z_0^2}$$

$$= \frac{-1}{\omega^2 L^2 + Z_0^2} (j^2 \omega^2 L^2 - 2j\omega L Z_0 + Z_0^2)$$


$$= \frac{-1}{\omega^2 L^2 + Z_0^2} (-2j\omega L Z_0 + Z_0^2 - \omega^2 L^2)$$

Recall $Z = R_e + jI_m$

$$\Rightarrow R_{e,r} = \frac{-1}{\omega^2 L^2 + Z_0^2} (Z_0^2 - \omega^2 L^2)$$

$$\Rightarrow jI_{m,r} = \frac{-1}{\omega^2 L^2 + Z_0^2} (-j2\omega L Z_0)$$

Complex numbers

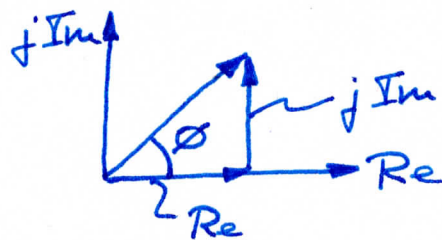

Phase angle $\tan \phi = \frac{Im}{Re}$

$$\Rightarrow \phi = \arctan \frac{Im}{Re} = \arctan \frac{-2\omega LZ_0}{Z_0^2 - \omega^2 L^2}$$

$$f \rightarrow 0 \Rightarrow \omega \rightarrow 0 \Rightarrow \underline{\Gamma = -1} \Rightarrow \underline{SC} \Rightarrow \phi = -\pi = -180^\circ$$

$$f \rightarrow \infty \Rightarrow \omega \rightarrow \infty \Rightarrow \underline{\Gamma = 1} \Rightarrow \underline{OC} \Rightarrow \phi = 0 = 0^\circ$$

(c) $f = 0.1 \text{ MHz}$ $Z_0 = 50 \Omega$ $L = 50 \mu\text{H}$ $\phi = ?$

$$\begin{aligned} \phi &= \arctan \frac{-2\omega LZ_0}{Z_0^2 - \omega^2 L^2} \\ &= \arctan \frac{-2 \cdot 2\pi \cdot 10^5 \cdot \frac{1}{s} \cdot 50 \times 10^{-6} \frac{Vs}{A} \cdot 50 \frac{V}{A}}{50^2 \frac{V^2}{A^2} - (2\pi)^2 \cdot 10^{10} \frac{1}{s^2} \cdot (50 \times 10^{-6})^2 \frac{V^2 s^2}{A^2}} \\ &= \arctan \frac{-3142}{2500 - 987} = \arctan(-2.077) \end{aligned}$$

$$\Rightarrow \underline{\phi = -64.3^\circ}$$

Note: **SC** = Short Circuit
OC = Open Circuit

Problem 4

(a) True

It is $v_{ph, T\text{-line}} \leq c$
 with $v_{ph} = \frac{\lambda}{T} = \lambda f$

Since $v_{ph, T\text{-line}} \leq c$

$\Rightarrow \lambda_{T\text{-line}} \leq \lambda_{\text{free space}}$

(b) False

Γ depends on Z_L . For example,
 if $Z_L = Z_0$ then $\Gamma = 0$.

(c) True

The transmission line is strongly
 attenuated so that Z_L becomes
 irrelevant.