

Name \_\_\_\_\_

**Part B (80 Points)**

- |                   |                   |
|-------------------|-------------------|
| 1. (10 Pts) _____ | 5. (12 Pts) _____ |
| 2. (16 Pts) _____ | 6. (16 Pts) _____ |
| 3. (10 Pts) _____ | 7. (11 Pts) _____ |
| 4. (5 Pts) _____  |                   |

Total \_\_\_\_\_

Be sure to simplify circuits into standard forms.

Draw circuit diagrams for all problems, especially re-draw as you simplify the circuits.

Be sure to fully annotate plots, even when the problem does not ask you to do this.

Show all of your work. Use the backs of pages if there is not enough room on the front.

Almost all problems can be solved using more than one method. Check your answers by using a second method.

At least skim through the entire quiz before you begin and then start with the problems you know best.

The proctor will only answer clarification questions where wording is unclear or where there may be errors/typos. No other questions will be responded to.

**Free Points:**

Problems 1 and 6 are required. For problems 2, 3, 4, 5 and 7, you can select up to 15 points worth of questions to not be graded. For these questions, you will receive half credit. Circle the letter or number associated with the questions that you would not like to be graded. Note that there are 16 individual question parts in problems 2-5 and 7. If you circle all 15 points, the maximum total grade you can receive for Quiz 1 is  $20 + 65 + 7.5 = 92.5$

**Granville T. Woods** (April 23, 1856 – January 30, 1910) The following comes from the Seattle Medium: ‘A sound argument can be made that Woods’ inventive genius was equal to if not superior to that of both Bell and Edison. During his brief life, Woods ... registered over 65 patents for electrical, mechanical, and communications devices which today we take for granted with virtually no awareness of their connection to (him). His inventions ranged from the electrified third rail common to most subway systems worldwide to 12 devices which modernized the railroad to an advanced telephone transmitter.’




‘Woods’ “advanced telephone transmitter” was so advanced ... that Alexander Graham Bell’s company purchased the rights to it ... because it was superior to what Bell had invented and out of fear that Woods might become a major competitor to the Bell company. Woods called his invention “telegraphony” featuring a combination of the best of the telegraph and the telephone.’

‘In 1887, he patented the Synchronous Multiplex Railway Telegraph which for the first time allowed communications between train stations and moving trains. It was this invention that ran him afoul of the powerful Thomas Alva Edison ... Edison sued Woods charging that he (Edison) was the first to invent the multiplex telegraph. After a costly court battle, Woods won the case. But even after losing to Woods, Edison remained so impressed with him that he offered the Black genius a partnership in one of his companies. In order to maintain his independence, Woods rejected the offer.’

As shown in these diagrams, his railroad communication system worked in a manner similar to modern cell phone near field communication. Coils were mounted under the rail car and in the track bed. He was probably the most important inventor for electrified railroads, like subways and even roller coasters.

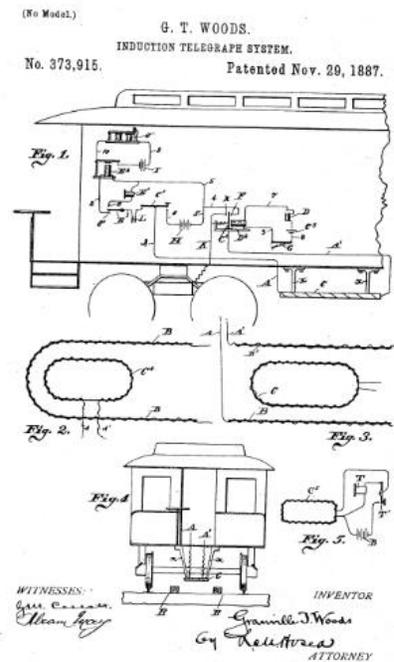Granville T Wood’s *Synchronous Multiplex Railway Telegraph* allowed for communication between moving trains and train depots, greatly improving railway safety.



**Inductance Specs – From Digilent Parts Kit Website****Electrical Specifications (@ 25 °C)**

| Part Number   | Inductance ( $\mu\text{H}$ ) | Tol.       | Q (Min.) | Test Frequency |          | SRF (MHz) Typ. | DCR ( $\Omega$ ) Max. | I dc (A) |
|---------------|------------------------------|------------|----------|----------------|----------|----------------|-----------------------|----------|
|               |                              |            |          | L              | Q        |                |                       |          |
| RL622-1R0K-RC | 1.0                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 150            | 0.013                 | 10       |
| RL622-1R5K-RC | 1.5                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 130            | 0.016                 | 8.5      |
| RL622-2R2K-RC | 2.2                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 100            | 0.021                 | 6.5      |
| RL622-3R3K-RC | 3.3                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 79             | 0.025                 | 5.5      |
| RL622-4R7K-RC | 4.7                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 51             | 0.030                 | 4.3      |
| RL622-6R8K-RC | 6.8                          | $\pm 10\%$ | 20       | 7.96 MHz       | 7.96 MHz | 29             | 0.035                 | 3.7      |
| RL622-100K-RC | 10                           | $\pm 10\%$ | 50       | 2.52 MHz       | 2.52 MHz | 14             | 0.045                 | 3.0      |
| RL622-120K-RC | 12                           | $\pm 10\%$ | 50       | 2.52 MHz       | 2.52 MHz | 13             | 0.050                 | 2.7      |
| RL622-150K-RC | 15                           | $\pm 10\%$ | 40       | 2.52 MHz       | 2.52 MHz | 12             | 0.056                 | 2.3      |
| RL622-180K-RC | 18                           | $\pm 10\%$ | 40       | 2.52 MHz       | 2.52 MHz | 11             | 0.061                 | 2.2      |
| RL622-220K-RC | 22                           | $\pm 10\%$ | 40       | 2.52 MHz       | 2.52 MHz | 9.2            | 0.070                 | 2.0      |
| RL622-270K-RC | 27                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 8.5            | 0.080                 | 1.7      |
| RL622-330K-RC | 33                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 7.8            | 0.090                 | 1.6      |
| RL622-390K-RC | 39                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 6.9            | 0.10                  | 1.5      |
| RL622-470K-RC | 47                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 6.5            | 0.16                  | 1.4      |
| RL622-560K-RC | 56                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 5.4            | 0.18                  | 1.3      |
| RL622-680K-RC | 68                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 4.9            | 0.21                  | 1.2      |
| RL622-820K-RC | 82                           | $\pm 10\%$ | 30       | 2.52 MHz       | 2.52 MHz | 4.1            | 0.23                  | 1.1      |
| RL622-101K-RC | 100                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 3.7            | 0.28                  | 0.91     |
| RL622-121K-RC | 120                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 3.4            | 0.32                  | 0.84     |
| RL622-151K-RC | 150                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 3.2            | 0.37                  | 0.75     |
| RL622-181K-RC | 180                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 2.8            | 0.58                  | 0.69     |
| RL622-221K-RC | 220                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 2.7            | 0.65                  | 0.64     |
| RL622-271K-RC | 270                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 2.4            | 0.75                  | 0.57     |
| RL622-331K-RC | 330                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 2.3            | 0.85                  | 0.54     |
| RL622-391K-RC | 390                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 2.1            | 1.0                   | 0.48     |
| RL622-471K-RC | 470                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 1.9            | 1.1                   | 0.46     |
| RL622-561K-RC | 560                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 1.8            | 1.4                   | 0.41     |
| RL622-681K-RC | 680                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 1.6            | 1.6                   | 0.38     |
| RL622-821K-RC | 820                          | $\pm 10\%$ | 20       | 796 KHz        | 796 KHz  | 1.5            | 1.8                   | 0.38     |
| RL622-102K-RC | 1000                         | $\pm 10\%$ | 50       | 252 KHz        | 252 KHz  | 1.3            | 2.9                   | 0.29     |
| RL622-122K-RC | 1200                         | $\pm 10\%$ | 50       | 252 KHz        | 252 KHz  | 1.1            | 4.0                   | 0.13     |
| RL622-152K-RC | 1500                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 1.0            | 6.1                   | 0.08     |
| RL622-182K-RC | 1800                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 1.0            | 6.4                   | 0.08     |
| RL622-222K-RC | 2200                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.9            | 6.8                   | 0.08     |
| RL622-272K-RC | 2700                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.9            | 7.7                   | 0.08     |
| RL622-332K-RC | 3300                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.7            | 9.0                   | 0.08     |
| RL622-392K-RC | 3900                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.6            | 14                    | 0.08     |
| RL622-472K-RC | 4700                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.5            | 16                    | 0.05     |
| RL622-562K-RC | 5600                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.4            | 18                    | 0.05     |
| RL622-682K-RC | 6800                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.4            | 19                    | 0.05     |
| RL622-822K-RC | 8200                         | $\pm 10\%$ | 20       | 252 KHz        | 252 KHz  | 0.3            | 21                    | 0.05     |
| RL622-103K-RC | 10,000                       | $\pm 10\%$ | 40       | 79.6 KHz       | 79.6 KHz | 0.3            | 25                    | 0.05     |

| Standard Resistor Values ( $\pm 5\%$ ) |    |     |      |     |      |      |
|--|----|-----|------|-----|------|------|
| 1.0                                    | 10 | 100 | 1.0K | 10K | 100K | 1.0M |
| 1.1                                    | 11 | 110 | 1.1K | 11K | 110K | 1.1M |
| 1.2                                    | 12 | 120 | 1.2K | 12K | 120K | 1.2M |
| 1.3                                    | 13 | 130 | 1.3K | 13K | 130K | 1.3M |
| 1.5                                    | 15 | 150 | 1.5K | 15K | 150K | 1.5M |
| 1.6                                    | 16 | 160 | 1.6K | 16K | 160K | 1.6M |
| 1.8                                    | 18 | 180 | 1.8K | 18K | 180K | 1.8M |
| 2.0                                    | 20 | 200 | 2.0K | 20K | 200K | 2.0M |
| 2.2                                    | 22 | 220 | 2.2K | 22K | 220K | 2.2M |
| 2.4                                    | 24 | 240 | 2.4K | 24K | 240K | 2.4M |
| 2.7                                    | 27 | 270 | 2.7K | 27K | 270K | 2.7M |
| 3.0                                    | 30 | 300 | 3.0K | 30K | 300K | 3.0M |
| 3.3                                    | 33 | 330 | 3.3K | 33K | 330K | 3.3M |
| 3.6                                    | 36 | 360 | 3.6K | 36K | 360K | 3.6M |
| 3.9                                    | 39 | 390 | 3.9K | 39K | 390K | 3.9M |
| 4.3                                    | 43 | 430 | 4.3K | 43K | 430K | 4.3M |
| 4.7                                    | 47 | 470 | 4.7K | 47K | 470K | 4.7M |
| 5.1                                    | 51 | 510 | 5.1K | 51K | 510K | 5.1M |
| 5.6                                    | 56 | 560 | 5.6K | 56K | 560K | 5.6M |
| 6.2                                    | 62 | 620 | 6.2K | 62K | 620K | 6.2M |
| 6.8                                    | 68 | 680 | 6.8K | 68K | 680K | 6.8M |
| 7.5                                    | 75 | 750 | 7.5K | 75K | 750K | 7.5M |
| 8.2                                    | 82 | 820 | 8.2K | 82K | 820K | 8.2M |
| 9.1                                    | 91 | 910 | 9.1K | 91K | 910K | 9.1M |

| Type             | $R_{int}$<br>( $\Omega$ ) | $V_{oc}$<br>(V) | Capacity <sup>a</sup><br>continuous, to 1V/cell |        |       |        | Size<br>(in) | Weight<br>(gm) | Connec <sup>b</sup> | Comments                  |
|------------------|---------------------------|-----------------|---|--------|-------|--------|--------------|----------------|---------------------|---------------------------|
|                  |                           |                 | (mAh)   | @ (mA) | (mAh) | @ (mA) |              |                |                     |                           |
| <b>9V "1604"</b> |                           |                 |   |        |       |        |              |                |                     |                           |
| Le Clanche       | 35                        | 9               | 300   | 1      | 160   | 10     | 0.65x1x1.9   | 35             | S                   |                           |
| Heavy Duty       | 35                        | 9               | 400   | 1      | 180   | 10     | "            | 40             | S                   |                           |
| Alkaline         | 2                         | 9               | 500   | 1      | 470   | 10     | "            | 55             | S                   | 280mAh@100mA              |
| Lithium          | 18                        | 9               | 1000  | 25     | 950   | 80     | "            | 38             | S                   | Kodak Li-MnO <sub>2</sub> |


**Capacitance Standard Values**

| These fixed capacitor values are the most commonly found |    |     |      |       |      |     |    |     |      |        |    |
|--|----|-----|------|-------|------|-----|----|-----|------|--------|----|
| pF   | pF | pF  | pF   | μF    | μF   | μF  | μF | μF  | μF   | μF     | μF |
| 1.0  | 10 | 100 | 1000 | 0.01  | 0.1  | 1.0 | 10 | 100 | 1000 | 10,000 |    |
| 1.1  | 11 | 110 | 1100 |       |      |     |    |     |      |        |    |
| 1.2  | 12 | 120 | 1200 |       |      |     |    |     |      |        |    |
| 1.3  | 13 | 130 | 1300 |       |      |     |    |     |      |        |    |
| 1.5  | 15 | 150 | 1500 | 0.015 | 0.15 | 1.5 | 15 | 150 | 1500 |        |    |
| 1.6  | 16 | 160 | 1600 |       |      |     |    |     |      |        |    |
| 1.8  | 18 | 180 | 1800 |       |      |     |    |     |      |        |    |
| 2.0  | 20 | 200 | 2000 |       |      |     |    |     |      |        |    |
| 2.2  | 22 | 220 | 2200 | 0.022 | 0.22 | 2.2 | 22 | 220 | 2200 |        |    |
| 2.4  | 24 | 240 | 2400 |       |      |     |    |     |      |        |    |
| 2.7  | 27 | 270 | 2700 |       |      |     |    |     |      |        |    |
| 3.0  | 30 | 300 | 3000 |       |      |     |    |     |      |        |    |
| 3.3  | 33 | 330 | 3300 | 0.033 | 0.33 | 3.3 | 33 | 330 | 3300 |        |    |
| 3.6  | 36 | 360 | 3600 |       |      |     |    |     |      |        |    |
| 3.9  | 39 | 390 | 3900 |       |      |     |    |     |      |        |    |
| 4.3  | 43 | 430 | 4300 |       |      |     |    |     |      |        |    |
| 4.7  | 47 | 470 | 4700 | 0.047 | 0.47 | 4.7 | 47 | 470 | 4700 |        |    |
| 5.1  | 51 | 510 | 5100 |       |      |     |    |     |      |        |    |
| 5.6  | 56 | 560 | 5600 |       |      |     |    |     |      |        |    |
| 6.2  | 62 | 620 | 6200 |       |      |     |    |     |      |        |    |
| 6.8  | 68 | 680 | 6800 | 0.068 | 0.68 | 6.8 | 68 | 680 | 6800 |        |    |
| 7.5  | 75 | 750 | 7500 |       |      |     |    |     |      |        |    |
| 8.2  | 82 | 820 | 8200 |       |      |     |    |     |      |        |    |
| 9.1  | 91 | 910 | 9100 |       |      |     |    |     |      |        |    |

**Problem 1 (10 Points) – Basic Voltage Divider**

A voltage divider consisting of two resistors and a DC voltage source is configured as shown.

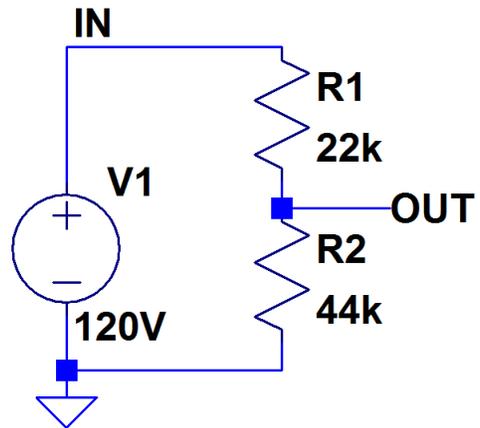a. Determine the output voltage across R2 (in Volts)




b. Determine the power delivered to the load R2 (in milli-Watts)

**Problem 2 (16 Points) – A Bit More Complicated Voltage Divider**

A somewhat more complicated voltage divider, consisting of more than the usual two resistors and DC source, is configured as shown.

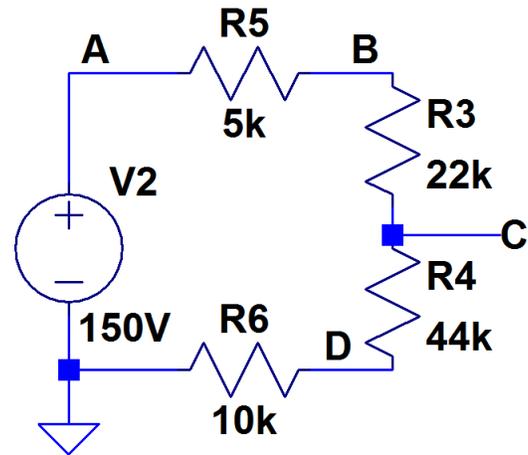
- a. (6 pts) Determine the voltages at B, C and D (in Volts)



- b. (4 pts) Determine the current through R5 (in milli-Amps)

The circuit is modified by replacing the 22kΩ & 44kΩ resistors R3 and R4 with resistors that are 10X larger.

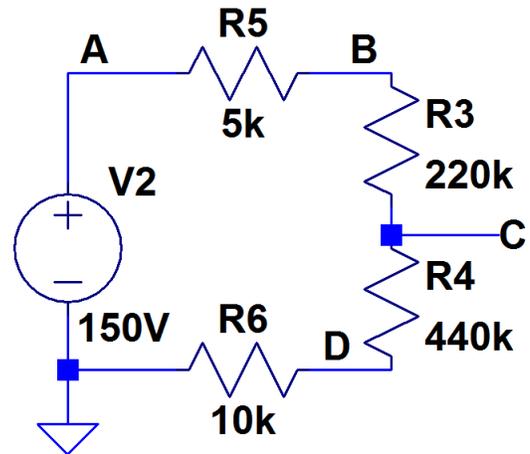
- c. (3 pts) Determine the voltage at C (in Volts)



- d. (3 pts) Determine the current through R5 (in milli-Amps)
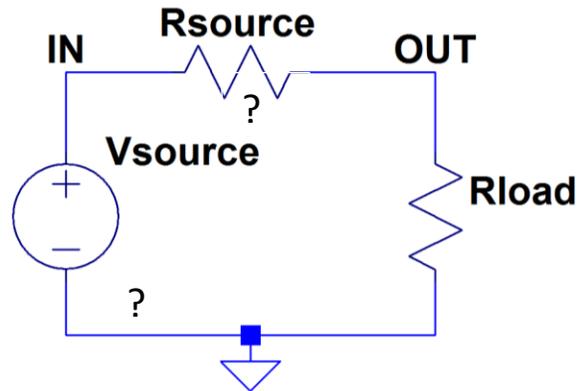
### Problem 3 (10 Points) – Source Characterization Using a Voltage Divider

Batteries and other voltage sources can generally be modeled by combining an ideal voltage source and a resistor. The circuit at the right is set up to study some kind of a black box DC voltage source. Six different load resistors are connected and the voltage  $V(\text{OUT})$  is measured. The results of the six trials are listed in the table below. *Note that there is more information than you need to find the source voltage and resistance. Note also that the source characteristics may be different than you have seen in class.*




| Trial | Rload | V(OUT) |
|-------|-------|--------|
| 1     | 1Ω    | .1V    |
| 2     | 3Ω    | .4V    |
| 3     | 10Ω   | 1.3V   |
| 4     | 30Ω   | 3.6V   |
| 5     | 100Ω  | 10.0V  |
| 6     | 300Ω  | 20.0V  |
| 7     | 1kΩ   | 30.8V  |
| 8     | 3kΩ   | 36.4V  |
| 9     | 10kΩ  | 38.8V  |
| 10    | 30kΩ  | 39.6V  |
| 11    | 100kΩ | 39.9V  |
| 12    | 300kΩ | 40.0V  |
| 13    | 1MΩ   | 40.0V  |

- Determine the source voltage  $V_{\text{source}}$  (in Volts)
- Determine the source resistance  $R_{\text{source}}$  (in Ohms)

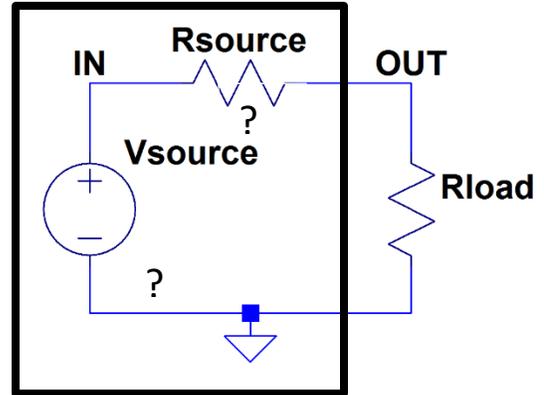
**Problem 4 (5 Points) – Measurements**

The black box circuit from the previous problem is redrawn at the right (with the box outline shown). What wires from your Analog Discovery board should be connected to this circuit (and where) to obtain the voltage information in the table? List the wires below and show their connection points on the circuit diagram. *There is more than one correct answer.*



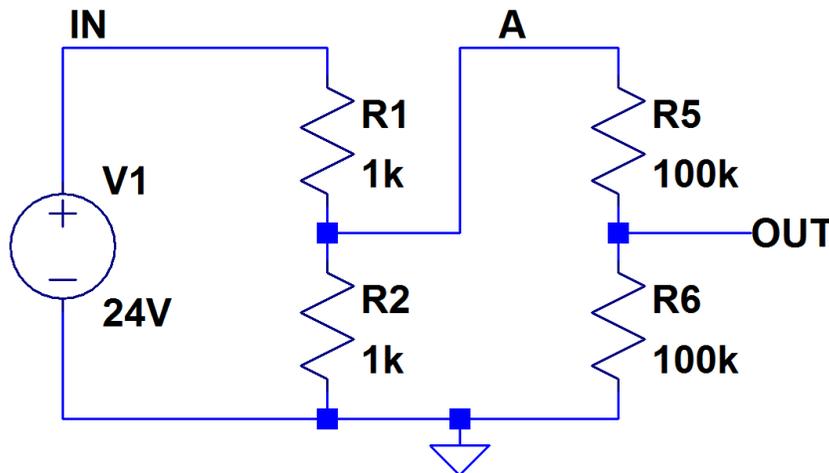**Problem 5 (12 Points) – Resistor Ladder Circuit**

A more complex circuit is formed by essentially connecting two voltage dividers. The voltage source is 24V DC, so that is the input voltage. The remainder of the circuit is built with resistor values: 1kΩ and 100kΩ.



.op

- a. (2 pts) Before beginning the analysis of this circuit, answer the following two general questions:
  - a. What is the approximate value for the series combination of two resistors,  $R_1$  and  $R_2$ , when  $R_1 \gg R_2$ ?
  - b. What is the approximate value for the parallel combination of two resistors,  $R_1$  and  $R_2$ , when  $R_1 \gg R_2$ ?

- b. (4 pts) Using the approximations of part a, find the voltages at node A and the output node OUT. This should give you voltages reasonably close to what LT-Spice can find for you.
- c. (2 pts) Assume that you replace resistors R5 and R6 with  $500\Omega$  resistors. Which of the following will be true?
- The voltages at nodes A and OUT will remain the same.
  - The voltages at nodes A and OUT will both increase.
  - The voltages at nodes A and OUT will both decrease.
  - The voltage at node A will increase while the voltage at node OUT will decrease.
  - The voltage at node A will decrease while the voltage at node OUT will increase.
- d. (4 pts) Now we want to see if the general prediction in part c is correct and, again, assume that R1 and R2 are equal to  $1\text{k}\Omega$ , while R5 and R6 are equal to  $500\Omega$  (as in part c), determine the voltages at nodes A and OUT.

### Problem 6 (16 Points) – Conceptual Questions

This problem contains some conceptual questions. The following addresses how to approach such questions, provided in the unlikely event that you have not seen such questions before.

A **conceptual question** is designed to help determine whether a student has an accurate working knowledge of a specific set of concepts. For example, from the background quiz you completed on the first day of class:

A 9V battery is connected across a 2k $\Omega$  resistor. If the resistor is replaced with a 10k $\Omega$  resistor, will the current from the battery

- Increase
- Decrease
- Stay about the same

This question tests conceptual knowledge of Ohm's Law. It can most rigorously be answered by recalling the relationship between voltage, current and resistance (the three parameters


mentioned directly or indirectly in the question).  $I = \frac{V}{R}$ . From this expression a larger  $R$  will

produce a smaller  $I$  for the same voltage (9V in this case). The answer does not depend on the exact values of the two resistances, only that a resistor is replaced with one that is larger. Then the current will be smaller, so the answer is b. Decrease.

**Conceptual Questions:** The answers for all questions are worth (2 pts) each, except where noted. Remember to briefly explain your answers.


a) Is the image shown at the right

- A short circuit?
- An open circuit?

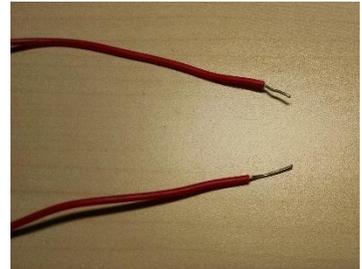

b) Is the image shown at the right


- A short circuit?
- An open circuit?

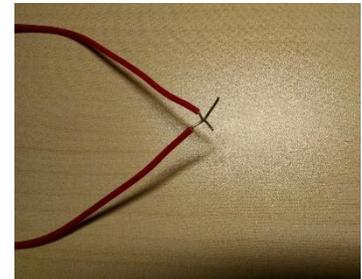

c) For the standard voltage divider configuration shown in part d), which of the following statements is true, for all values of resistance:

1. The voltage across each resistor is the same.
2. The current through each resistor is the same.

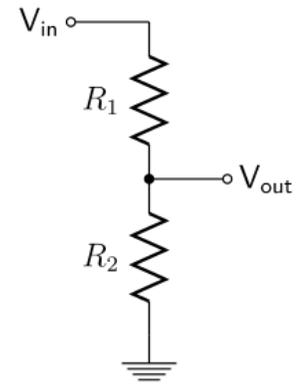d) In the standard voltage divider configuration shown at the right, resistor  $R_2$  is much larger than resistor  $R_1$ . Is the power dissipated in  $R_1$




1. Much greater than the power dissipated in  $R_2$
2. Much less than the power dissipated in  $R_2$
3. About the same as the power dissipated in  $R_2$

e) The configuration in part f) is a standard current divider. For this configuration, which of the following statements is true, for all values of resistance:

1. The voltage across each resistor is the same.
2. The current through each resistor is the same.

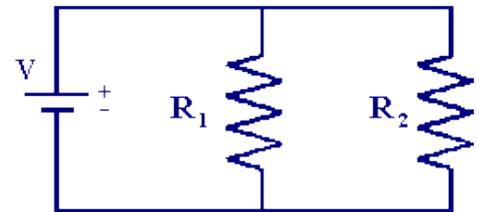f) In the circuit at the right, two resistors ( $R_2$  much larger than  $R_1$ ) are connected in parallel across a voltage source  $V$ . Is the power dissipated in  $R_1$



1. Much greater than the power dissipated in  $R_2$
2. Much less than the power dissipated in  $R_2$
3. About the same as the power dissipated in  $R_2$



For the next two questions, we return to the standard voltage divider configuration of part d).

g) For the standard voltage divider configuration, when  $R_2$  is a short circuit, the voltage across  $R_1$  will be (circle the correct answer): 0 or  $V_{in}$

h) For the standard voltage divider configuration, when  $R_2$  is an open circuit, the voltage across  $R_1$  will be (circle the correct answer): 0 or  $V_{in}$

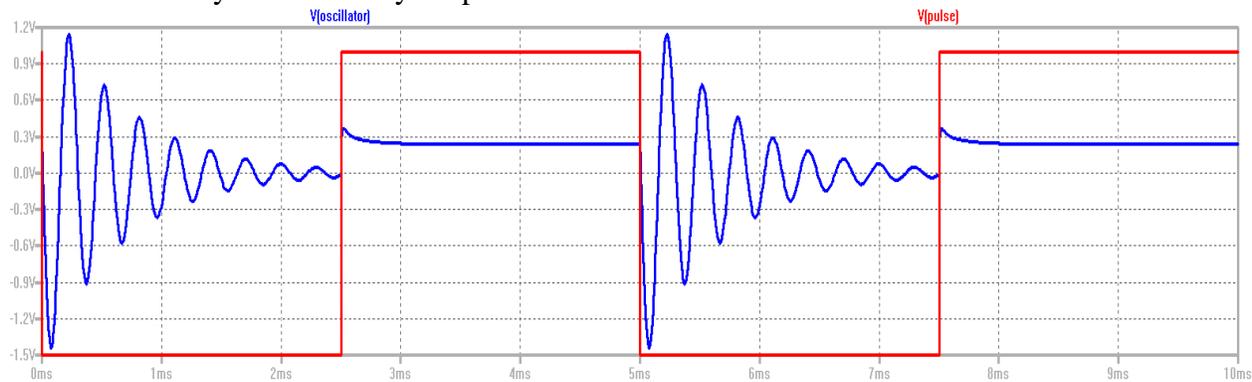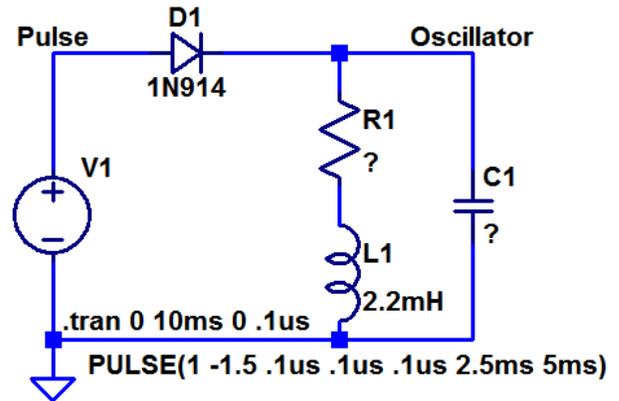**Problem 7 (11 Points) – LC Resonant Circuit Experiment**

The circuit at the right is similar to the one we studied in classes 5 and 7. A different inductor ( $L$  is given) and a different capacitor ( $C$  is unknown) are used. The resistance is also the DC Resistance of the inductor (also not given in the figure). The pulsed source is a square wave that is  $-1.5V$  when low and  $+1V$  when high. Two complete cycles of the Source and Oscillator voltages are shown below. The time scale is  $1ms/Div$  and the voltage scale is  $0.3V/Div$ . Recall that there are 10 divisions both horizontally and vertically. Express answers below to within 5%.



- (3 pts) What is the frequency of the Source square wave voltage  $V(\text{pulse})$ ?
- (3 pts) What is the frequency of the damped oscillation voltage  $V(\text{oscillator})$ ? *Hint: Can be found 2 ways, but one approach will be much easier.*
- (3 pts) What is the value of the capacitance? *Hint: The capacitor value is standard.*
- (2 pts) What is the value of the resistance? *Hint: The inductor is a standard component.*